Reg. No.



## V SEMESTER B.TECH (ELECTRICAL & ELECTRONICS ENGINEERING)

## END SEMESTER EXAMINATIONS, NOVEMBER 2019

## SUBJECT: POWER SYSTEM ANALYSIS [ELE 3105]

Date: 25 November 2019	Time : 3 Hours	Max. Marks: 15
Instructions to Candidates:		
✤ Answer ALL the questions.		

1A. The single line diagram of a two-machine system is as shown in Fig.1A. Draw the impedance diagram of the system choosing a base of 11.5 kV, 60 MVA in the motor circuit. The transformer  $T_2$  comprises of 3 single phase units each rated 15 MVA, 11/127 kV and 10% reactance.



**1B.** The three-phase ratings of a three winding transformer are:

Primary:Y connected 15MVA, 66kVSecondary:Y connected 10MVA, 13.2kVTertiary:Δ connected 5MVA, 2.3kV

Neglecting resistance, the leakage reactances are,  $x_{PS}=7\%$  and  $x_{PT}=9\%$  (both measured on primary);  $x_{ST}=8\%$  (measured on secondary). Calculate the per unit reactance of the per phase equivalent circuit for a base of 6 MVA, 86 kV in the primary circuit.

- 1C. Define the following: (i) Momentary current and (ii) Interrupting current as applied to the rating of a Circuit Breaker. Mention the suitable multiplication factors to determine the above currents in terms of respective symmetrical currents.
- **2A.** For the system shown in fig.2A, Calculate the fault current fed by  $G_1$  and  $G_2$  for a three-phase solid fault on the 132kV bus. Choose a base of 45MVA, 13.2kV on generator circuit. Neglect pre-fault current.

(05)

(02)

(06)



Fig. 2A

- **2B.** Derive the expression for 3 phase complex power in terms of symmetrical *(02)*
- **2C.** Compute the unbalanced currents  $I_a$ ,  $I_b$  and  $I_c$ , if the sequence components are  $I_{a1}=10+j9$  A,  $I_{a0}=0$  A and  $I_{a2}=$  4.5738-j0.6778 A. Assume abc sequence. (03)
- 3A. Derive an expression for the fault current when a short circuit fault occurs between lines `b' and `c' through a fault impedance Z<sub>f</sub>. Also show the interconnection of sequence networks for this fault.
- **3B.** Draw the sequence networks and the corresponding Thevenin's impedances when an unsymmetrical fault occurs at bus 2 shown in fig. 3B. The ratings of the components are given below  $G_1, G_2: 20 \text{ MVA}$ , star grounded through reactance, 11 kV,  $x_1=0.15 \text{ pu}$ ,  $x_2=0.1 \text{ pu}, x_0=0.05 \text{ pu}, x_n=0.03 \text{ pu}$   $T_1, T_2, T_3, T_4: 20 \text{ MVA}, 11/110 \text{ kV}, x=0.1 \text{ pu}$  Lines 1 & 2:  $x_1=x_2=0.1 \text{ pu}, x_0=0.35 \text{ pu}$  on a base of 20 MVA, 110 kV.



Fig. 3B

- **3C.** Two 6.6 kV, 3 phase 10 MVA alternators are connected to a common bus. Each alternator has  $x_1=0.15$  p.u.,  $x_2=0.1$  pu,  $x_0=0.05$  pu and  $x_n=0.06$  pu. An unsymmetrical fault occurs on the bus. Calculate the fault current in kA, if the fault is i) bolted (or solid) L-G, ii) L-L through a fault reactance of 0.01 pu and iii) solid L-L-G fault
- **4A.** A generator is transferring 1 per unit power to a load through a short line. A 3-phase fault occurs at the generator terminals. Use equal area criterion and find critical clearing angle & the corresponding time. Derive the formulae used. Given  $P_{max}=2$  pu (amplitude of power angle curve), H=6MJ/MVA, f=50 Hz.
- **4B.** A 200MVA, 11 kV, 50 Hz, 4 pole generator has H=6MJ/MVA. The machine is operating at a load of 120 MW when the load is suddenly increased to 160 MW. Find the rotor speed if the rotor deceleration is maintained for 5 cycles.

(03)

(05)

(03)

(04)

Page 2 of 3

- **4C.** Derive the expression for natural frequency of oscillation when an alternator is subjected to small changes in load.
- 5A. Eliminate node 3 by matrix algebra for the system shown in Fig.5A



Fig.5A

**5B.** Compute Jacobian elements for the system shown in Fig.5B at the end of one iteration using N-R method. Consider 100 MVA as the base.



Fig.5B

**5C.** Considering 100 MVA as base, find the voltages at buses 2 & 3 at the end of first iteration using G-S method for the system depicted in Fig.5C. Also find slack bus real & reactive power generation.



Fig.5C

(04)

(02)

(02)

(04)