Reg. No.



VII SEMESTER B.TECH (ELECTRICAL & ELECTRONICS ENGINEERING) END SEMESTER EXAMINATIONS, NOVEMBER 2019

SUBJECT: SWITCHGEAR AND PROTECTION [ELE 4101]

REVISED CREDIT SYSTEM

Time:	: 3 Hours	Date: 15 November 2019	Max. Ma	rks: 50
Instructions to Candidates:				
	✤ Answer ALL the question	15.		
	 Missing data may be suita 	ably assumed.		
1A.	Discuss Cassie's energy breaker.	balance theory of arc interruption in an A	C circuit	(03)
1B.	While disconnecting a p on its primary side can explain the phenomeno	oower transformer on no-load, the circuit encounter a severe duty. With neat way on encountered.	breaker veforms,	(03)
1C.	In a 3 phase, 220 kV s location of the circuit resistance of 600 Ω is breaker. Determine the	system, the reactance and capacitance u breaker are 8 Ω and 0.025 μ F, respects connected across the contacts of the following:	p to the tively. A e circuit	
	a) Natural frequency of	oscillations		
	b) Damped frequency o	of oscillations		
	c) Critical value of the r	resistance which will give no transient oso	cillations	
	d) Value of the resistance equal to one-fourth of t	ce which will give damped frequency of osc the natural frequency of oscillations.	cillations	(04)
2A.	Explain the construction neat diagram.	n and working of air break circuit breake	er with a	(03)
2B.	Write a technical note EHV transmission lines.	on the auto-reclosure scheme employed	l for the	(03)
2C.	With a connection dia injection method of syn	gram & waveform, explain the parallel thetic testing of circuit breaker.	current	(04)
3A.	Illustrate how discrimin protective relay are ach	ation between fuses & b/n fuse and over nieved.	current	(03)
3B.	Explain all the essentia	al qualities of protective relays		(04)
3C.	With a connection diagr star delta transformer	am, explain the Merz-price protection sch	neme for	(03)

- 4B. The generator is protected with Merz-price differential relay. Its ratings are 11kV, 5 MVA. The percentage of winding protected against ground fault is 80%. The relay setting is such that it trips for 20% of full load current. Calculate the resistance to be added in neutral to ground connection and what is the minimum value of earthing resistance to protect 90% of the winding.
- 4C. With the help of a relevant diagram and suitable illustrations, explain the protection scheme for a ring main system using definite time overcurrent relavs.
- **5A.** Obtain the 3 Zone settings for (i) impedance relay (ii) reactance relay and (iii) mho relay with a characteristic angle of 20° from the following data: C.T:1000/1 amp P.T: 220 kV/110 volts. Primary impedances of first, second and third line are $(2+j6) \Omega$, $(2.5+j5) \Omega$ and $(3.5+j7) \Omega$ respectively Zone #01 is designed to cover 75% of the first line. Zone #02 covers first line and extends up to 50% of the second line. Zone #03 covers both first and second line and extends up to 25% of the third line. **(04)**
- **5B.** What is the effect of single phasing operation of a 3 phase Induction motor on its performance? With the help of a neat connection diagram, explain the working of single phase preventer used to protect induction motor against single phasing
- **5C.** Describe the working principle of static relay with its block diagram, List out its limitations (03)

(03)

(04)

(03)