

Question Paper

Exam Date & Time: 30-Nov-2019 (09:30 AM - 12:30 PM)



MANIPAL ACADEMY OF HIGHER EDUCATION

INTERNATIONAL CENTRE FOR APPLIED SCIENCES
END SEMESTER THEORY EXAMINATION NOVEMBER/DECEMBER 2019

II SEMESTER B.Sc.(Applied sciences) in engg.

Elements Of Electrical and Electronics Engg. [IEE 121]

Marks: 100

Duration: 180 mins.

Answer 5 out of 8 questions.

- 1) Using network reduction techniques, for the circuit shown in figure 1A, determine the power supplied by the 6V source. (10)

A)

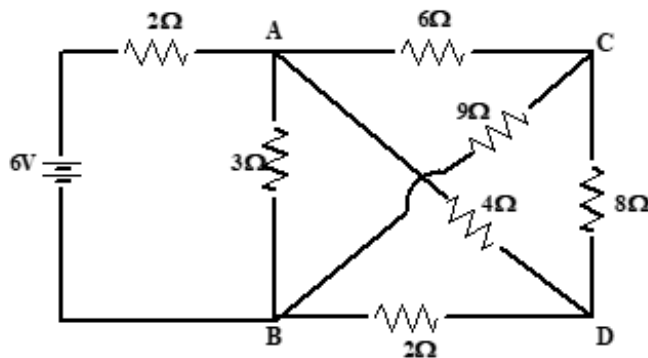


Figure 1

- B) For the circuit shown in the figure 1B, determine the power dissipated by 10 Ω resistor. (Use Mesh Analysis) (10)

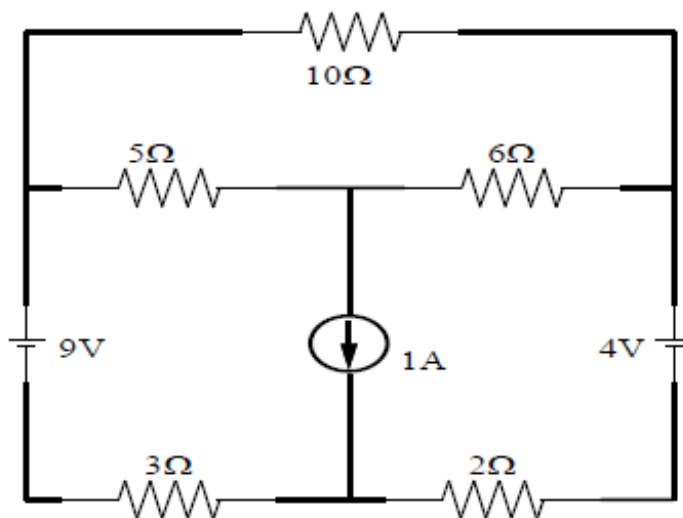


Figure 1B

- 2) For the circuit shown in figure 2A, use Node Voltage Analysis to calculate the power dissipated by the 10 Ω resistor. (13)

A)

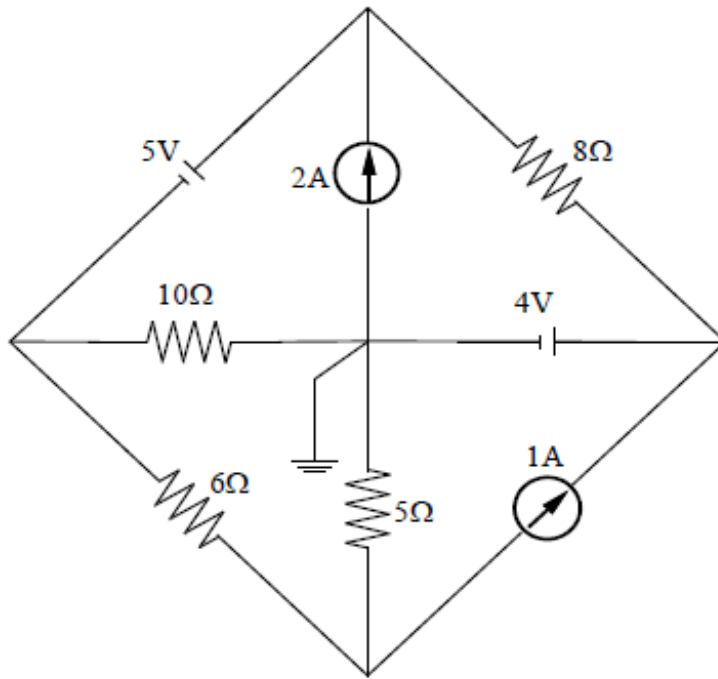


Figure 2A

B) Prove that for a R-L load connected to single phase AC supply, the active power dissipated is $V \cdot I \cdot \cos \theta$ where θ is the impedance angle. (7)

- 3) In a series parallel circuit the two parallel branches Z_a & Z_b are in series with Z_c as shown in Figure 3A. The impedances are $Z_a = (5+j20) \Omega$ and $Z_c = (5+j5) \Omega$. When 220V AC supply is applied to the circuit, the total power input is 3.25kW and current is 20A. (Assume that the net power factor is lagging in nature.) (12)
- A) Find (i) Impedance Z_b (ii) Current through Z_b

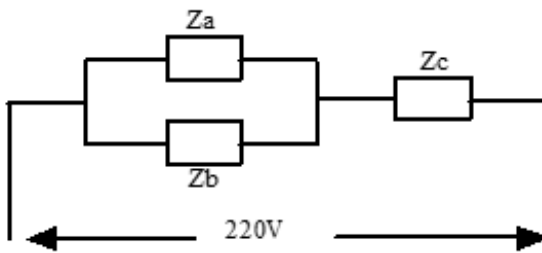


Figure 3A

B) The following loads are connected in parallel, across a single phase 110V, 50 Hz supply. (8)

- 400 W, 0.8 p.f lagging
- 540 VAR, 0.45 p.f. lagging
- 100 VA, UPF

Draw the equivalent power triangle, and hence determine the value of capacitance required to improve the power factor to 0.95 lagging.

- 4) A 3 phase, 400 V, 50 Hz, RYB, 3 wire supply feeds an unbalanced Y-connected load. The branch impedances of the loads are: $Z_R = (4 + j3) \Omega$, (13)

A)

$Z_Y = (6 + j8) \Omega$, $Z_B = (5 + j12) \Omega$. Using Mesh Analysis, find the line currents, the neutral displacement voltage and the readings of the 2 watt-meters connected to measure the 3 phase power with the current coils of the same inserted in the R and Y lines respectively. Sketch the Phasor diagram representing load voltages and currents.

- B) A 3 phase, 415 V, 50 Hz, RYB system supplies to three equal impedances of values $(12 + j5) \Omega$ each connected in delta. Determine the line and phase currents, total active power and the readings of the 2 watt-meters connected to measure the 3 phase power. (7)
- 5) With a neat block diagram and relevant equations, explain the working of a single phase transformer. Also list the various losses associated with a transformer. (10)
- A)
- B) Plot and briefly explain the effect of temperature variation on the I-V characteristics of a Silicon diode. Mark all salient points on the plot. Hence, derive the expression for dynamic resistance of a diode. (10)
- 6) **Starting from the fundamentals**, for a Half Wave rectifier, derive the expressions for the following (14)
- A)
- Rectification efficiency
 - Ripple factor
- Explain, with waveforms, how a capacitor filter reduces the ripple in a half wave rectifier output.
- B) In a FWR with a capacitor filter, the load current from the circuit operating from 230V, 50Hz supply is 10 mA. Estimate the value of capacitor required to keep the ripple factor to less than 1%. (6)
- 7) In a Full wave bridge rectifier, the transformer secondary voltage is $100 \sin \omega t$. The forward resistance of each diode is 25Ω and load resistance is 950Ω . Calculate (10)
- A)
- a) Dc output voltage
 - b) Ripple Factor
 - c) Rectification Efficiency
 - d) PIV across non conducting diode
 - e) Percentage regulation
 - f) Peak Load Current
- B) Sketch and briefly explain the common - emitter output characteristics. Define α_{dc} and β_{dc} for a transistor. Derive the relationship between α_{dc} and β_{dc} . Hence Calculate the values of I_C , I_E and β_{dc} for a transistor with $\alpha_{dc} = 0.98$ and $I_B = 120 \mu A$. (10)
- 8) With a neat circuit diagram, explain the working of a RC coupled amplifier. (10)
- A)
- B) Draw the block diagram of digital communication system and explain the function of each block. (10)

-----End-----