

Question Paper

Exam Date & Time: 14-Nov-2019 (02:00 PM - 05:00 PM)



MANIPAL ACADEMY OF HIGHER EDUCATION

INTERNATIONAL CENTRE FOR APPLIED SCIENCES
END SEMESTER THEORY EXAMINATIONS
NOVEMBER 2019
III SEMESTER B.sc. (Applied Sciences) in Engg.
ANALOG ELECTRONIC CIRCUITS [IEC 231]

Marks: 100

Duration: 180 mins.

Answer 5 out of 8 questions.

Missing data may be suitably assumed.

- 1) Draw and explain the circuit diagram of common base configuration using NPN transistor. Plot the input and output characteristics. Indicate cut-off, saturation and active regions. (5)
- A)
- B) The dc common base current gain for a certain transistor is, $\alpha_{dc} = 0.998$. Determine the emitter current I_E if the base current is $I_B = 40 \mu A$. Assume that the reverse saturation current, $I_{CBO} = 2 \mu A$. Also determine I_{CEO} . (5)
- C) Draw the small signal equivalent of the CE amplifier shown in fig. Q1C. Obtain expressions for g_m , r_e and output resistance of the amplifier from the model. (5)


 


Fig. Q1C

- D) For the transistor (Silicon) circuit shown in fig. Q1D, $R_B = 100 K\Omega$, $R_L = 820 \Omega$ and $V_{CC} = 10V$. Assume $V_{BE, sat} = 0.8V$ and $V_{CE, sat} = 0.2V$. Find the minimum base and collector current required in order to keep the transistor in saturation. Neglect I_{CBO} . Explain briefly the working of the circuit and draw the output waveform. (5)

 


 


Fig. Q1D

- 2) Determine I_B , I_C , I_E , V_{CE} , V_B , V_C and V_E for the voltage divider configuration shown in Fig Q2A given that $\beta=80$. Assume $V_{BE}=0.7V$. What is the region of operation? Neglect I_{CO} . (10)
- A)

 

FigQ2A

- B) Draw the circuit diagram of RC coupled amplifier with feedback using NPN transistor. (5)
Mention the function of each component. Explain the working at low, medium and high frequencies.
- C) Plot the frequency response of RC coupled amplifier with and without feedback. (5)
Indicate the salient features on the plot. In a 3-stage RC coupled amplifier, if the individual stage voltage gains are: $A_1=50dB$, $A_2=0dB$ and $A_3=10dB$ respectively, find the output voltage at each stage and overall gain in decibels if the input voltage applied is $V_i=10\sin(2\pi ft)$ millivolts.

- 3) (5)
- A)

For the circuit in **Fig. Q3A**, $\mu_n C_{ox} = 100 \mu A/V^2$ and $V_{TH} = 0.4V$. Calculate

- Drain current.
- If the gate voltage increases by 20 mV, what is the change in the drain voltage?
- What choice of R_D places the transistor at the edge of the triode region with value of I_D as in part i)?
- Determine the value of W/L that places M_1 at the edge of saturation with V_{GS} as in part i).

 


Fig Q3A

- B) Calculate the maximum allowable gate voltage in **Fig. Q3B**, if M_1 must remain saturated. Assume $\mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$ and $V_{TH} = 0.4\text{V}$ (5)

 


Fig Q3B

- C) (5)

If $\lambda = 0.1 / \text{V}$, $\mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$, $V_{TH} = 0.4\text{V}$ and $W/L = 10/0.18$, construct the small-signal model of the circuit shown in **Fig. Q3C**. Compute V_{DS} , g_m and r_o


 


Fig Q3C

- D) An NMOS device with $\lambda = 0.1/V$ must provide a gain of 25 with $V_{DS} = 1$ V. Determine the required value of W/L , if $I_D = 1$ mA and $\mu_n C_{ox} = 100 \mu A/V^2$ (5)

- 4) Design a circuit of **Fig. Q4A** for a drain current of 1 mA. If $W/L = 10/0.18$, $\mu_n C_{ox} = 100 \mu A/V^2$, $V_{TH} = 0.4$ V. Compute R_1 and R_2 such that the input impedance is at least 50 k Ω (5)

 

FigQ4A

- B) If $W/L = 20/0.18$, $\mu_p C_{ox} = 200 \mu A/V^2$ and $\lambda = 0$, determine V_{GS} , V_{DS} and I_D for the circuit shown in **Fig. Q4B**. Draw the small signal model. (5)

 


Fig Q4B

- C) (5)

The CS stage of **Fig. Q4C** must provide a voltage gain of 10 with a bias current of 1 mA. Assume $\lambda_1 = 0.2/V$, and $\lambda_2 = 0.25/V$, $\mu_n C_{ox} = 100 \mu A/V^2$, $\mu_p C_{ox} = 50 \mu A/V^2$, $V_{TH} = 0.4$ V.

(a) Compute the required value of $(W/L)_1$.

(b) If $(W/L)_2 = 10/0.18$, calculate the required value of V_b .

 


Fig Q4C

- D) In the circuit of **Fig. Q4D**, M_1 and M_2 have lengths equal to $0.2 \mu m$, $\mu_n C_{ox} = 100 \mu A/V^2$ (5)
 $V_{TH} = 0.4$ V and $\lambda = 0.2/V$. Determine W_1 and W_2 such that $I_{D1} = 2I_{D2} = 2$ mA. Assume $V_{DD} = 1.8$ V.

$V_{TH} = 0.4V$, and $k = 1/V$. Determine W_1 and W_2 such that $I_X = 2I_Y = 2\text{ mA}$. Assume $V_{DS1} = V_{DS2} = V_B = 1V$. What is the output resistance of each current source?

 


Fig Q4D

- 5) State Barkhausen criteria for sustained oscillations. Draw the circuit diagram of Hartley oscillator and explain its working. Write the expression for frequency of oscillations (5)
 - A) With the help of a circuit diagram, explain the working of transformer coupled Class B push pull power amplifier. Derive an expression for the maximum power efficiency. Mention one drawback of this amplifier. (5)
 - B) With the help of a block diagram, explain positive feedback. Derive an expression for gain in a positive feedback amplifier. Mention the application of positive feedback. (5)
 - C) State and explain Millers theorem with an illustration. Explain any one application of this theorem with necessary circuit (5)
- 6) Draw the circuit diagram of High Frequency Model of MOSFET and explain. Write the expressions for the cutoff frequencies on the input and output side of the amplifier. (5)
 - A) In an RC phase shift oscillator using FET, the value of resistors and capacitors in the feedback circuit are $R = 150\text{ K}\Omega$ and $C = 0.25\text{ Nano Farads}$. Determine the frequency of oscillation. If the value of $R_D = 1\text{ k}\Omega$ and $g_m = 2500\text{ millimhos}$, find the gain of the amplifier. (5)
 - B) With suitable diagrams, explain how power amplifiers are classified based on the operating point. (5)
 - C) Determine the voltage gain, input and output impedance with feedback for voltage Series feedback having $A = -100$, $R_i = 10\text{ k}\Omega$ and $R_o = 20\text{ k}\Omega$ for feedback of i) $\beta = -0.1$ ii) $\beta = -0.5$ (5)
- 7) Draw the block schematic of i) Voltage shunt ii) Current series feedback amplifiers. What is the effect of series and shunt feedback on the input and output resistance of an amplifier? (5)
 - A) Draw the circuit diagram of a crystal oscillator and explain the working. Mention any two advantages of Crystal oscillators. (5)
 - B) Explain the construction, working and characteristics of MOSFET. Sketch output and transfer characteristics. (5)
 - C) With necessary current equation explain Triode and Saturation region in MOSFET. Explain how current varies when width, length is varied with necessary plot. (5)
- 8) Explain the following: (20)
 - i) Early effect in BJT
 - ii) Channel length modulation in MOSFET

iii) Advantages and disadvantages of Positive and Negative feedback

iv) Piezoelectric effect in crystals
(5X4=20)

-----End-----