

Question Paper

Exam Date & Time: 28-Dec-2019 (09:30 AM - 12:30 PM)



MANIPAL ACADEMY OF HIGHER EDUCATION

INTERNATIONAL CENTRE FOR APPLIED SCIENCES
END SEMESTER THEORY EXAMINATIONS NOVEMBER 2019
III SEMESTER B.sc. (Applied Sciences) in Engg.
SWITCHING CIRCUITS AND LOGIC DESIGN [ICS 232]

Marks: 100

Duration: 180 mins.

Answer 5 out of 8 questions.

- 1) Simplify the following expressions using algebraic manipulation. (12)
- A) i) $F(A, B, C, D) = \sum m(3, 7, 9, 12, 13, 14, 15)$
ii) $f(a, b, c, d, e) = a'c'e' + a'c'd' + a'de + ab'c'e$
iii) $F(A, B, C, D) = (A' + C' + D')(B' + C' + D)(A + B' + C')$
iv) $F(A, B, C) = \prod M(0, 1, 5)$
(4X3=12)
- B) i) Derive the minimum cost SOP expression for the following function using K-map and implement using only NOR gates. Write all prime implicants and Essential prime implicants. (8)
 $F(a, b, c, d) = \sum m(0, 1, 2, 5, 7, 8, 10, 12, 14, 15)$
ii) Find the minimum cost SOP and POS expression for the following function using K-map.
 $F(w, x, y, z) = \sum m(0, 1, 3, 4, 7, 11, 13, 15) + d(9, 12, 14)$
(5+3=8)
- 2) A circuit with two outputs has to implement the following functions (10)
- A) $f(x_1, x_2, x_3, x_4) = \sum m(0, 2, 4, 6, 7, 9) + d(10, 11)$
 $g(x_1, x_2, x_3, x_4) = \sum m(2, 4, 9, 10, 15) + d(0, 13, 14)$
Implement it and compare its cost with combined costs of two SOP implementations that implement f and g separately. Assume that the input variables are available in both complemented and complemented forms.
- B) i) Perform 2's complement addition for the following : (10)
a) $(+5) + (+2)$ b) $(-5) + (+2)$ c) $(+5) + (-2)$ d) $(-5) + (-2)$
ii) Design and write the behavioral Verilog code for 4-bit adder/subtractor unit.
(4+6=10)
- 3) i) Design a single-digit BCD adder. (10)
- A) ii) Design and write Verilog code to convert BCD to excess-3 code using a four-bit adder.
(3+7=10)
- B) Design a BCD to 2421 code converter using 8:1 MUXes. Write Verilog code to implement this. (10)

- 4) i) Write behavioral Verilog code to convert an N bit binary number into equivalent gray code. Use for loop. (9)
- A) ii) write the truth table and circuit diagram for 4-to-1 Multiplexer.
iii) write the truth table and circuit diagram for three-input majority function using 4-to-1 multiplexer.
(3X3=9)
- B) i) Write the truth table for 3-to-8 decoder and design 3-to-8 decoder using two 2-to-4 decoders. (11)
ii) Design and Write Verilog code to implement $f(A, B, C) = \sum m(0, 2, 3, 4, 5, 7)$ using 3 to 8 binary decoder and an OR gate. Use case statement.
(5+6=11)
- 5) i) Write the truth table for 4-to-2 priority encoder with active high enable and active low output. (11)
- A) ii) write Verilog code for 8:1 multiplexer using two 2-to-4 decoders and external gates. Implement the 2-to-4 decoder module using for loop.
(3+8=11)
- B) i) Design a 4-bit comparator circuit using full adders. The inputs to the comparator are $A=a_3a_2a_1a_0$ and $B=b_3b_2b_1b_0$. The output is $AeqB$, which is high when $A=b$ and low when $A \neq B$. (9)
ii) A combinational circuit building block receives an 8 bit input A_7-0 , and produces a 3 bit output Y_2-0 and one 1 bit output Z . Y indicates the most significant line number of the input that is TRUE. Z should be TRUE if there are one or more TRUE bits on the input. What is this building block? Draw the block diagram and the truth table.
(3+6=9)
- 6) i) Draw the logic diagram of D flip flop. Write its characteristic table, characteristic equation, and excitation table. (12)
- A) ii) With neat diagram explain the working of D type positive edge triggered Flip-Flop.
(6+6=12)
- B) The logic diagram of a sequential circuit is given in Figure Q6.B. Derive the state table and state diagram of the circuit. (8)

 


Figure Q6.B

- 7) Design a counter with the following repeated nonbinary sequence: 0, 1, 2, 3, 4, 5, 6. Use JK flip-flops. Treat the unused states as a don't-care (10)
- A)

conditions.

- B) i. Design a 4-bit bi-directional shift register for the following operations using (10)
D flip flops and MUXs.

Shift	Load	Operation
0	0	No change
0	1	Load parallel data
1	d	Shift right

ii. Design and write the Verilog code for 4-bit asynchronous up counter using T Flip-Flop.

(4+6=10)

- 8) Explain the following with a neat diagram for each. (12)

- A) i) NMOS realization of a NAND gate.
ii) NMOS realization of a NOR gate.
iii) CMOS realization of a NAND gate.
iv) CMOS realization of a NOR gate.

(4X3=12)

- B) i) Discuss PLA with a neat logic diagram. (8)
ii) Define a tri-state buffer. Write its truth table.

(6+2=8)

-----End-----