



INTERNATIONAL CENTRE FOR APPLIED SCIENCES

MAHE, MANIPAL

B.Sc. (Applied Sciences) in Engg.

End – Semester Theory Examinations – Nov./ Dec. 2020

III SEMESTER - ANALOG ELECTRONIC CIRCUITS (IEC 231)

(Branch: CS, E&E and Mechatronics)

Time: 3 Hours

Date: 19 November 2020

Max. Marks: 50

- ✓ Answer ALL the questions.
- ✓ Missing data, if any, may be suitably assumed

1. For the circuit shown in Fig.Q1 below determine I_{BQ} , I_{CQ} , V_{CEQ} , V_C , V_E , V_B . Draw the load line.

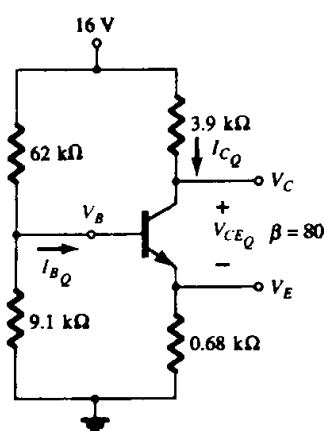


Fig.Q1

10M

- 2A. Draw the circuit diagram of RC coupled amplifier without feedback using NPN transistor. Mention the function of each component. Explain the working at low, medium and high frequencies. 5M
- 2B. Define α_{dc} and β_{dc} of a transistor. Write the expressions for α_{dc} and β_{dc} . In a transistor, 99% of the carriers injected into the base cross over to the collector region. If collector current is 4mA and collector leakage current is 6 μ A, calculate emitter and base currents. 5M
- 3A. For the circuit in Fig. Q3A, $\mu_{nCox} = 200 \mu\text{A/V}^2$ and $V_{TH} = 0.5V$, $I_d = 0.1\text{mA}$ and $\lambda = 0$. Calculate:

- i) Small signal Voltage gain of the CS stage.
- ii) Verify that M_1 operates in saturation
- iii) Draw small signal model for Fig.Q3A

5M

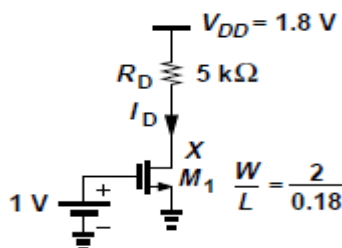


Fig. Q3A

- 3B. State and prove Miller's theorem. For the circuit shown in **Fig. Q3B**, draw the small signal model. Using Miller's theorem, determine Miller's input and output impedances.

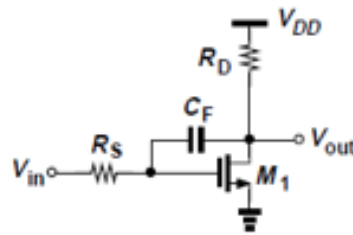


Fig.Q3B

5M

- 4A. Draw the circuit diagram of a Hartley oscillator. In a Hartley oscillator $L_1=20\ \mu\text{H}$, $L_2=2\ \text{mH}$ and C is variable. Find the range of C for frequency range 1MHz to 2.5 MHz Neglect the mutual inductance. **5M**
- 4B. Define class A, class B and class AB power amplifiers. With the help of output characteristics and the dc load line, illustrate their operation. What are the theoretical efficiencies of a series-fed class A and class B power amplifiers? **5M**
5. Explain the Following:
- ii) Second order effects in MOSFET
 - ii) Cross over Distortion
 - iii) Emitter follower
 - iv) MOS trans conductance
- 2.5X4=10M**
