



INTERNATIONAL CENTRE FOR APPLIED SCIENCES
MAHE, MANIPAL
B.Sc. (Applied Sciences) in Engg.
End – Semester Theory Examinations – Nov./ Dec. 2020
III SEMESTER - NETWORK ANALYSIS (IEE 231)
(Branch: E&E)

Time: 3 Hours

Date: 25 November 2020

Max. Marks: 50

- ✓ Answer ALL the questions.
- ✓ Missing data, if any, may be suitably assumed

1A Apply Mesh current analysis and find the currents I_1 and I_2 for the network shown in Fig.1A.

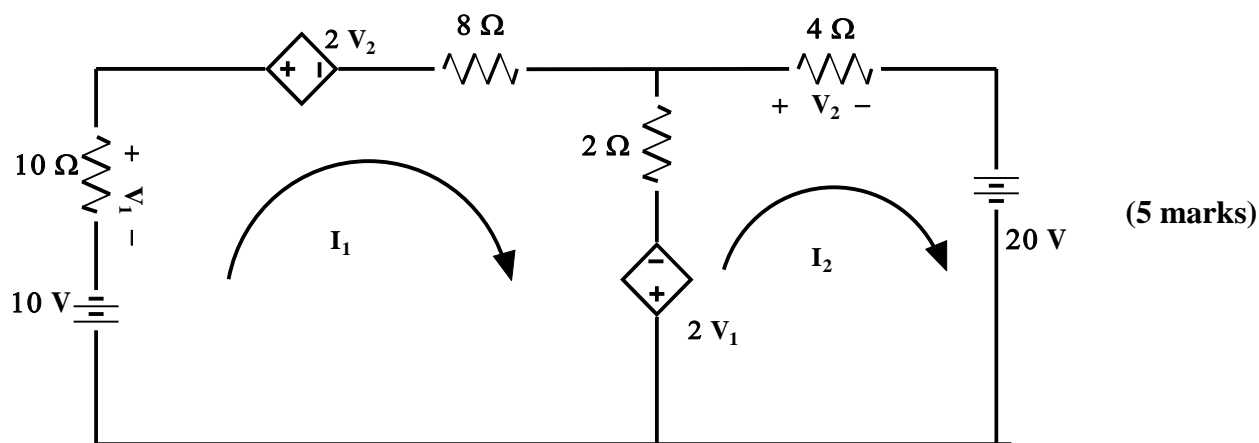


Fig. 1A

1B Apply Super Mesh analysis and find the currents I_1 , I_2 and I_3 for the network shown in Fig.1B.


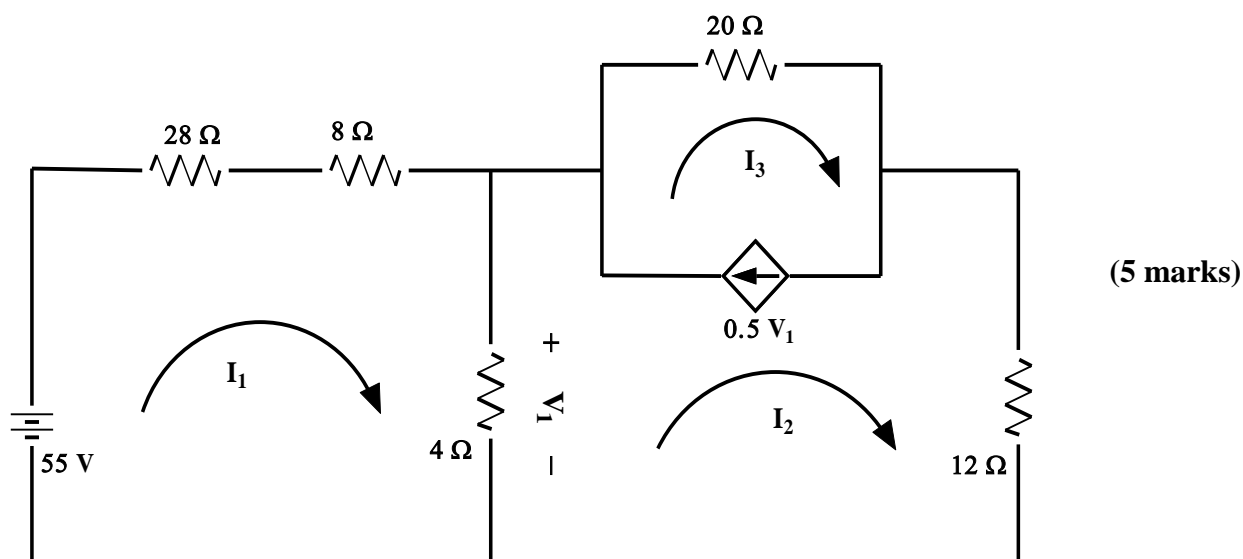


Fig. 1B

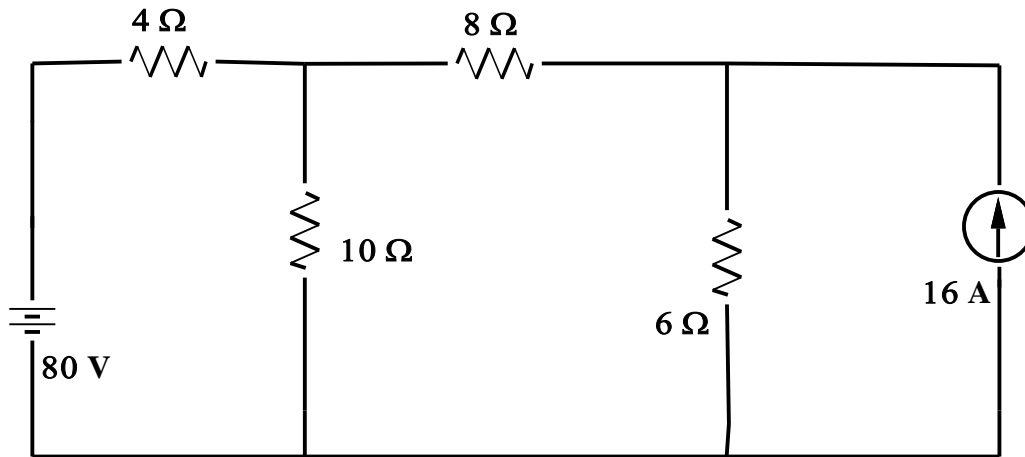
- 2A** Apply Superposition theorem and find the current through 8Ω resistor for the circuit shown in Fig.2A.



(5 marks)

Fig. 2A

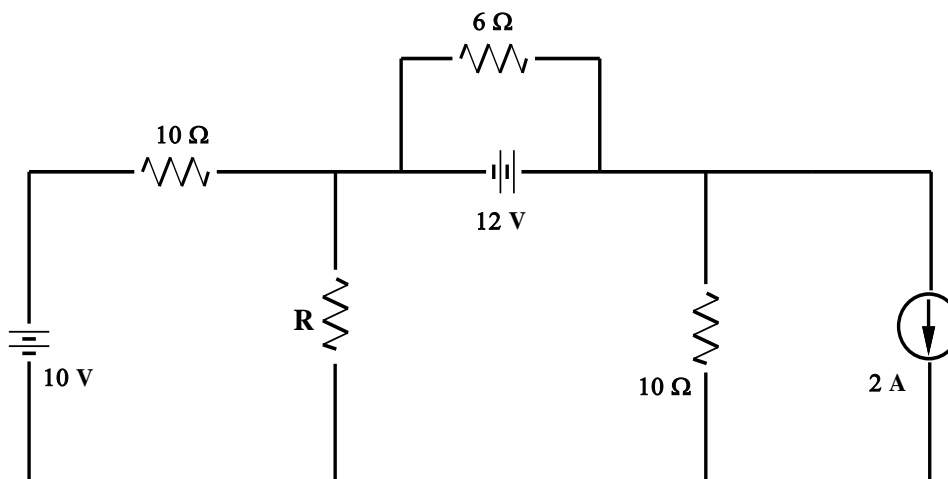
- 2B** Find the maximum power transferred to the resistor 'R' for the circuit shown in Fig.2B.



(5 marks)

Fig. 2B

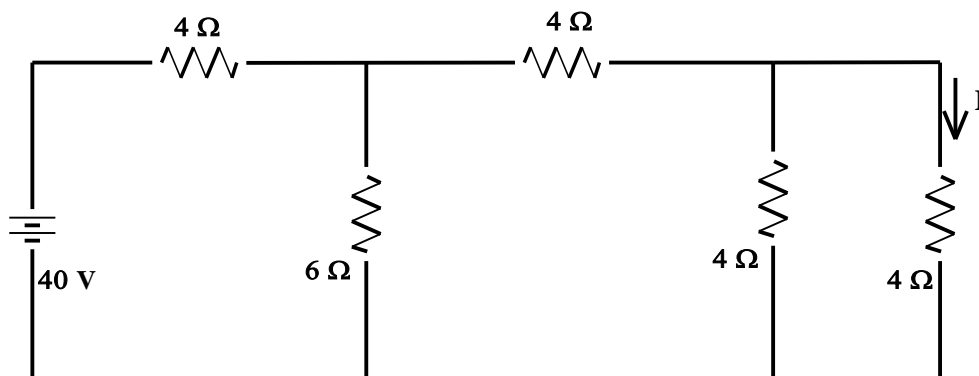- 3A** State Reciprocity theorem and prove it for the linear, bilateral circuit shown in Fig.3A.



(5 marks)

Fig. 3A

- 3B** For the network in Fig.3B steady state is reached with the switch closed. The switch is opened at $t = 0$. Find the expression for current inductor current $i_L(t)$ and inductor voltage $v_L(t)$ using time domain analysis.

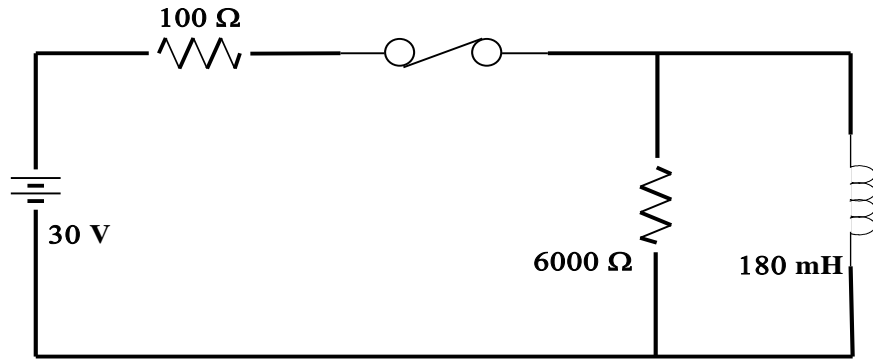


Fig. 3B

(5 marks)

- 4A** In the network shown in Fig. 4A switch is closed at $t = 0$. Find the expression for current $i(t)$ for $t > 0$ using time domain analysis.

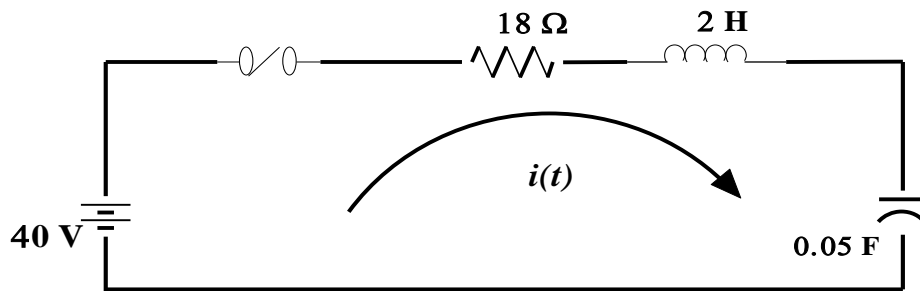


Fig. 4A

(5 marks)

- 4B** Apply Laplace Transform to find $i(t)$ and $\frac{d}{dt}i(0^+)$ for the network shown in Fig.4B. Assume the circuit is initially at rest and switch closes at $t = 0$.


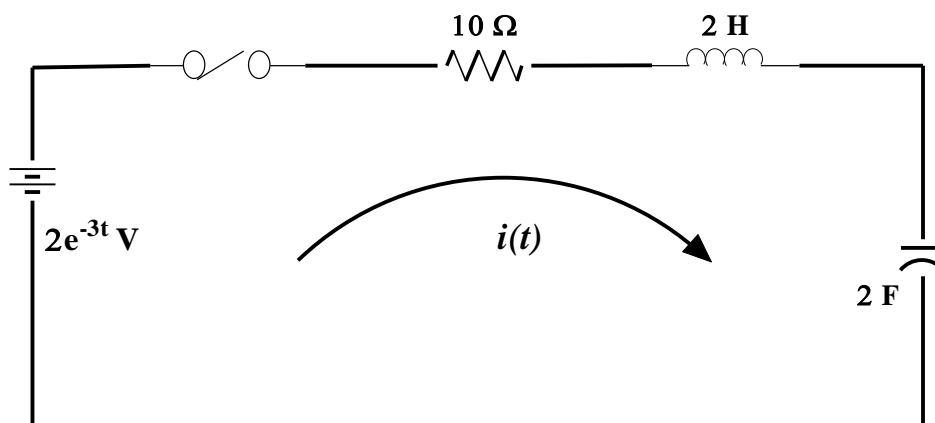


Fig. 4B

(5 marks)

5A In the network shown in Fig. 5A switch is closed at $t = 0$. Find $i_2(t)$.

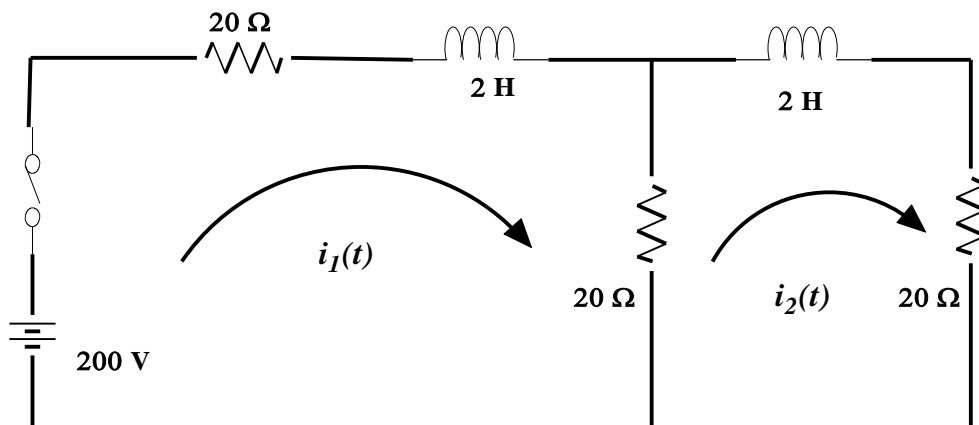
Network is un-energized before switch is closed.



(5 marks)

Fig. 5A

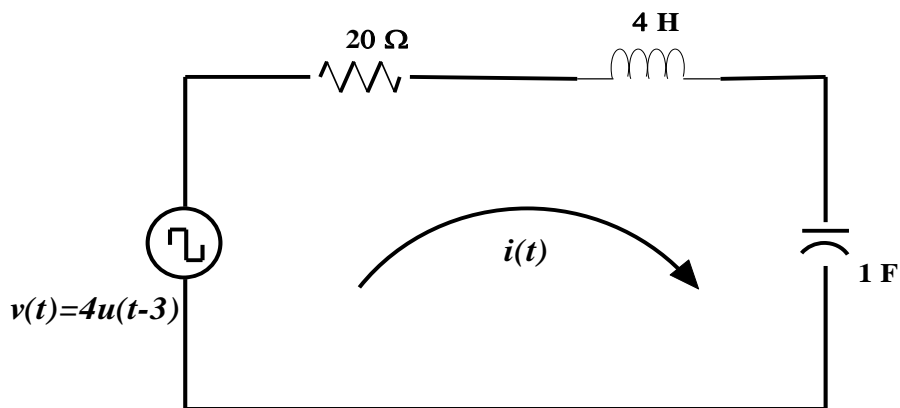5B Apply Laplace Transform to find the current $i(t)$ for the circuit shown in Fig. 5B.



(5 marks)

Fig. 5B
