

## THIRD SEMESTER BTECH. (E & C) DEGREE END SEMESTER EXAMINATION MARCH 2021 SUBJECT: NETWORK ANALYSIS (ECE - 2154)

## **TIME: 3 HOURS**

MAX. MARKS: 50

## Instructions to candidates

- Answer **ALL** questions.
- Missing data may be suitably assumed.
- Do not use Laplace Transforms unless specified.
- 1A. For the circuit shown in Fig. Q1A, find the Thevenin's equivalent network to the left of terminals A and B.
- 1B. In the network shown in Fig. Q1B, the power loss in the load resistor  $R_L$  is 18W. Find the magnitude of  $V_0$  and the current supplied by it.
- 1C. For the network shown in Fig. Q1C, find the voltage  $V_x$  using Superposition Theorem.

(4+3+3)

- 2A. In the circuit shown in Fig. Q2A, determine  $V_c$  at t = 0.2sec.
- 2B. In the circuit shown in Fig. Q2B, determine the expression for  $i_1(t)$  for t > 0.
- 2C. For the circuit shown in Fig. Q2C, find the voltage  $V_0$  at t =1.3msec.

(4+3+3)

- 3A. A square wave with  $T_1 = 0.1$  sec,  $T_2 = 0.2$  sec as shown in Fig.Q3A is applied to an RC low pass circuit. If the time constant of the circuit is 0.1 sec, calculate the output voltages and draw the output waveform.
- 3B. A limited ramp from a generator rises linearly to Vs volts in a time period  $Ts = 0.1 \mu s$  and remains constant for 2  $\mu s$ . This signal is applied to a differentiating circuit whose time constant is 0.01  $\mu s$ . The resultant pulse at the output of the differentiator has a maximum value of 15 V. What is the peak amplitude of the ramp at the output of the generator?
- 3C. A positive step input of magnitude V is applied to high-pass RC circuit at t = 0. Derive the expression for the output voltage and calculate the fall time. Show that the fall time is  $\frac{0.35}{f_1}$  where  $f_1$  is the lower cut-off frequency.

(4+3+3)

- 4A. Determine the voltage  $v_x$  in the circuit shown in Fig. Q4A using Laplace Transform method.
- 4B. Find the current  $i_2$  in the circuit shown in Fig. Q4B at t = 0.15sec.
- 4C. For the circuit shown in Fig. Q4C, determine the expression for i(t) using Laplace transform. (4+3+3)
- 5A. Find ABCD parameters for the network shown in Fig. Q5A.

ECE – 2154

- 5B. Find Hybrid parameters for the network shown in Fig. Q5B.
- 5C. Derive the expressions for y parameters in terms of z parameters.

(4+3+3)









