

Exam Date & Time: 10-Mar-2021 (09:00 AM - 12:00 PM)



THIRD SEMESTER B.TECH (ELECTRONICS AND INSTRUMENTATION ENGG.)
 END SEMESTER EXAMINATIONS, MARCH 2021
DIGITAL ELECTRONICS CIRCUITS [ICE 2152]

Marks: 50

Duration: 180 mins.

A

Answer all the questions.

Instructions to Candidates: Missing data may be suitably assumed

- 1) Define any four performance matrices of logic families. (2)
 - A)
 - B) How is an error detecting code different from an error correcting code? Encode data bits 0111 into 7 bit even parity hamming code. Decode the received hamming code message '0011011' assuming that single error has occurred. (3)
 - C) Using QM method, obtain the minimal expression for the function, $f = \prod M(1, 4, 5, 11, 12, 14).d(6, 7, 15)$. Implement it in universal logic. (5)

- 2) Design a circuit to detect the numbers 0, 1, 4, 6, 7 and 8 in a 4 bit XS - 3 code input. Implement it using universal logic. (4)
 - A)
 - B) With neat circuit diagram, design a 2-bit magnitude comparator. (3)
 - C) Design a half - subtractor using NOR logic. (3)

- 3) Realize the logic expression, $f = \sum m(2, 4, 5, 7, 9, 10, 14, 15)$ using (i) 8:1 MUX, (ii) 4:1 MUX. (4)
 - A)
 - B) Design a basic 10 – line to 4 – line encoder circuit. (3)
 - C) With suitable logic diagram, explain the function of Twisted Ring Counter. Also draw its timing diagram. (3)

- 4) The input signals shown in Fig.Q4A are applied to an S-R flip flop with active - high PRESET and CLEAR. (2) Draw the output waveform for a positive and negative edge triggered S-R flip-flop. Assume that the present state of flip flop is '0'.
 - A)

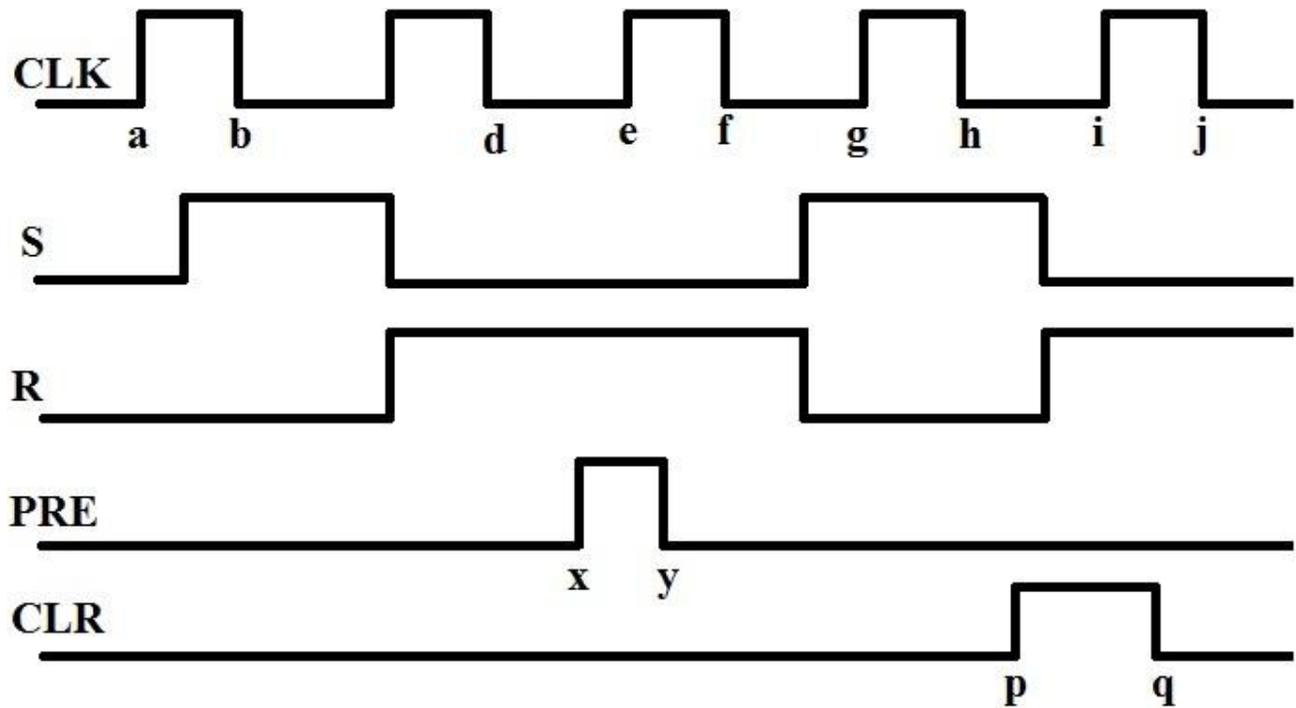


Fig.Q4A

- B) Design a cyclic counter using T flip flop that counts 2, 6, 7, 11, 12, 13, 2, 6 ... and unused states of the counter change to 7 at the next clock pulse. (5)

- C) An asynchronous sequential circuit is described by the excitation and output functions

$$Y_1 = x_1x_2 + x_1y'_2 + x'_2y_1$$

$$Y_2 = x_2 + x_1y'_1y_2 + x'_1y_1$$

$$z = x_2 + y_1$$

(3)

Derive the transition table and output map. Draw the logic diagram of the circuit.

- 5) A clocked sequential circuit with single input x and single output z produces an output $z = 1$ whenever the input x completes the sequence 1101 with overlapping allowed. Obtain the state diagram and design the circuit with D flip flops for a Mealy type sequence detector. (5)

A)

- B) Draw an ASM chart and state table for a 2-bit up-down counter having mode control input, $M = 1$: Up counting

$M = 0$: Down counting

(3)

The circuit should generate an output '1' whenever the count becomes either minimum or maximum.

- C) Describe the critical race condition in asynchronous sequential circuit with suitable example. (2)

-----End-----