

# Question Paper

Exam Date & Time: 05-Mar-2021 (09:00 AM - 12:00 PM)



**MANIPAL INSTITUTE OF TECHNOLOGY**  
MANIPAL  
(A constituent unit of MAHE, Manipal)

THIRD SEMESTER B.TECH( Electronics and Instrumentation) END SEMESTER EXAMINATIONS, MAR 2021

## ELECTRONIC MEASUREMENTS [ICE 2153]

Marks: 50

Duration: 180 mins.

A

Answer all the questions.

Instructions to Candidates:

Missing data may be suitably assumed

- 1) State any two errors that can occur during the measurement of resistance, (2)  
capacitance and inductance using bridges and suggest suitable remedy  
for the same.
- A)
- B) Using necessary equations and phasor diagram, prove that the number of (3)  
revolutions in a single phase induction type energy meter is proportional to  
the energy consumed.
- C) In the AC bridge shown in Fig.Q1C, under the balance conditions, obtain (3)  
the values of the suitable combination of components used for Z.

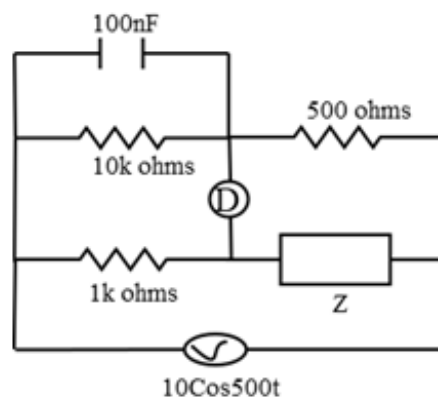


Fig. Q1C

- D) Derive the expression for the deflection in an electrostatic deflection (2)  
system of a CRO. Hence obtain the expression for magnetic deflection  
sensitivity.
- 2) Explain shortcomings of the passive matrix LCD display with suitable (4)  
example. State the measures used to overcome these shortcomings.
- A)
- B) Draw the block diagram of cathode ray tube and explain its functions. (3)
- C) Explain the working of DSO with block diagram and describe the various (3)  
modes of operation.

- 3) (4)

- A) What are the uses of Q-meter and explain the procedure of measuring quality factor of unknown components connected in series to Q-meter with necessary equations.
- B) 4-bit successive approximation technique is used to convert 11.2V to binary output with  $V_{ref}$  as 16 volts. Explain the conversion process with required steps and block diagram. (4)
- C) What is sampling? Draw different types of sampling circuits. (2)
- 4) Explain working of digital frequency meter along with operation of gated control flip-flop used for the same. (4)
- A)
- B) Explain the principle of working of a magnetic tape recorder. What are the basic components and their functions? (3)
- C) Explain different types of marking mechanism used in strip chart recorder. (3)
- 5) What is wave analyzer? Describe the construction and working of wave analyzers for audio-frequency and MHz ranges. (5)
- A)
- B) Distinguish principle of working of a spectrum analyzer and wave analyzer. (2)
- C) Draw the block diagram of a spectrum analyzer. How is the spectrum of a given signal displayed on spectrum analyzer? (3)

-----End-----