

|  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|
|  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|



# MANIPAL INSTITUTE OF TECHNOLOGY

MANIPAL

(A constituent unit of MAHE, Manipal)

## VII SEMESTER B.TECH (ELECTRICAL & ELECTRONICS ENGINEERING) ONLINE EXAMINATIONS, JANUARY - FEBRUARY 2021

### MODERN POWER CONVERTER [ELE-4010]

REVISED CREDIT SYSTEM

Time: 3 Hours

Date: 27 January 2021

Max. Marks: 50

#### Instructions to Candidates:

- ❖ Answer **ALL** the questions.
- ❖ Missing data may be suitably assumed.

- 
- 1A.** Design a boost converter with input voltage of 3V, output voltage is 5 V load current is 1Amp and Switching frequency 100kHz. Consider 40% peak current ripple and 80% efficiency. **(04)**
- 1B.** Design a buck converter for continuous inductor current with the following specification output voltage  $V_o = 18$  V load resistance  $10\Omega$ , output voltage ripple less than 0.5%. The input voltage is 48V and switching frequency  $f = 40$  kHz, Determine (a) duty ratio  $D$  (b) The value of inductor  $L$  and capacitor  $C$ . (c) The average value of  $I_L$ . The maximum and minimum value of inductor current. **(04)**
- 1C.** What are the problem of Hard switching? explain the possible solutions **(02)**
- 2A.** What kind of output rectifier and filter circuit is used in a fly back converter? With neat diagram and waveform explain the operation of fly-back converter. **(05)**
- 2B.** What are the assumptions are making for design and analysis of single switch forward converter used in SMPS? Mentions the benefits of two switch forward converters are used in SMPS. **(05)**
- 3A.** What are the different types of symmetrical converter? Why high frequency transformer used in Push pull converter. Derive an expression to estimate the output voltage in push pull converter. **(04)**
- 3B.** A Cuk converter has the following parameters:  $V_g = 10$  V,  $V_o = 24$  V,  $I_o = 1$  A,  $f_s = 100$  kHz. Determine the value of the energy storing capacitor ( $C_1$ ) such that the capacitor voltage ripple should be less than 3%. **(03)**
- 3C.** Explain the steps in the manipulation of small signal AC model of the buck boost converter in to canonical form. **(03)**
- 4A.** What is the need of resonant converter in switched mode power supply? Explain the operation of Parallel loaded resonant DC-DC converter using suitable circuit diagram and waveform, If witching frequency is greater than resonant frequency ( $\omega_s > \omega_0$ ). **(05)**

- 4B.** Zero current switch buck converter operates with input voltage of 18V, load current of 1Amp, and resonant frequency of 1 MHz load is  $10\Omega$ . Determine the following (a) resonant inductor and capacitor. (b) Peak switch current (c) peak voltage rating of the capacitor (d) the linear charging period of the inductor **(05)**
- 5A.** Discuss in detail the basic constraints for the design of a high frequency inductor when the core geometrical factor Kg method is employed for the design. **(04)**
- 5B.** A series resonant dc-dc converter operates in continuous conduction mode with  $\omega_s/\omega_0 = 1.3$ . The input voltage is 100V, the resonant Inductor and capacitance are  $L_r = 10\mu\text{H}$  and  $C_r = 2\mu\text{F}$ . The load resistance is  $20\Omega$ . Calculate the peak inductor current. **(04)**
- 5C.** What are the factors affecting the choice of zero voltage switching resonant converter in switched mode power supply. **(02)**