



# MANIPAL INSTITUTE OF TECHNOLOGY

MANIPAL  
(A constituent unit of MAHE, Manipal)

## SEVENTH SEMESTER B.TECH. (INSTRUMENTATION AND CONTROL ENGG.) END SEMESTER DEGREE EXAMINATIONS, JANUARY - 2021

**SUBJECT: VLSI DESIGN [ICE 4001 ]**

TIME: 3 HOURS

03-02-2021

MAX. MARKS: 50

**Instructions to candidates :** *Answer ALL questions and missing data may be suitably assumed.*

- 1A. Compare various VLSI technologies based on their speed to power performance.
- 1B. What are enhancement mode and depletion mode transistors? Explain differences based on their mechanism of operation.
- 1C. With neat diagrams explain the p-well process for CMOS fabrication. (2+3+5)
- 2A. What are the building blocks of an FPGA?
- 2B. Explain body effect.
- 2C. Obtain the pull-up to pull-down ratio for an nMOS inverter driven through four pass transistors. (2+3+5)
- 3A. Write a note on the limits of miniaturization.
- 3B. Design a 4:1 multiplexer in CMOS logic.
- 3C. Prove that the changeover between logic levels is symmetric for a CMOS Inverter. (2+4+4)
- 4A. How do the static and dynamic components of power dissipation contribute to scaling factor?
- 4B. Calculate the capacitance for Metal 1 ( $L = 16\lambda$ ,  $W = 3\lambda$ ) shown in fig Q4B. How will the capacitance be if the area of same material is i) polysilicon, ii) n-type diffusion.



Fig. Q 4B

- 4C. Draw a 2 Input XOR gate in CMOS logic and represent it in stick notation. (2+3+5)
- 5A. Differentiate between semicustom and full custom IC design.
- 5B. Model the relationship between built in junction potential and the applied voltage.
- 5C. With a neat diagram explain the configuration of Boundary Scan test. (2+4+4)