

INTERNATIONAL CENTRE FOR APPLIED SCIENCES MAHE, MANIPAL B.Sc. (Applied Sciences) in Engg. End – Semester Theory Examinations – May 2021 II SEMESTER: Elements of Electrical and Electronics [IEE 121] (BRANCH: E & E)

	Time: 3 Hours	Date: 20 May 2021	Max. Marks: 50	
	 ✓ Answer ALL Qu ✓ Missing data, if 	 ✓ Answer ALL Questions. ✓ Missing data, if any, may be suitably assume. 		
1A	Derive the expression fo capacitor in an AC cir instantaneous power.	instantaneous power and average pout. Plot the waveforms for indu	power dissipated by a pure actor voltage, current and	
1B	The voltage applied to a purely inductive coil of self-inductance $30mH$ is given by equation		ce $30mH$ is given by the	
	v(t) Find the equation of the r	$= 50 \sin(156t) + 100 \sin(470t) +$ esulting current wave.	25 sin(786 <i>t</i>)	
1C	Evaluate the expression v_1 diagram. Given $v_1 = 5 \sin v_1$	$= v_1 + v_2$ using the phasor method $u(\omega t + 60^0)$ and $v_2 = -20\cos(\omega t - 1)$	and draw the phasor – 45 ⁰)	
2A	Explain with the help of r the expression for the RM	ecessary diagrams the process of AC S value of AC sinusoidal voltage	voltage generation. Derive	
AD			, • , 1 • •,	

2B Determine the power factor, true power, reactive power and apparent power in the circuit shown in Fig.2B.





- 3A Derive the expression for ripple factor and Transformer utilization factor in full wave rectifier. Draw the circuit diagram and plot necessary waveforms. (3)
- **3B** For the circuit shown in Fig.3B, determine
 - a) DC output voltage
 - b) Rectification efficiency

Assume all the diodes are ideal.





3C A current 5A flows through a non-inductive resistance in series with choking coil when supplied at 250V, 50Hz. If the voltage across the resistance is 125V and across coil is 200V. Calculate (i) impedance, resistance and reactance of the coil, (ii) The power absorbed by the coil and (iii) The total power. Draw the phasor diagram.

(5)

(4)

(2)

- 4A Explain the working of a PN junction diode with the help of a neat diagram. Draw the VI characteristics of a PN junction diode. (3)
- **4B** A resistor and capacitor is in series with a variable inductor is connected to 200V, 50Hz supply. The maximum current is 0.314A by varying the inductance. The voltage across the capacitor is 300V. Find the value of R, L and C.
- 4C Draw the VI characteristics of Zener diode. Write down the differences between Zener breakdown and Avalanche breakdown. (3)

5A Find the equivalent resistance between the points A and B for the circuit shown in Fig.5A



5B Explain the working of PNP transistor. Draw and explain the input and output characteristics of BJT in Common Emitter configuration.



(5)