



MANIPAL INSTITUTE OF TECHNOLOGY

(A constituent unit of MAHE, Manipal 576104)

#### III SEM B. Tech (BME) DEGREE END SEMESTER EXAMINATIONS, MARCH-2021. SUBJECT: ANALOG ELECTRONICS (BME 2151) (REVISED CREDIT SYSTEM) Monday, 1<sup>St</sup> March, 2021; 0:00 A M to 12:00 NOON

Monday, 1<sup>st</sup> March, 2021; 9:00 A.M to 12:00 NOON

# **TIME: 3 HOURS**

MAX. MARKS: 50

### **Instructions to Candidates:**

## 1. Answer ALL questions

## 2. Missing data may be suitably assumed

1. (A) For the following circuit, graphically determine  $I_{DQ}$  and  $V_{GSQ}$ , and determine the voltages 5  $V_D$ , and  $V_S$ .



(B) Determine the lower cut-off frequency of the following amplifier circuit.



(C) Is it possible to relate  $\alpha_{dc}$  and  $\beta_{dc}$  of a BJT? Justify your answer.

3

2

- (i) The value of resistors "R<sub>2</sub>" required to produce distortion-free output
- (ii) Trickle current that eliminates the distortion
- (iii) Maximum a.c output power, and
- (iv) Minimum power rating of the transistors



- (B) For the emitter degenerative biasing circuit of a BJT, employing a voltage divider 3 network, prove that the stability factor is  $(1 + \beta) \frac{1 + \frac{R_B}{R_E}}{1 + \beta + \frac{R_B}{R_E}}$
- (C) With an appropriate example illustrate that a bipolar junction transistor can be used as an 2 amplifier.
- 3. (A) For an emitter-follower circuit employing NPN transistor in fixed bias configuration, 5 prove that:
  - (i)  $Zi = R_B \parallel \beta(\mathbf{r}_e + R_E)$
  - (ii)  $Z_o = r_e \parallel R_E$
  - (iii)  $A_V = 1$
  - (B) In an RC phase shift oscillator if  $C_1 = C_2 = C_3 = 200 \text{ pF}$ .

- 3
- (i) Choose resistors required to produce sustained oscillations of frequency 4KHz
- (ii) Select appropriate valued collector resistor ( $R_C$ ) if emitter resistor is 120  $\Omega$
- (C) What causes cross-over distortion in a Class–B power amplifier? How do you eliminate 2 such distortion? Explain.

4. (A) For the circuit shown below, choose value of  $R_D$  and  $R_S$  so as to establish a gain of 10 5 using a relatively high level of trans-conductance defined at  $V_{GSQ} = \frac{1}{4} V_P$ . Also test if the solution holds good or not?



- $(B) \quad \mbox{Considering the feedback, analyse the following circuit for:}$ 
  - (i) Voltage gain
  - (ii) Input resistance
  - (iii) Output resistance

Assume :  $h_{fe}$  = 50,  $h_{ie}$  = 1 K $\Omega$ , and  $h_{re}$  =  $h_{oe}$  = 0



3

(C) Identify the feedback topology and draw a labelled a.c equivalent circuit of the following 2 amplifier circuit.



- 5. (A) How does an UJT relaxation oscillator produces saw-tooth waveform, and how do you 5 determine the frequency of oscillations? Explain.
  - (B) Draw the circuit diagram of BJT current-series feedback amplifier, and find out its 3 de-sensitivity and input impedance.
  - (C) How does the negative feedback affect the input and output impedances in voltage-series 2 and current-shunt configurations?