



**THIRD SEMESTER BTECH. (E & C) DEGREE END SEMESTER EXAMINATION**  
**MARCH 2021**

**SUBJECT: DIGITAL SYSTEM DESIGN USING VERILOG (ECE - 2153)**

**TIME: 3 HOURS**

**MAX. MARKS: 50**

**Instructions to candidates**

- Answer **ALL** questions.
- Missing data may be suitably assumed.

- 1A. Design a circuit using K-map which converts 4-bit XS-3 code to its equivalent BCD code. Implement the minimum expression using NOR logic only.
- 1B. Design and implement a 4-bit shift register which performs operations as given in **Table 1B**.
- 1C. Write a Verilog code for divide-by-6 ripple counter using negative edge triggered JK flip flops.

(4+3+3)

- 2A. Implement the following functions using Xilinx FPGA

$$F_1 = \bar{A}BC + \bar{B}C + AB$$

$$F_2 = \bar{A}B + A\bar{B} + A\bar{C} + \bar{A}C$$

$$F = \overline{F_1 \oplus F_2}$$

Show the interconnection between various blocks. Specify the number of CLBs and LUTs required. Implement the design and give the content of each LUT.

- 2B. For the given Boolean function, determine a minimal sum using VEM technique, where  $x, y$  and  $z$  are the map variables.

$$f(A, B, x, y, z) = Ax\bar{y}\bar{z} + A\bar{x}\bar{y}z + Ax\bar{y}z + \bar{B}\bar{x}\bar{y}z + B\bar{x}y\bar{z} + \bar{x}yz + \bar{x}\bar{y}\bar{z}$$

- 2C. Implement 1010 overlapping sequence detector using Moore model. Use positive edge triggered D flip flop and required logic gates.

(4+3+3)

- 3A. Design a synchronous counter which goes through 0, 3, 6, 7 using positive edge triggered XY flip flop and all unused states will go to '0'. The truth table of XY flip-flop is given in **Table 3A**.

- 3B. Write a structural Verilog code for 2-bit comparator using 1-bit comparator and built-in primitives.

- 3C. Consider the circuit shown in **Fig. 3C**. Map the circuit using minimum number of decoder and basic gates.

(4+3+3)


- 4A. Consider the Boolean network given by the following equations

$$U_1 = U_2U_4U_5; \quad U_2 = U_3U_4; \quad U_3 = CU_4; \quad U_4 = A + D; \quad U_5 = BU_4;$$

4C. Write sequential Verilog code for synchronous modulo-8 Gray code counter.

$$(4+3+3)$$

PS		I/P	NS		O/P
y <sub>1</sub>	y <sub>2</sub>	X	Y <sub>1</sub>	Y <sub>2</sub>	Z
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	1	0	0
1	1	1	0	1	1

 

**Fig. 4B**