



## FIRST SEMESTER M.TECH. (ME/DEC) DEGREE END SEMESTER EXAMINATION

**JULY 2021**

**SUBJECT: DIGITAL VLSI DESIGN (ECE - 5152)**

**TIME: 2 HOURS**

**MAX. MARKS: 40**

### Instructions to candidates

- Answer any **FOUR Full** questions.
- Missing data may be suitably assumed.

- 1A. Discuss CMOS inverter with the help of circuit and VTC highlighting the impact of beta ratio on the performance of the circuit.
- 1B. Estimate the raise time and fall time of a CMOS inverter and establish the condition for obtaining symmetrical operation. (5+5)
- 2A. With the help of neat diagrams explain the fabrication of CMOS inverter using SOI process. What are its merits and demerits?
- 2B. i) Describe Latch-up phenomenon in bulk CMOS.  
ii) List the major sources of latch up and the remedies employed to prevent latch up. (5+5)
- 3A. With the help of suitable diagrams explain the key timing parameters related to sequential logic and explain the impact of the same on the circuit performance.
- 3B. With the help of neat diagrams explain clock distribution techniques. Also discuss their salient features. (5+5)
- 4A. i) Explain various technology scaling approaches and compare them.  
ii) Illustrate the impact of full scaling on Current density and Power delay product.
- 4B. Discuss any two techniques used to drive large capacitive loads in VLSI and compare them. (5+5)
- 5A. Show the complete architecture of 4 MB SRAM memory assuming that the architecture has 16 blocks/banks, and each block is square in shape.
- 5B. Discuss the working of 3T DRAM cell with the help of circuit and necessary waveforms. Highlight its salient features. (5+5)
- 6A. Implement XOR logic using i) Pseudo NMOS and ii) Dynamic CMOS logic. Also compare the circuits taking static CMOS as a reference.
- 6B. i) What is the need for design rules? Give reasons.  
ii) Explain different types of design rules and compare them. (5+5)