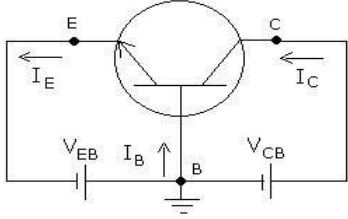
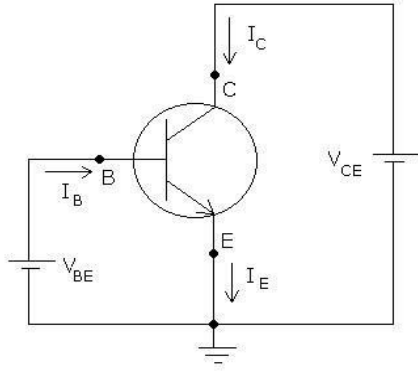
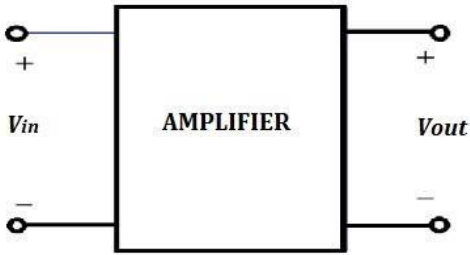
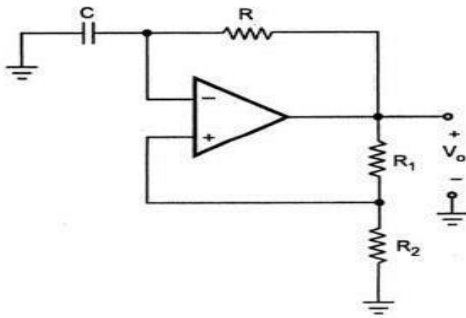


ECE - 1051: Basic Electronics

List of Formulae

1.	Diode Current	$I_D = I_s \left\{ e^{\frac{kV_D}{T_K}} - 1 \right\}$	I_s : Reverse saturation current V_D : Bias potential $k = 11,600/\eta$ T_K : Operating temperature in kelvin.
2.	Ripple Factor of Half-wave rectifier with capacitor filter	$\frac{1}{2\sqrt{3}fCR_L}$	f : frequency. C : Capacitance. R_L : Load resistance.
3.	Ripple Factor of fullwave rectifier with capacitor filter	$\frac{1}{4\sqrt{3}fCR_L}$	f : frequency. C : Capacitance. R_L : Load resistance.
4.	DC output voltage of Half-wave rectifier	$\frac{2fCR_L}{1+2fCR_L}$	f : frequency C : Capacitance R_L : Load resistance
5.	DC output voltage of full-wave rectifier	$\frac{4fCR_L}{1+4fCR_L}$	f : frequency C : Capacitance R_L : Load resistance
6.	Emitter Current of Bipolar junction transistor	$I_E = I_C + I_B$	I_C : Collector current I_B : Base current

7.	Collector Current of Bipolar junction transistor in CB Configuration	 $I_C = \alpha I_E + I_{CBO}$	α : Common-base current gain I_{CBO} : Common base leakage current
8.	Collector Current of Bipolar junction transistor in CE Configuration	 $I_C = \beta I_B + I_{CEO}$	β : Common emitter current gain. I_{CEO} : Common emitter leakage current.
9.	Voltage Gain of Amplifier in decibels	 $(A_V)_{dB} = 20 \log_{10} \left(\frac{V_{Out}}{V_{In}} \right)$	V_{Out} :Output voltage V_{In} :Input voltage

10.	Common Mode Rejection Ratio (CMRR)	$CMRR = 20\log\left(\frac{A_d}{A_{cm}}\right)$	A_d :Differential voltage gain A_{cm} :Common mode voltage gain
11.	Time period of output of Operational amplifier based square wave generator	 $T = 2RC\ln\left(\frac{1+\beta}{1-\beta}\right)$	β : Feedback factor $= \frac{R_2}{R_1 + R_2}$ R : Resistance. C : Capacitance

12.	Output voltage of Differential Amplifier	$V_o = A_d V_d + A_{cm} V_{cm}$	A_d : Differential voltage gain A_{cm} : Common mode voltage gain. V_d : Differential voltage. V_{cm} : Common mode voltage.
13.	Commutative Law	Property 1: $(x + y) = (y + x)$ Property 2: $x \cdot y = y \cdot x$	x, y, z, \dots are Boolean Variables
14.	Associative Law	Property 1: $(x + y) + z = x + (y + z)$ Property 2: $(x \cdot y) \cdot z = x \cdot (y \cdot z)$	
15.	Distributive Law	Property 1: $x (y + z) = x \cdot y + x \cdot z$ Property 2: $x + x \cdot y = x + y$	

16.	DeMorgan's Theorem	Theorem 1: $\overline{x+y} = \bar{x} \cdot \bar{y}$ Theorem 2: $\overline{x \cdot y} = \bar{x} + \bar{y}$	
17.	Amplitude Modulated signal	$S(t) = A_c[1 + k_a m(t)] \cos(2\pi f_c t)$	A_c : Amplitude of carrier signal. k_a : Amplitude sensitivity. $m(t)$: Modulating signal. f_c : frequency of carrier signal.
18.	Modulation Index of AM Signal	$\mu = k_a m(t)$	k_a : Amplitude sensitivity. $m(t)$: Modulating signal.
19.	Frequency Modulated signal	$S(t) = A_c \cos[2\pi f_c t + 2\pi k_f \int_0^t m(t) dt]$	A_c : Amplitude of carrier signal. k_f : Frequency sensitivity. $m(t)$: Modulating signal. f_c : frequency of carrier signal
20.	Carson's rule	$B_T = 2(\Delta f + f_m)$	Δf : Frequency deviation. f_m : frequency of modulating signal

