

III SEMESTER B.TECH (ELECTRICAL & ELECTRONICS ENGINEERING) MAKE-UP EXAMINATIONS, APRIL 2022

ELECTRICAL CIRCUIT ANALYSIS [ELE 2153]

REVISED CREDIT SYSTEM

Time:	3	Hrs.
	-	

Date: 19 APRIL 2022

Max. Marks: 50

Instructions to Candidates:

- ✤ Answer ALL the questions.
- Missing data may be suitably assumed.
- **1A.** Determine the current in the capacitor branch by superposition theorem in the circuit shown.





1B. In the network shown, find the value of R_L to which the maximum power can be delivered?



(04)

1C. Determine the current 'I' flowing in the 1Ω resistor in the circuit shown in figure.



(02)

- 2A. Evaluate the convolution integral y(t) = x(t) * h(t) of the following signals: $x(t) = 2\{u(t+1) - u(t-1)\}$ and $h(t) = t\{u(t+2) - u(t-2)\}$ Plot the relevant waveforms for x(t), h(t), and y(t). (05)
- **2B.** The first derivative of a waveform f(t) is given by $f^{1}(t) = \delta(t) + u(t) - 3.5u(t-2) + 2.5u(t-4) + 2\delta(t-5)$. Sketch f(t) and $f^{1}(t)$. (03)
- **2C.** Evaluate $\int_{-\infty}^{\infty} (e^{-t} \cos t\delta(t) + \sin 2t\delta(t \frac{\pi}{4})) dt$
- **3A** Find the Laplace transform of the periodic waveform shown in figure



(02)

3B In the circuit shown, switch is moved from A to B at t = 0, after attaining steady state at position A. Find i(t) for t > 0 using time domain analysis.



(04)

- **3C** A special generator has a voltage variation given by the equation v(t) = t, where t is the time in seconds and $t \ge 0$. This generator is connected to an RL series circuit where $R = 2\Omega L = 1H$ at time t = 0, by the closing of a switch. Find the equation of the current as a function of time i(t) using Laplace domain analysis. **(03)**
- **4A** Mention and prove the eigen function of CT-LTI systems. **(02)**
- **4B** Determine the Fourier series coefficients of the following signal:

 $x(t) = e^{-2t}$; $0 \le t \le 2$ repeating in every 2 units of time.

Plot the magnitude and phase spectrum for 7 frequency samples following symmetry and antisymmetric property, respectively. **(03)**

4C Consider an LTI system with frequency response

$$H(\omega) = \begin{cases} 1; & |\omega| < \omega_c \\ 0; & |\omega| > \omega_c \end{cases}.$$

The input to this filter is $x(t) = \frac{\sin at}{\pi t}$.

Find the output y(t) using properties of Fourier transform for

(i)
$$a < \omega_c$$
 and (ii) $a > \omega_c$.

(05)

5A Find the h parameters of the network shown.



5B Decompose the network shown into two, 2 port networks connected in cascade and hence find the overall T parameters.



5C A two port network is defined by the parameters: $Y_{21} = 6$, $Y_{22} = 8$, $h_{11} = 5$, $h_{12} = 2$. Find the T parameters. **(02)**