


**Department of Instrumentation and Control Engineering**  
**End Semester Examinations January 2022**  
**Analog Electronic Circuits – ICE 2151**

**PART B Question Paper**

***Instructions:** Answer All Questions, missing data may be suitably assumed  
Writing + Submission Time: 75 +10 minutes*

---

1. For the circuit shown in **Fig. Q1**, find
- The voltage at node 'X' by viewing 'M1' as a Common Source stage degenerated by the impedance seen at the source of 'M2'.
  - The voltage at node 'Y' by viewing 'M1' as a source follower and 'M2' as a common gate stage.
  - The differential voltage gain  $(V_X - V_Y)/V_{in}$

 

**Fig. Q1**

**[4M]**

2. Design a common source amplifier of **Fig. Q2** satisfying the following conditions
- When  $\lambda = 0$ ,  $R_G = 0$ , small signal gain is 5
  - When  $\lambda \neq 0$ ,  $R_G = 0$ , small signal gain is 4.88
  - When  $\lambda = 0$ ,  $R_G = 10k\Omega$ , small signal gain is 4

Assume  $V_{DD} = 1.8V$ ,  $V_G = 1V$ ,  $I_D = 2mA$ ,  $R_S = 100\Omega$ ,  $V_{TH} = 0.4V$ ,  $\mu_n C_{OX} = 100\mu A/V^2$ .  
With  $R_G = 0$ , what would be the maximum gain that could be obtained from the circuit?

iv)

 


Fig. Q2

[4M]

3. Design a circuit to drive a  $50\Omega$  load with a voltage gain of 0.5 and a power budget of 10mW. Assume  $\mu_n C_{ox} = 100 \mu A/V^2$ ,  $V_{TH} = 0.5 V$ ,  $\lambda = 0$ , and  $V_{DD} = 1.8 V$  [3M]
4. Consider a NMOS with  $W=2\mu m$ ,  $L=0.18\mu m$  and 0.7V across its gate and source terminals. Determine its all small signal parameters. Assume  $\mu_n C_{ox}=100\mu A/V^2$ ,  $V_{th}=0.4V$ ,  $\lambda=0$  and  $V_{DD}=1.8V$ . [3M]
5. Find the loop gain and closed loop gain of the circuit shown in Fig. Q5. [3M]

 


Fig. Q5

6. Calculate the oscillating frequency of a FET Hartley oscillator with  $C = 250pF$ ,  $L_1 = L_2 = 1.5 mH$ , and mutual inductance between  $L_1$  and  $L_2$  is 0.5 mH. [3M]

\*\*\*\*\*