## END SEMESTER EXAMINATIONS (JANUARY 2022) -QUESTION PAPER - PART A

(Copy)

COURSE CODE	: ICE-2154
COURSE NAME	: NETWORRK ANALYSIS AND SIGNALS
SEMESTER	: 111
DATE OF EXAM	: 20/01/2022
DURATION	: 45 + 3 minutes

#### Instructions for Students:

(1) ANSWER ALL THE QUESTIONS.
(2) EACH QUESTION CARRIES 1 MARK.
(3) YOU ARE INSTRUCTED TO INFORM THE INVIGILATOR AFTER SUBMISSION OF THIS FORM IN THE CHAT SECTION.

\* Required

\* This form will record your name, please fill your name.

#### STUDENT NAME: \*

2

**REGISTRATION NUMBER: \*** 

The value must be a number

Question (1 Point)

# A LTI system has impulse response $h(t) = \delta(t-t_0)$ where $t_0$ is a positive constant. The system is

- Causal & unstable
- 🔘 Non causal & stable
- Noncausal & unstable
- Causal & stable



#### For the circuit shown, Norton's current through the terminals AB is -



🔘 0.5 A

🔘 - 1 A

() 1 A

2/14/2022 - 0.5 A



### For the network shown Z<sub>22</sub> is



Fourier series representation is used for analysis of---- signals. (1 Point)

 $\bigcirc\,$  both for periodic and non periodic

O Aperiodic

O periodic

7

Question (1 Point)

Signal x(t) = u(10-t) is

None of these

All the above

🔵 left sided

Bounded,

Non causal

#### Question (1 Point)

## Signal $x(t) = (\cos (2\pi t))^2$ is .... with fundamental period—and is – signal.

🔵 Periodic, 1 sec, Power

O Periodic, 1 sec, Energy

Periodic, 0.5 sec, Power

Non periodic, 0.5 sec, Power

For the circuit shown in figure, if  $v = 20e^{-2t}$  V and  $i = 0.5 e^{-2t}$  A, determine R and C values.



O 40 Ohms, 12.5 mF

20 Ohms, 12.5 F

20 Ohms, 12.5 mF

20 Ohms, 12.5 micro F

## Two LTI systems with $h_1(t) = \delta(t+3)$ and $h_2(t) = \delta(t-3)$ are connected in parallel. Overall system is

Memoryless, stable and causal system

Memory, stable and non-causal system

Memoryless, stable and non-causal system

Memoryless, unstable and causal system

11

In the circuit shown in figure below switch is closed at t = 0, before which steady state has been reached. Inductor current at  $t = \infty$  is –



2/14/2022

Looking at terminals A and B, Thevenin's equivalent voltage for the circuit shown in figure below is --.



$\bigcirc$	4	V
------------	---	---

🔘 5 V

🔘 -4 V

🔘 -5 V

### System $y(t) = t^2 x(t)$ is

🔘 Linear

O Non Causal

O None of these

◯ Time invariant

◯ stable

$$\int_{-\infty}^{\infty} (t-1)^2 \,\delta(t-1)dt =$$

0 -1

 $\bigcirc$  0

01

O none of these



() 1 A

2/14/2022 -1 A

Question (1 Point)



For the circuit shown in figure, determine the current in load resistance of  $3\Omega$ .



() 2 A

🔘 1.5 A

() 1 A

🔾 3 A

18

What is the function value x(0) if  $X(s) = \frac{s+4}{(s+1)(s+2)}$ 

0 1

0 2

O Infintte

0

2/14/2022

Fourier transform of  $x(t) = e^{-2(t-1)}u(t-1)$  is

(1) 
$$X(j\omega) = \frac{e^{j2\omega}}{2+j\omega}$$
  
(2)  $X(j\omega) = \frac{1}{2+j(\omega-1)}$   
(3)  $X(j\omega) = \frac{e^{-j\omega}}{2+j(\omega-1)}$   
(4)  $X(j\omega) = \frac{e^{-j\omega}}{2+j\omega}$ 

03

0 1

0 2

 $\bigcirc$  None of these

In the circuit shown, voltage V across 2A current source is ---



🔾 32 V

○ 12 V 2/14/2022

Question (1 Point)

Sequence  $x(n) = (-1)^{n^2}$ 

O unbounded

 $\bigcirc$  right sided

 $\bigcirc$  None of these

O All the above

left sided

For the network shown in figure, determine the current through  $R_L = 20\Omega$  resistor.



🔘 0 A

🔵 1 A

🔵 2 A

🔵 1.5 A

## . Expression for current i(t) for the circuit shown in figure is t=0 IH (1) 2e<sup>-5t</sup> (2) $2(1-e^{-5t})$ (3) $2e^{-0.2t}$ $(4)2(1-e^{-0.2t})$

0 4

01

Question (1 Point)

In the circuit shown in figure below switch is closed at t = 0, before which steady state has been reached. Current in 10Ω resistor at t = 0+ is –



2/14/2022 1 A

In the circuit shown in figure below, switch is opened at t = 0, before which steady state has been reached. Capacitor voltage at t = 0+ is –



() 4 V

 $\bigcirc vv$ 

🔘 8 V

🔵 12 V

$$\sum_{k=-\infty}^{\infty} \frac{\sin^2 k\pi/4}{k^2} = (1) \frac{\pi^2}{8} \qquad (2) \frac{\pi^2}{4} \qquad (3) \frac{1}{8} \qquad (4) \frac{1}{4}$$

In the circuit shown in figure below switch is closed at t = 0, before which steady state has been reached. Inductor current at t = 0 + is - 1



🔾 3 A

🔾 2 A

O A 0

🔾 1 A

28

# What is the function value $x(\infty)$ if $X(s) = \frac{s+4}{s^3+3s^2+s}$



None of these

0 4

0 ()

2/14/2022

```
Which one of the following is the signal corresponding to

a_k = |k| - 3 \le k \le 3; \omega_0 = \pi

(1) 3\cos(3\pi t) + 2\cos(2\pi t) + 1\cos(\pi t)

(2) 6\cos(3\pi t) + 4\cos(2\pi t) + 2\cos(\pi t)

(3) 6\cos(3\pi t) + 4\cos(2\pi t) + 2\cos(\pi t) + 1

(4) 6\sin(3\pi t) + 4\sin(2\pi t) + 2\sin(\pi t)
```

0 4

0 1

О З





In the circuit shown in figure below, switch is opened at t = 0, before which steady state has been reached. Capacitor voltage at  $t = \infty$  is –



🔘 12 V

🔾 4 V

() 8 V

 $\bigcirc$  0 V

Th:	e fundamental pe $\frac{2\pi}{\omega_0}$	riod 2.	l of a discrete $\frac{\omega_0}{2\pi}$	tim 3.	te complex exponente $2\pi\omega_0 m$	ntial 4.	sequence is $\frac{2\pi m}{\omega_0}$
0 4							
0 1							
0 2							
3							

This content is neither created nor endorsed by Microsoft. The data you submit will be sent to the form owner.

📲 Microsoft Forms