



MANIPAL INSTITUTE OF TECHNOLOGY

MANIPAL

(A constituent unit of MAHE, Manipal)

THIRD SEMESTER B. TECH (ELECTRONICS AND INSTRUMENTATION)

PROCTORED ONLINE END SEMESTER EXAMINATION Jan. 2022

SUBJECT: NETWORK ANALYSIS AND SIGNALS (ICE 2154)


TIME: 75 MINUTES

DATE: 20-01-2022

MAX MARKS: 20


Note: Answer All questions.

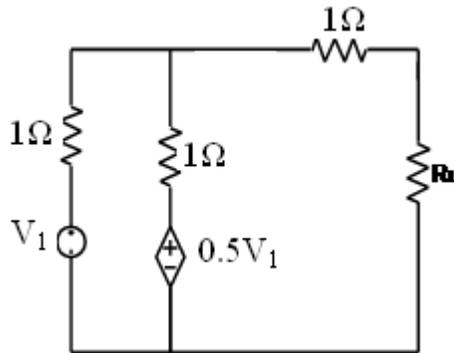- 1 A For the circuit shown in figure, find the value of R_L for maximum power to the load. Also calculate the maximum power delivered to the load.




3

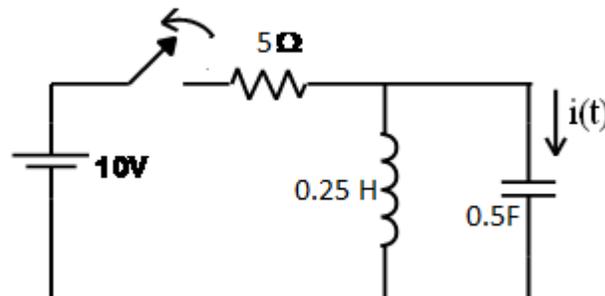- B In the network shown in figure, the switch k is opened at $t=0$ after the network has attained steady state with the switch closed. Obtain expression for current $i(t)$ in complementary and particular solution form. Also obtain total solution for $i(t)$.



3

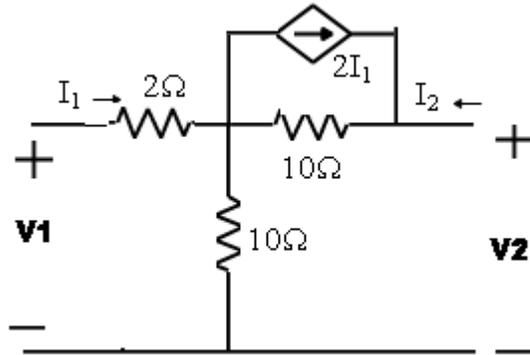C For the network shown in figure determine Z and Y parameters.



4

2 A Input $x(t)$ and impulse response $h(t)$ of a LTI system is given by $x(t) = u(t - 2) - u(t - 4)$ and $h(t) = u(t + 2) - u(t - 2)$. Use convolution integral to evaluate the output $y(t)$ of the system and sketch $y(t)$.

4

B Evaluate appropriate Fourier representation and sketch magnitude and phase spectra of

(i) $x(t) = 1 + \cos(2\pi t) + \sin(3\pi t)$

3

(ii) $x(t) = e^{3t} u(-t)$

C A LTI system is described by $\frac{d^2 y(t)}{dt^2} + 3 \frac{dy(t)}{dt} + 2y(t) = \frac{dx(t)}{dt} + 2x(t)$.

Determine (i) Frequency response of the system (ii) impulse response of the system (iii) Output of the system for an input $x(t) = e^{-2t} u(t)$

3
