

Exam Date & Time: 23-Apr-2022 (02:00 PM - 05:00 PM)



## MANIPAL ACADEMY OF HIGHER EDUCATION

THIRD SEMESTER B.TECH END SEMESTER MAKE UP EXAMINATIONS, APRIL 2022

### ELECTRONIC MEASUREMENTS [ICE 2153]

**Marks: 50**


**Duration: 180 mins.**

#### A

**Answer all the questions.**

Instructions to Candidates: Answer ALL questions Missing data may be suitably assumed

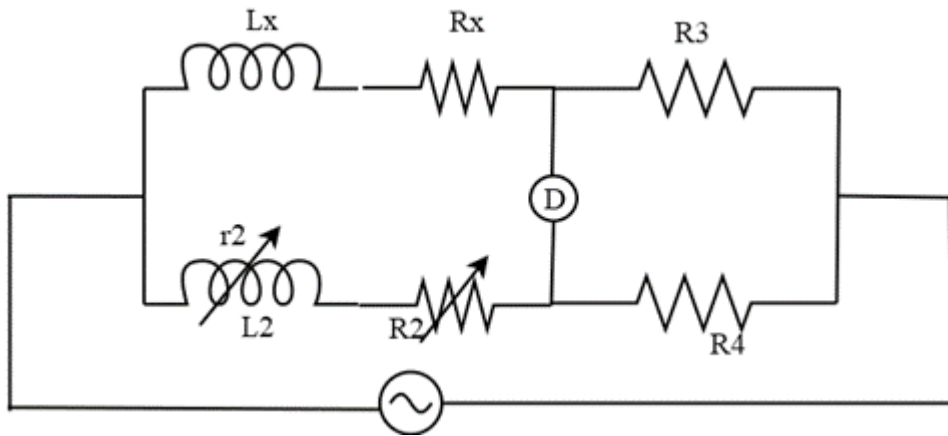- 1) Derive the expression of unknown inductance using Anderson bridge and draw the phasor diagram for the same. (4)
  - A)
  - B) Draw the circuit diagram for the measurement of energy in a 3 phase 3 wire system using 2 element energy meter. (2)
- i
- ii A single-phase energy meter makes 500 revolutions per kWh. It is found on testing as making 40 revolutions in 58.1 seconds at 5kW full load. Find the percentage error. (2)
- C) Explain the operation of potentiometric recorder with its schematic. (2)
- 2) With a block diagram explain the working of different components of CRT. (4)
  - A)
  - B) Explain the working of high impedance probe and active probe with necessary diagram. (4)
  - C) Derive an expression for harmonic distortion. (2)
- 3) Differentiate the working of passive matrix and active matrix LCD display with necessary figures. Also explain the operation for 5X5 LCD active matrix display to represent the character 'Z'. (5)
  - A)
  - B) Explain the working of swept heterodyne spectrum analyser with its diagram. (3)
  - C) Find the value of  $L_x$  and  $R_x$  at balanced condition for the bridge shown below, when  $L_2=70\text{mH}$ ,  $r_2=600\Omega$ ,  $R_2=300\Omega$ ,  $R_3=200\Omega$  and  $R_4=300\Omega$ . (2)



- 4) State the disadvantage of single slope ADC and also explain the mitigation process to overcome the same with necessary figures and equations. (4)
- A)
- B) Explain the working of different components of magnetic recorder with its block diagram. (3)
- C) Draw a circuit for 4-bit R-2R type DAC. With necessary equations, derive the expression for output voltage for the digital input 0010. (Consider logic 1 as 'V'). (3)
- 5) An unknown impedance component is connected in series with working coil for measurement of Q-factor. With necessary figure and equations, derive the expression for Q-factor. (4)
- A)
- B) With a block diagram explain the working of frequency selective wave analyzer. (3)
- C) Explain the working of digital frequency meter with gate control flip-flop with necessary figures. (3)

-----End-----