Reg. No.



## (A constituent unit of MAHE, Manipal)

## V SEMESTER B. TECH (ELECTRICAL & ELECTRONICS ENGINEERING) END SEMESTER ON-LINE PROCTORED EXAMINATIONS DECEMBER 2021

## **POWER SYSTEM ANALYSIS [ELE 3154]**

REVISED CREDIT SYSTEM

| Time <sup>.</sup> 75 Minutes + 10 Minutes | Date: 30 December 2021 | Max Marks: 20 |
|---|------------------------|---------------|

## Instructions to Candidates:

- ✤ Answer ALL questions.
- Time: 75 minutes for writing + 10 minutes for uploading.
- Write your name, registration number, section and sign on the top right corner of every answer sheet.
- Write page numbers and total number of pages on each page.
- Missing data may be suitably assumed.
- **1A.** For the system shown in Fig. 1A, determine the generator terminal voltage. The transformer 'T' comprises of 3 single phase units each rated 16.667 MVA, 14/127 kV and 10% reactance. Choose 100MVA, 14kV in the generator circuit.



**1B.** Consider the 3 bus system shown in Fig. 1B. The generators are of 100 MVA with transient reactance of 10% each. Both transformers are 100 MVA with a leakage reactance of 5%. The reactance of each of the lines to a base of 100 MVA, 110 kV is 10%. Obtain the short circuit current in p.u for a 3 phase solid short circuit on bus 3. Assume pre-fault voltage to be 1.0 pu



(02)

**1C.** A synchronous generator is connected to a synchronous motor through a transmission line Fig. 1C. A fault occurs at one-third distance away from the motor towards the generator. The symmetrical components of the current from the generator towards the fault are (in pu):  $I_{a1} = 0.8 - j \ 1.4$ ;  $I_{a2} = j \ 0.5$ ;  $I_{a0} = j \ 3.375$  and from the motor toward the fault are  $I_{a1} = -0.8 - j \ 3.1$ ;  $I_{a2} = j \ 0.625$ ;  $I_{a0} = 0$ .

Assume  $X_1 = X_2$  for generator, motor and transmission line. Describe the type of fault. What is the fault current? Also find the pre-fault current if any, in line 'a'.



- **2A.** A 20 MVA, three-phase, 50 Hz generator delivers rated power at unity power factor via a step up transformer, double circuit transmission line and step down transformer to an infinite bus bar. The generator unit has a kinetic energy of 2.5 MJ/MVA at rated speed. It's Xd' = 0.3 per unit. The transformers have negligible resistance and reactance of 0.3 per unit on a 20 MVA base. The voltage behind the transient reactance is 1.05 per unit and the voltage of the infinite bus is 1 per unit. A three phase short circuit occurs at the mid-point of one of the transmission lines. Determine the variation of power angle using point by point method for a period of 0.5 sec with  $\Delta t$ =0.05sec.
- **2B.** For the power system described in question 2A, ascertain the stability of the system. Also determine the accelerating power and the power angle at the end of 0.6 sec.
- **2C.** A two bus power system is as shown below. Using Newton Raphson method, determine the voltage magnitude  $|V_2|$  and power angle  $\delta_2$  at bus no. 2 at the end of 1 iteration.



Assume the following initial conditions  $\delta_2^{(0)} = 0$ (zero) rad,  $V_2^{(0)} = 1$  p. u,  $|V_1|=1$  p.u.

(03)

ELE 3154

(05)