



MANIPAL INSTITUTE OF TECHNOLOGY

MANIPAL
(A constituent unit of MAHE, Manipal)

V11 SEMESTER BTECH. (E & C) DEGREE END SEMESTER EXAMINATION

FEBRUARY 2022-March 2022

SUBJECT: Electronic System Design (ECE -4072)

TIME: 75 minutes

MAX. MARKS: 20M

Instructions to candidates

- Answer **ALL** questions.
- Missing data may be suitably assumed.

Q. No.	Questions	Marks
1A.	Discuss typical signal flow chain of electronic system design with an example and discuss different stages of system development.	5
1B.	Discuss exponential law of reliability. The failure rate per hour of a certain electronic product is given by: $0.02(1 + 30e^{-2t} + e^{-\frac{t}{20}})$ Find MTTF at $t=104$ hours.	3
1C.	A displacement sensor produces an output of 10mV per centimetre of movement and has an output resistance of $300\ \Omega$. It is connected to an amplifier that has an unloaded voltage gain of 15, an input resistance of $5k\Omega$ and an output resistance of 150Ω . The output of the amplifier is connected to a voltmeter with an input resistance of $2k\Omega$. Evaluate what voltage will be displayed on the voltmeter for a displacement of the sensor of 1 meter	2
2A.	i) Implement first-order sigma-delta modulator using a switched capacitor integrator. ii) Suppose a system is using a 12-bit ADC to output a temperature value once every second (1Hz). calculate the oversampling frequency to increase the resolution the measurement to 16 bits.	5
2B.	Using the switched capacitor technique, implement the first order passive RC Low pass circuit so that the product of RC is 1msec and $f_{clk}=100KHz$. Assume $C1=10pF$.	3
2C.	Build the bathtub curve used to correlate quality and reliability of an electronic product	2