



### FIRST SEMESTER M.TECH (POWER ELECTRONICS & DRIVES) END SEMESTER ON-LINE PROCTORED EXAMINATIONS

FEBRUARY 2022

POWER SEMICONDUCTOR CONTROLLED DRIVES [ELE 5173]

REVISED CREDIT SYSTEM

Time: 75 Minutes + 10 Minutes

Date: 07 February 2022

Max. Marks: 20

**Instructions to Candidates:**

- ❖ Answer ALL the questions.
- ❖ Missing data may be suitably assumed.
- ❖ Time: 75 minutes for writing + 10 minutes for uploading.

- 1A.** A motor is used to drive a hoist. Motor characteristics are given by  
Quadrant I and II:  $T = 200 - 0.2N$ , N-m  
Quadrant III and IV:  $T = -200 - 0.2N$ , N-m  
where N is the speed in rpm. When the hoist is loaded, the net load torque  $T_L = 100$  N-m and when it is unloaded, net load torque  $T_L = -80$  N-m.  
Obtain the equilibrium speed for operation in second and fourth quadrants with drawing a neat sketch showing the operation of a hoist in above quadrants. **(03)**
- 1B.** A motor drives a winch drum which has to lift up a weight of 250kg at a uniform speed of 1.2m/s. The motor is running at a speed of 1200rpm. The moment of inertia of motor and the winch are  $0.2 \text{ kgm}^2$  and  $0.3 \text{ kgm}^2$  respectively. In the absence of weight, motor develops a torque of  $80.05 \text{ N-m}$  when running at 1200rpm. Determine the following,  
(i) Equivalent torque referred to motor shaft  
(ii) Equivalent moment of inertia referred to the motor shaft. **(02)**
- 1C.** A 220V, 1.98kW, 1500rpm separately excited DC motor is fed from a single phase fully controlled rectifier with an ac source voltage of 230V, 50Hz. Armature resistance  $R_a$  is  $2.03 \Omega$  and armature inductance  $L_a$  is 50mH. For  $\alpha = 60^\circ$  and operating efficiency = 90%, find no load and critical speed for the drive. Also derive the expression used. **(05)**
- 2A.** A 2.2 kW, 220V, 11.6A, 1500 rpm dc separately excited motor has an armature resistance and inductance of  $2 \Omega$  and 32.5mH respectively. This motor is controlled by a Class A chopper with a frequency of 500Hz and the input voltage of 220V. The motor is driving a load whose torque is proportional to the speed. At duty cycle  $D = 0.9$  the motor runs at 1260rpm. Calculate the value of duty cycle at 800rpm. **(02)**

- 2B.** A 440V, 50Hz, 6 pole delta connected 3-phase induction motor operating with 5.501% slip, has the rotor resistance referred to the stator is  $2\Omega$ . The motor speed is controlled by stator voltage control and the motor drives a load whose torque is given as  $T_L=k(1-s)$ . Estimate the motor speed and torque when the terminal voltage is 280V. Neglect the stator impedance and rotor leakage reactance. **(04)**
- 2C.** Draw the circuit schematics of the 3 phase AC voltage controller for 3 phase induction motor to control the speed of a water pump application for star and delta connected stator. Draw the block diagram of the closed loop speed control of the 3 phase AC voltage controller. Also explain the functioning of each block. **(04)**