

Exam Date & Time: 25-Jul-2022 (02:00 PM - 05:00 PM)



MANIPAL ACADEMY OF HIGHER EDUCATION

FOURTH SEMESTER B.TECH MAKEUP EXAMINATIONS, JULY 2022
DIGITAL SYSTEM DESIGN [BME 2253]

Marks: 50

Duration: 180 mins.

A

Answer all the questions.

Instructions to Candidates: Answer ALL questions Missing data may be suitably assumed

- 1) Differentiate the full-custom and semicustom Application Specific Integrated Circuit (ASIC). Write an advantage and disadvantage of each of above ASIC. (3)
 - A)
 - B) Design a two input CMOS OR gate with a neat circuit, mention the details of pullup and pull-down transistors. Verify the operation of gate considering possible input combinations. (3)
 - C) Design multiplexer using TG and other basic gates. Explain its operation. (4)
- 2) State Shannon's expansion theorem considering three logic variables. Design a MUX based circuit by applying the theorem to find the co factors of the following function with respect to variable w_2 : (4)
 - A) $f(w_1, w_2, w_3) = w_1w_2 + w_1w_3 + w_2w_3$. (4)
 - B) Design an AND-OR plane of a PLA considering NMOS programmable switches to realize the following function: $Y = ABC + B'C$. Draw the diagram and explain the operation of the given planes. (3)
 - C) Explain the architecture of PAL. Differentiate PAL and Complex PLD. (3)
- 3) Design a CMOS inverter circuit and explain how it is different from a NMOS inverter. (3)
 - A)
 - B) Design a Verilog HDL module for realizing the following function using gate primitive: $F = AB + AB' + C$. Show that instance of the specified module are created in two styles. (3)
Note: Write comments on each line.

- C) Discuss the architecture of a CPLD along with its advantage and disadvantage. (4)
- 4) Describe the FPGA configurable logic block (CLB) with a neat diagram. How it is different from CPLD. (4)
- A)
- B) Design 2 input LUTs design, for realising the given function, $F = AB + CD'$. Write the details of function table and the LUT used for each stage. (3)
- C) Illustrate the role of Verilog HDL in the digital system design. Explain how these HDL is different from a programming language like C++ or python. (3)
- 5) Design a Verilog HDL module to synthesis a full adder circuit using assignment statements. (3)
- A)
- B) Explain how always block statement are used in the design of a basic sequential circuit in Verilog HD. (3)
- C) Discuss the two types of module instantiation. How they are different. Consider an example and create a of a module instance. (4)

-----End-----