

Question Paper

Exam Date & Time: 30-Jun-2022 (09:00 AM - 12:00 PM)



MANIPAL ACADEMY OF HIGHER EDUCATION

SECOND SEMESTER B.TECH. EXAMINATIONS (MIT MANIPAL) - JUNE/JULY 2022
SUBJECT : ECE 1051 - BASIC ELECTRONICS

Marks: 50

Duration: 180 mins.

Answer all the questions.

- 1A) An AC voltage of 230V, 50Hz is applied to transformer having turns ratio 10:1. The secondary of transformer is connected to half wave rectifier. The diode has cut-in voltage 0.6V and forward resistance 10Ω . If the load resistance is 500Ω , determine the average and rms values of output current and voltage. What should be the PIV rating of the diode? (4)
- 1B) Find the static and dynamic resistances of germanium diode at 30°C for 0.2 V forward bias voltage. Assume the reverse saturation current as $1\mu\text{A}$ at 30°C . (3)
- 1C) For the Zener diode regulator, $R_S = 10\Omega$, $V_Z = 10\text{V}$, $V_i = 25\text{V}$. Find the minimum and maximum current through Zener diode when the load resistance R_L is varied between 10Ω and 100Ω . (3)
- 2A) Draw the circuit diagram of RC coupled Amplifier and explain the role of each component. If the mid band gain of the amplifier is 10dB and cut-off frequencies are 1KHz and 100KHz, sketch the frequency response of amplifier indicating the bandwidth and the gain at cut-off frequencies. (4)
- 2B) For a fixed bias circuit using Si transistor, $R_B = 500\text{K}\Omega$, $R_C = 2\text{K}\Omega$, $V_{CC} = 15\text{V}$, $I_{CBO} = 20\mu\text{A}$ and $\beta = 70$. Find the collector current and voltage at operating point. Take $V_{BE} = 0.7\text{V}$. (3)
- 2C) A BJT has alpha (dc) 0.998 and collector-to-base reverse saturation current $1\mu\text{A}$. If emitter current is 5mA, calculate the collector and base currents. Draw the input and output characteristics of common base configuration. (3)
- 3A) Simplify the Boolean expression using 4 variable Karnaugh Map $F = \sum m(0,2,5,7,8,10,13,15)$. Realize the simplified expression in terms of NAND gate. (4)
- 3B) Design an OP-AMP circuit, such that the output voltage is given by $V_{OUT} = -(0.5V_1 + 0.75V_2)$, where V_1 and V_2 are input voltages. Choose $R_F = 10\text{K}\Omega$. (3)
- 3C) An OP-AMP has differential voltage gain of 100,000 and CMRR of 60dB. If non inverting input voltage is $150\mu\text{V}$ and inverting input voltage is $140\mu\text{V}$, calculate the output voltage of OPAMP. (3)
- 4A) Draw the circuit diagram of JK flipflop using NAND gates. Write the truth table. State the differences between latches and Flipflops. (4)
- 4B) Perform $15_{(10)} - 31_{(10)}$ using two's complement method. (3)
- 4C) Generate (7, 4) Hamming code for the binary data '1000'. Also, write the 2421 BCD representation of decimal number 7. (3)
- 5A) An audio signal $10\sin(2\pi 1000t)$ volts amplitude modulates a carrier of $40\sin(2\pi 1000 \times 10^3 t)$ volts. Find the modulation index, sideband frequencies, Bandwidth and amplitude of each side band components. (4)
- 5B) Given a FM signal $V_{FM}(t) = 10 \cos [2\pi 10^8 t + 5\sin(2\pi 15000t)]$, Calculate the carrier frequency, modulating frequency, frequency deviation and Bandwidth. (3)
- 5C) Sketch the ASK, FSK and PSK signals for the 6-bit binary data '101001'. (3)

-----End-----