

Exam Date & Time: 16-Jun-2022 (02:00 PM - 05:00 PM)



MANIPAL ACADEMY OF HIGHER EDUCATION

FOURTH SEMESTER B.TECH END SEMESTER EXAMINATIONS, JUNE 2022
DIGITAL SYSTEM DESIGN [BME 2253]

Marks: 50

Duration: 180 mins.

A


Answer all the questions.

Instructions to Candidates:


Answer ALL questions Missing data may be suitably assumed

- 1) Classify the Semi-custom Application Specific Integrated Circuit (ASIC). Identify the one such device with programmable provision and discuss its benefit over full-custom ASIC. (3)
 - A)
 - B) Design a three input CMOS AND gate with a neat circuit, mention the details of pullup and pull-down transistors. Verify the operation of gate considering possible input combinations (3)
 - C) Design latch using TG and other basic gates. Explain its operation. (4)
- 2) State Shannon's expansion theorem. Design a MUX based circuit by applying the theorem to find the co factors of the following function with respect to variable w1: (4)
 - A) $f(w1, w2, w3) = w1w2 + w1w3 + w2w3$.
 - B) Design an AND-OR plane of a PLA considering NMOS programmable switches to realize the following function: $Y = A'B + C'D$. Draw the diagram and explain the operation of the given planes. (3)
 - C) Explain the architecture of Complex PLD with a central PIA. Differentiate how Complex PLD is different from a Simple PLD. (3)
- 3) Apply the knowledge of the NMOS transistor and arrange them as SRAM cell circuit, and illustrate the working details of the circuit. (3)
 - A)

 - B) Design a Verilog HDL module for realizing the following function using gate primitive:
 $F = AB + A'C + CD$. Show that instance of the specified module are created in two styles.
 Note: Write comments on each line. (3)
- C) Identify the benefit of Programmable Logic devices. Draw the architecture of a simple Programmable array logic and explain how the macrocell helps in the design of a sequential or combinational logic circuit. (4)
- 4) Describe the general architecture of FPGA. Further elaborate the elements configurable logic block (CLB) and discuss its role in the design of a digital system. (4)
- A)
- B) Design 2 input LUTs design, for realising the given function, $F = A'B + CD$. Write the details of function table and the LUT used for each stage. (3)
- C) Identify the general important steps considered during the design a system using FPGA. Illustrate the role of HDL in the digital system design are using FPGA. (3)
- 5) Design a Verilog HDL module to synthesis a half adder circuit using assignment statements. Consider a time scale of 1ns/ 1ps. (3)
- A)
- B) Design a Verilog module for 1-bit full adder (as shown in figure 5(i). Write a new Verilog module for synthesising a 4-bit adder described in the figure 5(ii), using the instances of the above designed 1-bit adder module. Specify the instantiation method used. (4)



5 (i) 1 bit adder logic circuit

 

5 (ii) 4bit adder circuit

- C) Design a basic sequential circuit module using Verilog HDL module using always block. (3)

-----End-----