



DEPARTMENT OF MECHATRONICS

IV SEMESTER B.TECH. (MECHATRONICS)

END SEMESTER EXAMINATIONS, JUNE 2022



SUBJECT: LINEAR INTEGRATED CIRCUITS & APPLICATIONS [MTE 2254]



Time: 3 Hours


MAX. MARKS: 50

Instructions to Candidates:

❖ Answer all questions.

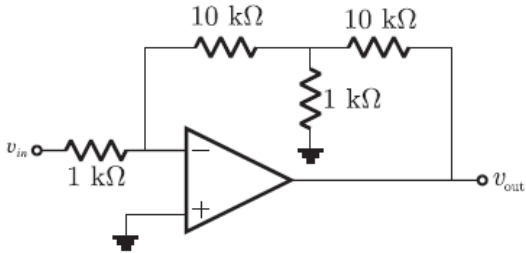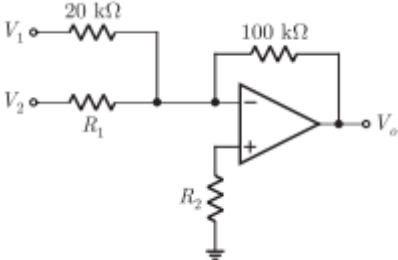Q. No		M	C	P	L	B
			O	O	O	L
1A.	Assuming the operational amplifier to be ideal, Obtain the gain $\frac{V_{out}}{V_{in}}$ for the circuit shown in figure 1A.	3	1	1	1	3
	 <p>Figure 1A</p>					
1B.	Consider the opamp circuit shown in figure 1B.	4	1	1	1	3
	 <p>Figure 1B</p> <p>a) If $V_1 = 0.2V$, $V_2 = 0.6V$ and $V_o = -7V$ and the opamp is ideal. Calculate the value of R_1.</p> <p>b) Let $V_1 = V_2 = V_c \sin 2\pi ft$ and $R_1 = 20k\Omega$. The opamp has a slew rate of $0.5V/\mu S$ with its parameter being ideal. Obtain the value of V_c and Frequency F.</p>					

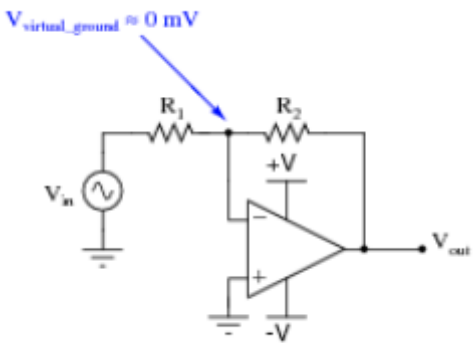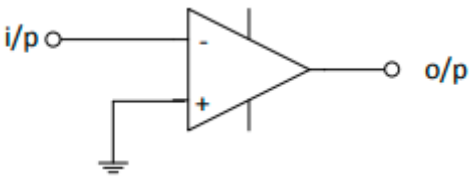	c) Let $V_1=V_2$ and $R_1 = 20k\Omega$. Assume that opamp is ideal except for non-zero input bias current. Obtain the value R_2 for which output voltage of opamp to be zero.					
1C.	<p>The junction between the two resistors and the inverting input of the operational amplifier is often referred to as a virtual ground, the voltage between it and ground being (almost) zero over a wide range of circuit conditions:</p> <p>a) If the operational amplifier is driven into saturation, though, the “virtual ground” will no longer be at ground potential. Explain the reason for this , and mention the condition(s) which may cause this to happen.</p>  <p style="text-align: center;">Figure 1C</p>	3	1	2	2	4
2A.	<p>If the input to the circuit of figure 2A is a sine wave. Determine the output . Justify the reason for the obtained output.</p>  <p style="text-align: center;">Figure 2A</p>	2	1	1	1	4
2B.	The input of a certain regulator increases by 3.5 V. As a result, the output voltage increases by 0.042 V. The nominal output is 20 V. Determine the line regulation in both % and in % V.	2	3	1	1	3
2C.	<p>Justify the correctness or otherwise of the following statements:</p> <ol style="list-style-type: none"> 1. Switching regulators are more efficient than linear regulator making them ideal for low voltage high current applications. 2. The voltage drop of switching regulator is similar to a resistor voltage drop. 3. Sample-and-hold circuits in analog-to digital converters (ADCs) are designed to stabilize the input analog signal during the conversion process. 	6	3	2	2	4
3A.	Explain the working of two basic linear regulators.	3	3	1	1	2

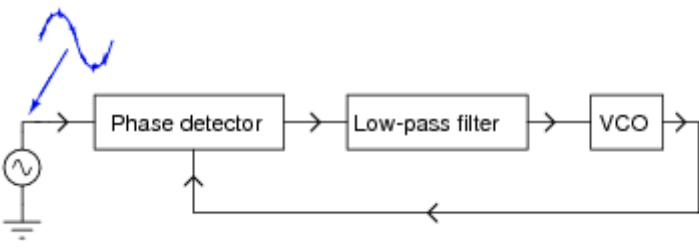3B.	The PLL acts like a low-pass filter, the high-frequency VCO noise mostly get rejected. Justify the correctness of the statement with the working principle.	4	3	2	2	4
3C.	<p>Suppose that a “noisy” AC signal of constant frequency is connected to the input of a phase-locked loop circuit:</p>  <p>Characterize the output waveform generated by the VCO. Will it be “noisy” as well? Justify.</p>	3	3	3	5	4
4A.	In a R-2R ladder type DAC if a switch status is '0', 0V is applied and if a switch status is '1', 5V is applied to the corresponding terminal of the DAC. Obtain the output voltage (V_0) for the switch status $S_0 = 0, S_1 = 1, S_2 = 1$.	2	4	1	1	3
4B.	Mention the major advantage of the R/2R ladder digital-to-analog, as compared to a binary-weighted digital-to-analog converter?	3	4	1	1	2
4C.	A 4-bit successive approximation type ADC has a full scale value of 15V. Obtain the sequence of the states, if SAR traverse, for the conversion of an input of 8.15V. With the help of a block diagram explain the working of SAR.	5	4	1	1	3
5A.	Design a flow chart for building time monitored touchless automatic sanitizer dispenser using 555 timer.	3	2	3	5	5
5B.	Highlight the need of an hour to develop an eco friendly process for the recycling of waste printed circuit board.	3	1	7	5	4
5C.	Discuss any four performance parameter for assessing the working of a industry grade voltage regulators.	4	3	1	1	2