

Question Paper

Exam Date & Time: 08-Jul-2022 (09:30 AM - 12:30 PM)



MANIPAL ACADEMY OF HIGHER EDUCATION

INTERNATIONAL CENTRE FOR APPLIED SCIENCES

II SEMESTER B.Sc.(Applied Sciences) in Engg.

END SEMESTER THEORY EXAMINATION- MAY/JUNE-2022

Elements Of Electrical and Electronics Engg. [IEE 121 - S2]

Marks: 50

Duration: 180 mins.

Answer all the questions.

Missing data, if any, may be suitably assumed

- 1) Find the current I for the circuit shown in Fig.Q1A. (3)

A)

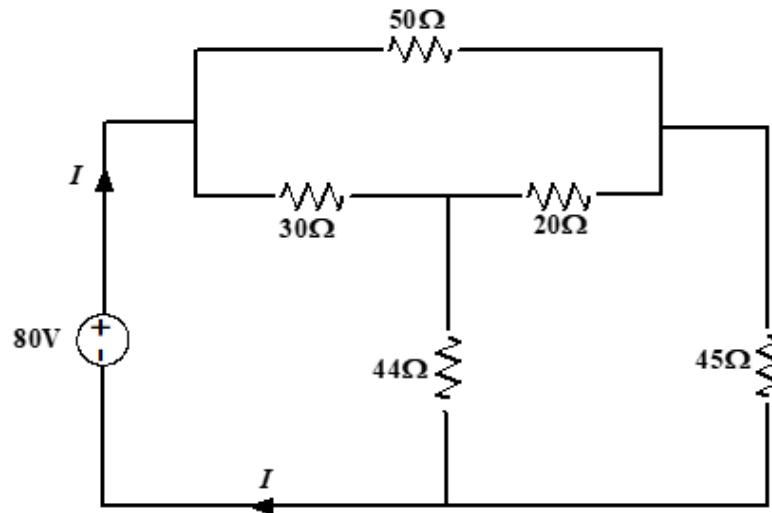


Fig.Q1A

- B) Find the average value, RMS value, peak factor and form factor for the waveform shown in Fig.Q1B (5)

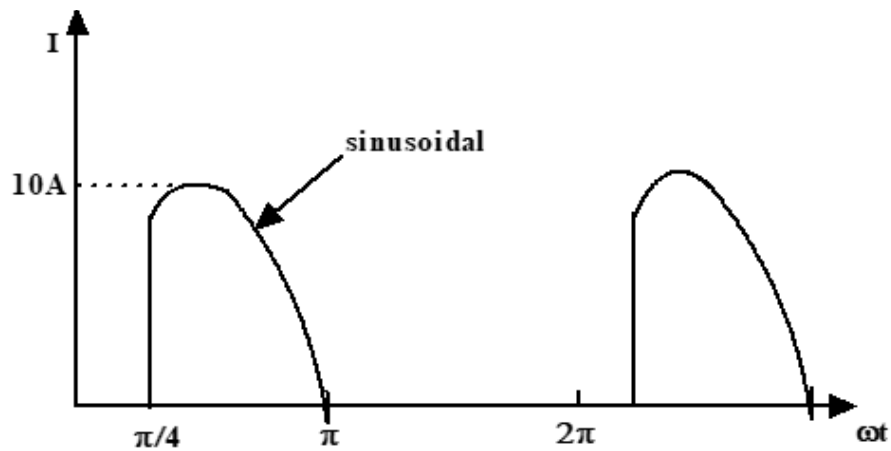


Fig.Q1B

C) Draw to scale a vector diagram showing the following voltages:

(2)

$$e_1 = 25 \sin \omega t, \quad e_2 = \sin \left(\omega t + \frac{\pi}{3} \right), \quad e_3 = 30 \cos \omega t, \quad \text{and} \quad e_4 = 20 \sin \left(\omega t - \frac{\pi}{4} \right)$$

Find the resultant and draw to scale a vector diagram showing all the voltages.

2) Derive the expression for instantaneous power and average power dissipated (5)
by a pure inductor in an AC circuit. Plot the waveforms for inductor voltage,
current and instantaneous power.

A) A series circuit has a resistance of 2Ω , an inductance of 0.25H , a variable (3)
capacitance, connected across a 230V , 50Hz supply. Calculate
(a) The value of the capacitance for resonance.
(b) The voltage across the inductor and the capacitor at resonance.
(c) The Q factor of the circuit

C) A single phase transformer has 500 primary and 1000 secondary turns. The (2)
net cross-sectional area of the core is 50cm^2 . If the primary winding is
connected to a 50Hz supply at 400V , calculate
(a) The peak flux density in the core
(b) The voltage induced in the secondary winding.

3) A supply of 200V , 50Hz is connected to a 20Ω resistor in series with a choke (5)
coil. The reading of the voltmeter across the resistor is 100V and across the
coil is 150V . Calculate
(a) The power factor of the circuit
(b) The power consumed in the resistance
(c) The power consumed in the coil.

B) A resistance of 30Ω is connected in series with an inductance of 0.25H (5)
across 230V , 50Hz supply. Find the
(a) Inductive reactance (b) Total impedance

(c) Current through the circuit (d) Voltage across resistance