

Question Paper

Exam Date & Time: 27-Jun-2022 (02:00 PM - 05:00 PM)



MANIPAL ACADEMY OF HIGHER EDUCATION

Manipal School of Information Sciences, Manipal
Second Semester Master of Engineering - ME (VLSI Design Degree Examination - June 2022)

Advanced VLSI Design [VLS 5201]

Marks: 100

Duration: 180 mins.

Monday, June 27, 2022

Answer all the questions.

- 1) What are the different ways of fabricating capacitors in CMOS VLSI process? Compare each of them. (TLO 1.1) (10)
- 2) With diagram, explain a basic current mirror using MOSFETs, taking into account the channel length modulation. (TLO 2.1) (10)
- 3) Design a current sink to sink a current of $10\mu\text{A}$. Estimate the minimum voltage across the current sink and the output resistance.
[Data: $V_{DD} = +5\text{V}$, $V_{SS} = 0\text{V}$, $L = 5\mu\text{m}$, $V_{GS} = 1.2\text{V}$, $V_{th} = 0.83\text{V}$, $\lambda = 0.06/\text{V}$, $K_n = 50\mu\text{A/V}^2$]
(TLO 2.1) (10)
- 4) With the help of a schematic diagram and a small-signal equivalent circuit, obtain the expression for the small-signal incremental voltage gain, A_v of a CMOS Common-Source amplifier with passive resistor load. (TLO 3.1) (10)
- 5) With the help of a small-signal equivalent circuit, obtain the expression for A_v of a CMOS Common-Gate amplifier with passive resistor load. Assume finite output impedance r_o and signal source impedance R_s . (TLO 3.1) (10)
- 6) Draw a neat schematic and explain the Thermal Voltage Referenced Self-Biasing circuit. (TLO 2.2) (10)
- 7) What is Common Mode Range (CMR) of a differential amplifier? Explain, with diagram, how do you measure it? (TLO 4.1) (10)
- 8) What are the advantages of *switched-capacitor* circuits? With the help of a simple diagram, explain a switched-capacitor resistor circuit. (TLO 5.2) (10)
- 9) With neat diagrams, explain Analog Multiplying Circuit using Squaring Circuit. (TLO 5.1) (10)
- 10) With the help of neat diagrams, explain the working of Cyclic DAC and Pipeline DAC. (TLO 6.2) (10)

-----End-----