

Question Paper

Exam Date & Time: 10-Dec-2022 (02:30 PM - 05:30 PM)



MANIPAL ACADEMY OF HIGHER EDUCATION

FIRST SEMESTER B.TECH END SEMESTER EXAMINATIONS, NOV 2018

DIGITAL ELECTRONICS [BME 2153]

Marks: 50

Duration: 180 mins.

A

Answer all the questions.

Section Duration: 180 mins

Instructions to Candidates: Answer ALL questions Missing data may be suitably assumed

- 1) Write the a) Min Terms b) Max Terms c) Standard SOP Form d) Minimal SOP e) Canonical POS (5)
Form f) Minimal POS;

A)


A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

for the given Truth Table.

- B) Discuss 4-bit Johnson's counter with the help of D flip flop and truth table. (3)
- C) Determine the grey code equivalent of the given binary number a) 1001 b) 1010. (2)
- 2) Illustrate the following using Active high and Active low decoder $F(A,B,C) = \sum m(0,2,3,7)$ and $G(A,B,C) = \sum m(1,4,6,7)$ (4)
- A) .
- B) Design a Full subtractor using 1:8 De-MUX (4)
- C) Describe 1 bit comparator with help of logic diagram and Truth table. (2)
- 3) Explain S-R latch using NOR gate with relevant logic diagram and Truth table. (4)

- A)
- B) Illustrate Master Slave J-K Flip flop using NAND gates. (4)
- C) Explain T flip flop with relevant logic diagram and Truth table. (2)
- 4) Determine the ASM chart (5)

A)

 

for the given state diagram.

- B) Explain Moore machine with help of block diagram and T Flip flop. (3)
- C) Summarize any two differences between Moore and Mealy machine. (2)
- 5) Design CMOS NAND gate with the relevant logic diagram and truth table. (4)
- A)
- B) Design TTL NAND gate with the relevant logic diagram and truth table. (4)
- C) Explain any two characteristics of digital logic family. (2)

-----End-----