

Question Paper

Exam Date & Time: 23-Jan-2023 (09:30 AM - 12:30 PM)



MANIPAL ACADEMY OF HIGHER EDUCATION

THIRD SEMESTER B.TECH MAKE-UP EXAMINATIONS, JAN-FEB 2023

ANALOG ELECTRONICS [BME 2151]

Marks: 50

Duration: 180 mins.


Answer all the questions.

Instructions to Candidates:

- (i) Answer ALL questions
- (ii) Missing data may be suitably assumed
- (iii) Draw neat diagrams wherever necessary

- 1) Devise R_B and R_C for a Silicon transistor circuit in common emitter configuration to produce $I_B = 36.36\mu A$, $V_{CEQ} = 14V$ and $I_{CQ} = 11.67mA$. Assume $V_{CC} = 14V$ and $V_{BE} = 8.7V$. (2)
- A)
- B) A common emitter amplifier employing Ge transistor is biased using voltage divider bias. The various circuit parameters are $V_{CC} = 16V$, $R_C = 3K\Omega$, $R_E = 2K\Omega$, $R_1 = 56K\Omega$, $R_2 = 20K\Omega$ and $\alpha = 0.985$. Determine: (4)
- i. Operating point
 - ii. Stability factor "S"
- C) Bias an NPN transistor in fixed bias configuration and derive an expression for stability factor "S". (4)
- 2) Determine V_{GSQ} , I_{DQ} and V_{DSQ} of the following circuit using graphical analysis. (4)


A)

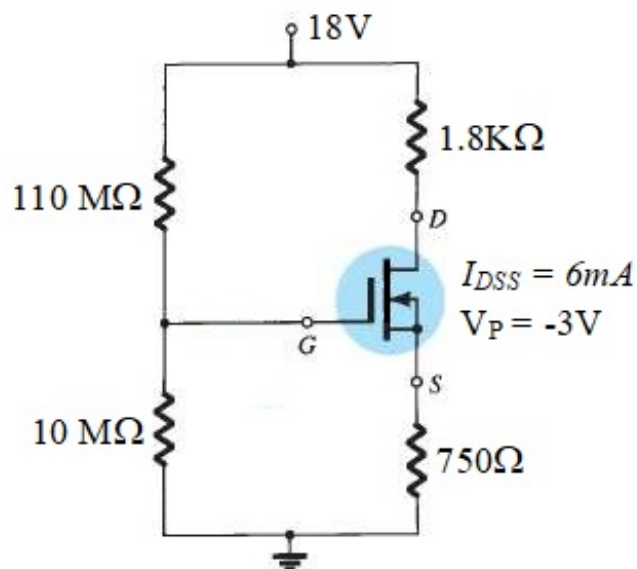

- B) Making use of a tuned circuit with two capacitors and one inductor, how do you generate sinusoidal (3)


frequency of 10 MHz? Illustrate.

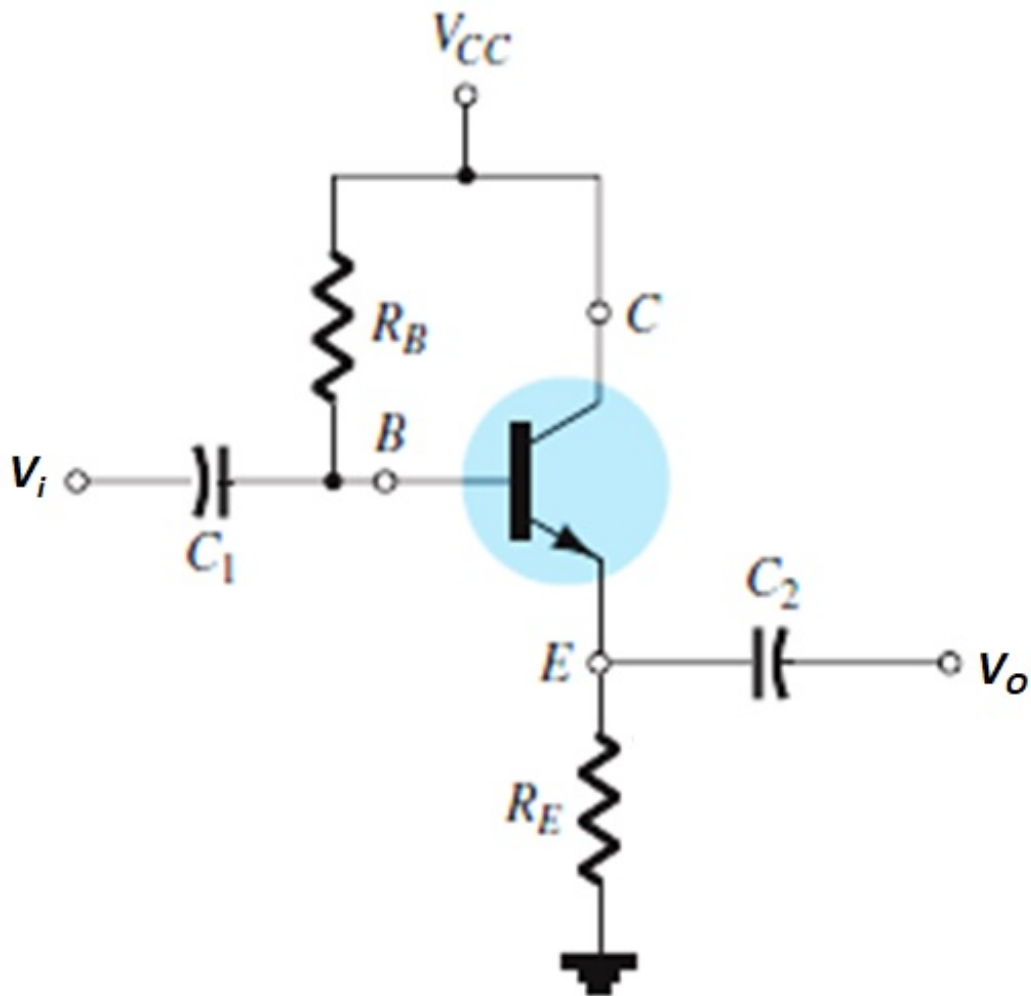- C) Draw the small signal model of the following circuit and analyse it for input and output impedances. (3)




- 3) Develop a small signal model of the following circuit and estimate input & output impedances and voltage gain. (4)

A)

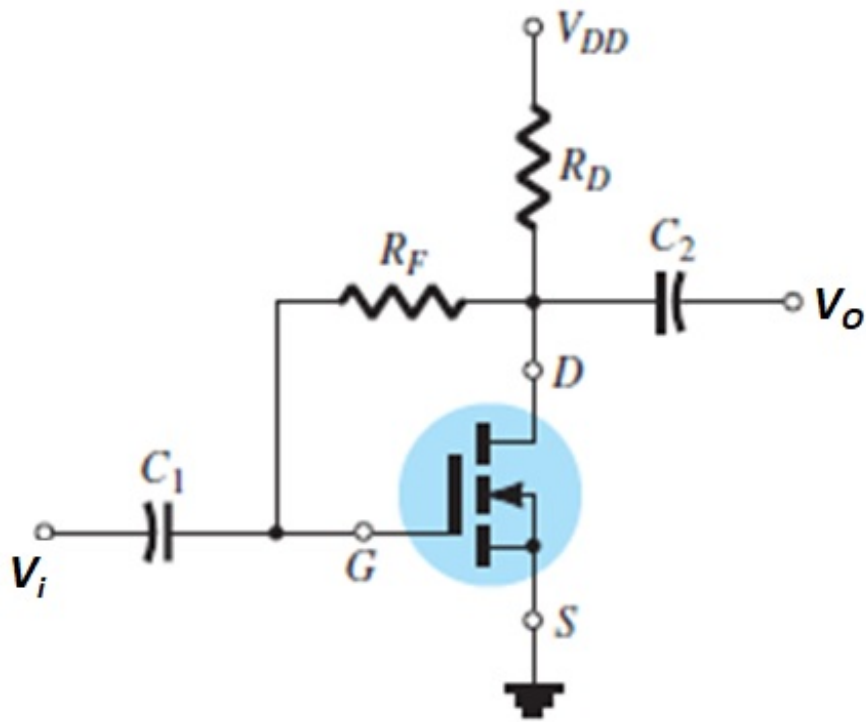

B) For the circuit shown below, having $I_{DQ} = 6.7\text{mA}$ and $V_{GSQ} = 12.5\text{V}$, and $g_{os} = 20\mu\text{S}$. (4)

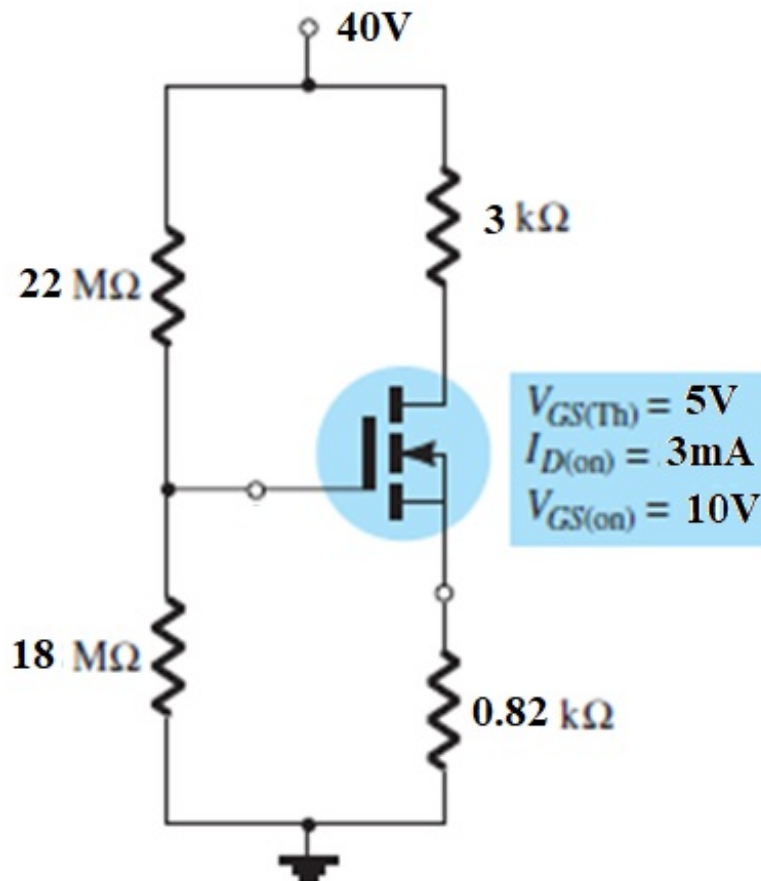1. Determine g_m
2. Find r_d
3. Calculate Z_i
4. Find Z_o with and without r_d
5. Find A_v with and without r_d




C) Write any two advantages and any two drawbacks of Class-A power amplifier. (2)

4) Draw circuit diagram and equivalent ac circuit (considering the loading effect of feedback network) of a BJT based voltage-series feedback amplifier, and derive input impedance and voltage gain with feedback. (4)

A)

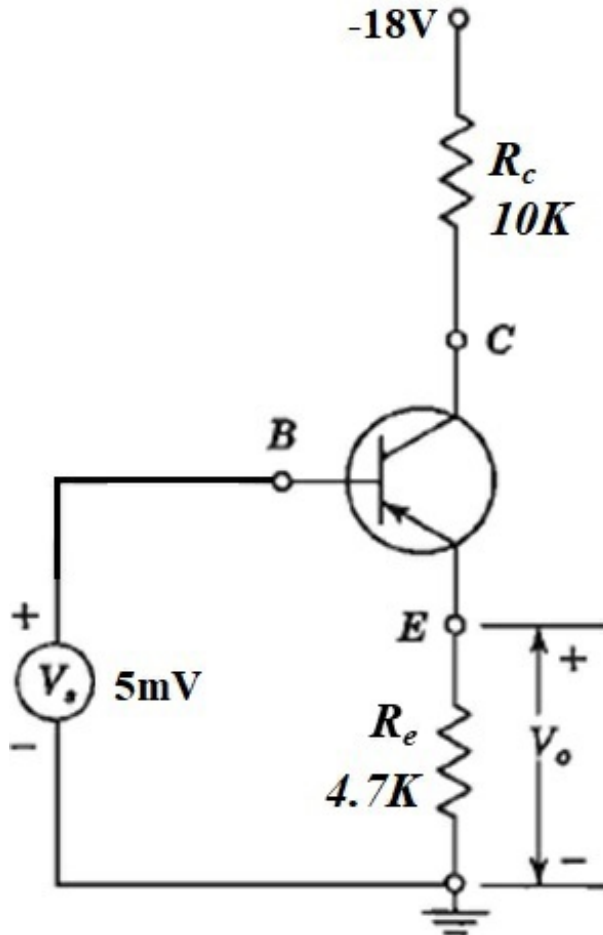B) Determine output voltage, input impedance and output impedance of the following circuit. Assume $V_S = 5\text{mV}$, $R_S = 0\Omega$, $h_{fe} = 50$, $h_{ie} = 1.1\text{K}\Omega$ and $h_{re} = h_{oe} = 0$. (4)




C) What is de-sensitivity in feedback amplifiers? How it affects the characteristics of amplifiers? (2)


5) Define and explain Barkhausen criteria. (2)

A)

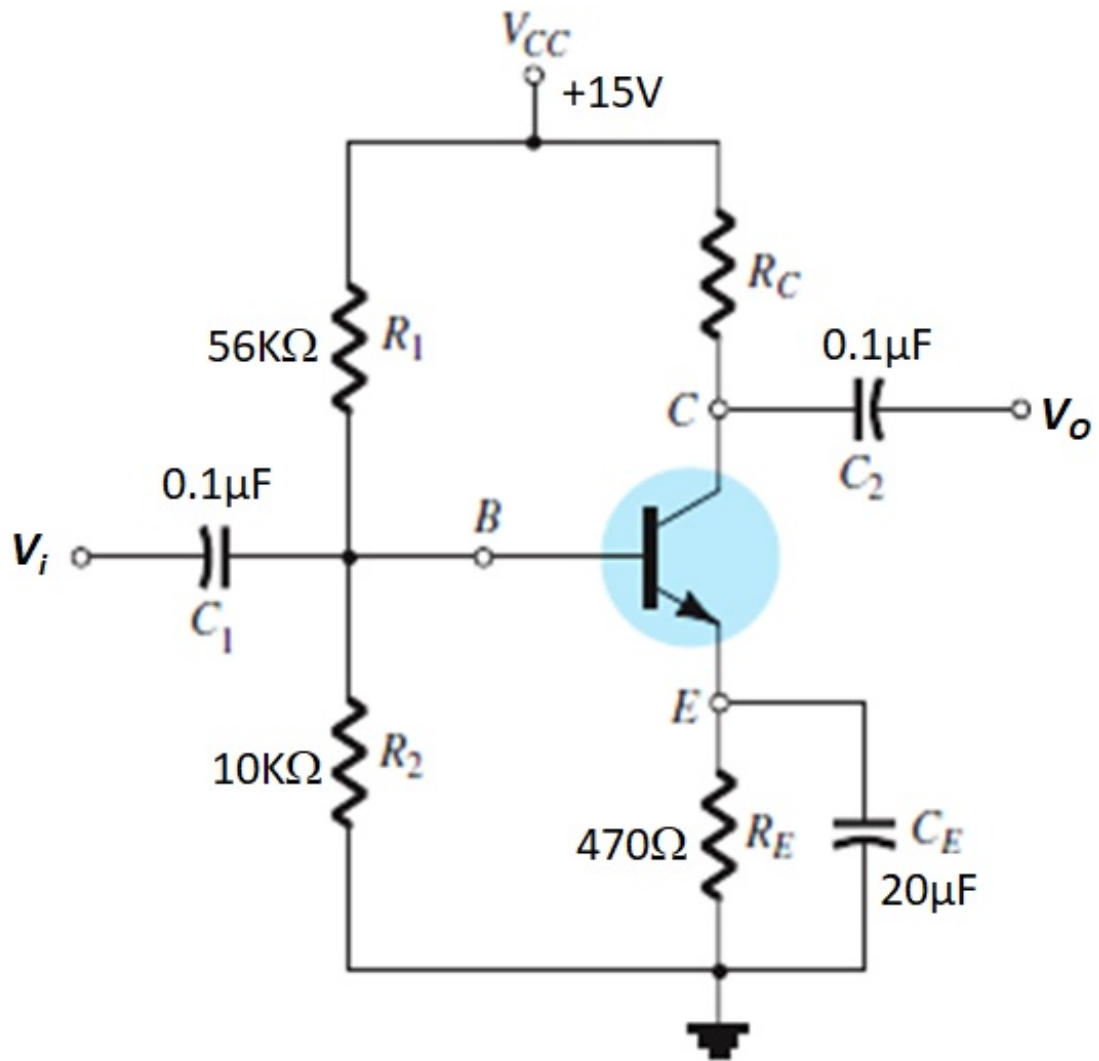B) Modify the following amplifier circuit in to a sinusoidal oscillator to produce sustained oscillations of frequency 5 KHz. Also determine the value of R_C required. Assume $r_o = \infty$ and Silicon transistor. (4)



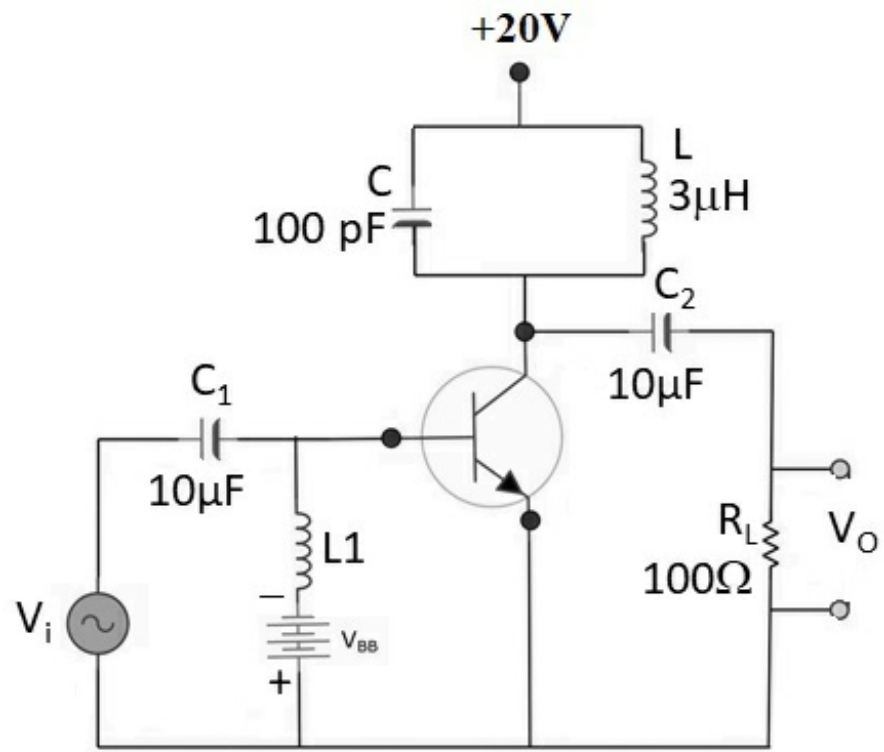- C) For the power amplifier shown below, the operating frequency is 3MHz and $V_{CE(\text{Sat})} = 0.3\text{V}$. (4)
Determine:
- A.C power output
 - D.C power drawn by the circuit
 - Efficiency, and
 - Conduction angle, if peak current is 500 mA



-----End-----