

# Question Paper

Exam Date & Time: 01-Feb-2023 (09:30 AM - 12:30 PM)



## MANIPAL ACADEMY OF HIGHER EDUCATION

THIRD SEMESTER B.TECH MAKE UP EXAMINATIONS, JAN-FEB 2023

NETWORK ANALYSIS [BME 2154]

Marks: 50

Duration: 180 mins.


A

Answer all the questions.


Instructions to Candidates: Answer ALL questions Missing data may be suitably assumed

- 1) For the network shown apply nodal analysis and calculate the current  $I$  in  $5\ \Omega$  resistor. (3)


A)

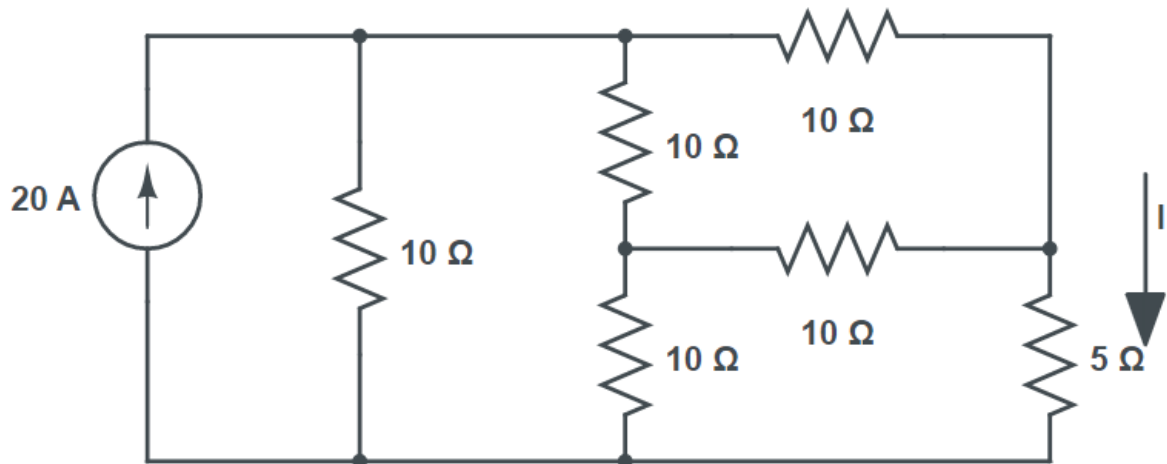

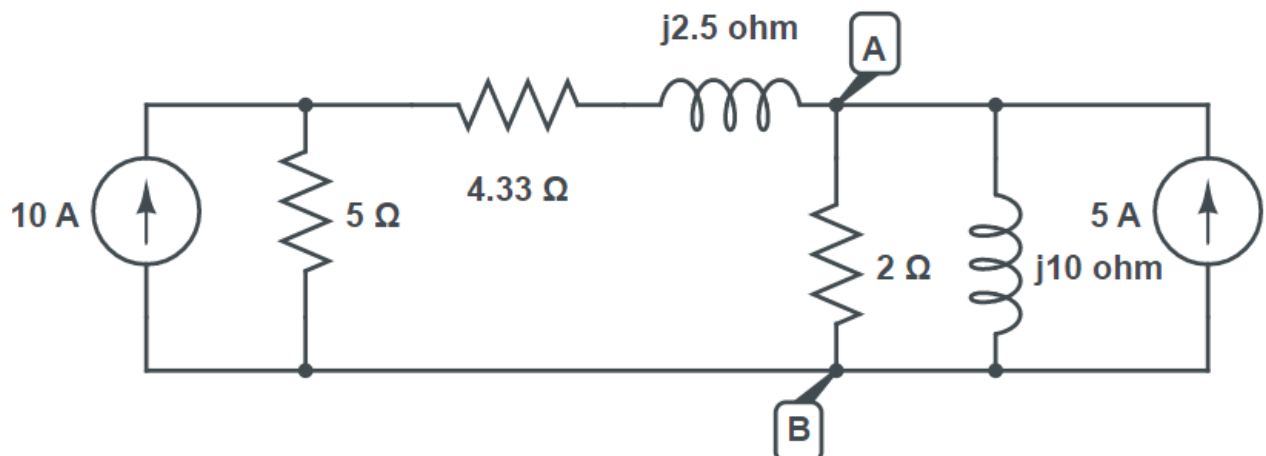- B) In the circuit shown apply superposition theorem and calculate voltage  $V_{AB}$  across  $2\ \Omega$  resistor. (3)




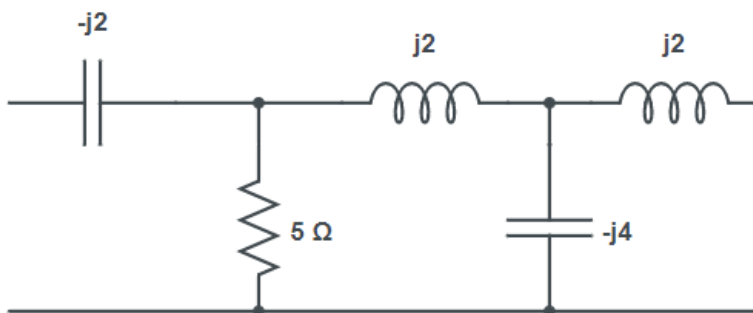- C) Obtain the star equivalent to the circuit shown. (4)





- 2) For the coupled circuit shown calculate the values of current and  $V_o$ . (4)

A)

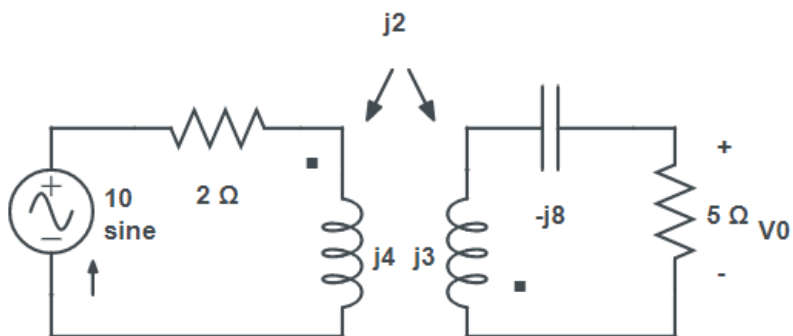

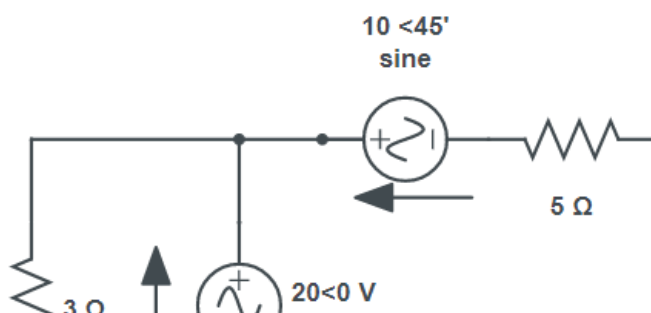- B) In the circuit shown the reactance and resistance associated with the load are varied. Determine  $Z_L$  for it to receive the maximum power and obtain the maximum power. (3)



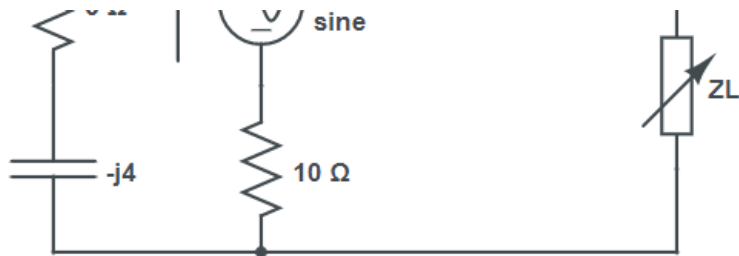


C) For a series RLC circuit  $V=2$  V,  $L=20$  mH,  $C=0.02$   $\mu$ F and  $R=20$   $\Omega$ . Calculate: (3)


- i. Resonant frequency
- ii. Q of the coil
- iii. Maximum current
- iv. Band width
- v. Half power frequencies
- vi. Voltage across elements at resonant.

3) For the network shown the switch is opened at  $t=0$ , calculate  $V$ ,  $dv/dt$  and  $d^2 v/dt^2$  at  $t=0^+$ . (3)

A)

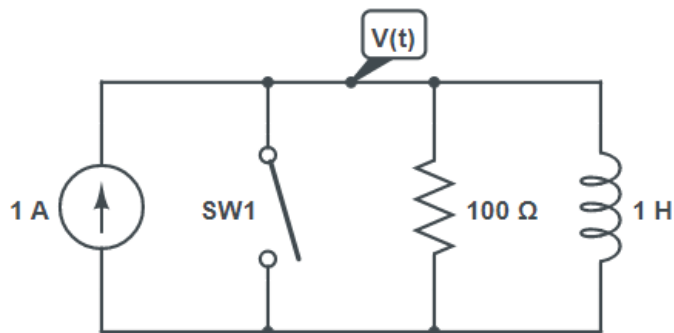

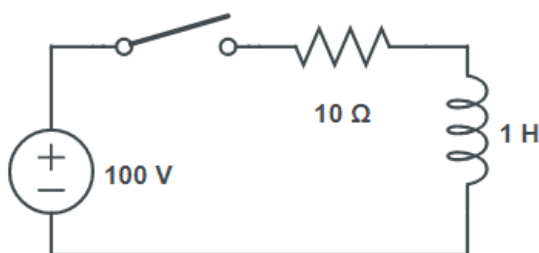B) For the circuit shown the switch is closed at  $t=0$  with initial zero current in inductor, calculate  $I$ ,  $di/dt$  and  $d^2 i/dt^2$  at  $t=0^+$ . (4)




C) Determine the step response of RL circuit using initial conditions. (3)

4) Derive the initial value and final value to: (4)

A)

$$F(s) = \frac{s^3 + 7s^2 + 5}{s(s^3 + 3s^2 + 4s + 2)}$$

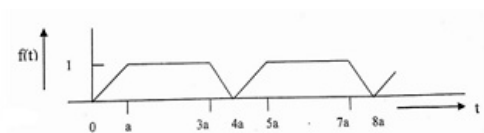
B) Determine the Laplace transform for the periodic waveform. (3)



C) Determine Laplace transform of  $f(t) = 1, \text{ for } t = 0 \text{ and } f(t) = 0, \text{ for } t \neq 0$ . (3)


5) For the circuit shown Obtain the Z parameters. (3)

A)

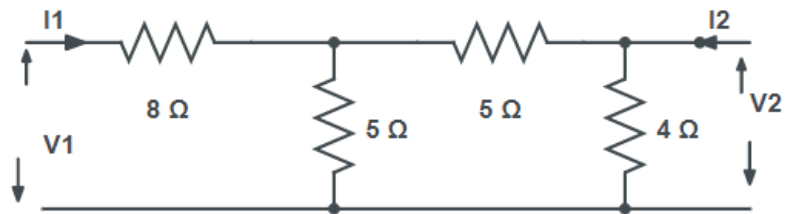

B) Derive the Y parameters in terms of Z parameters. (4)

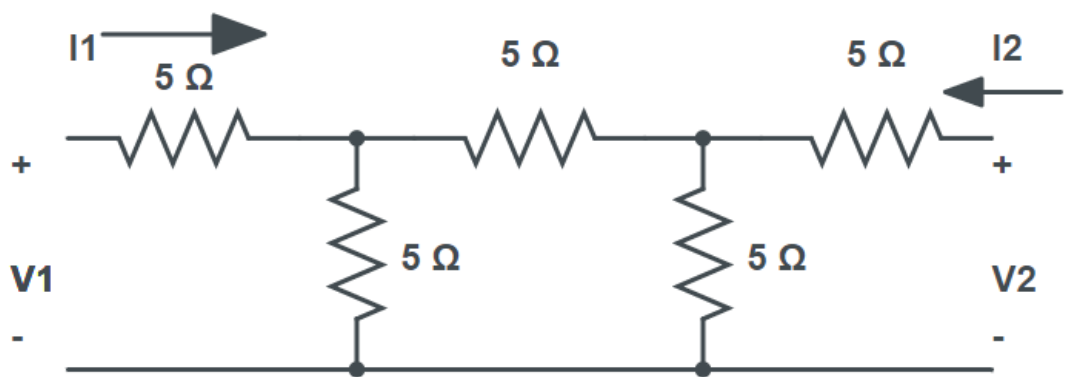C) Derive the expression of Y parameter. (3)



-----End-----