

Question Paper

Exam Date & Time: 13-Dec-2022 (02:30 PM - 05:30 PM)



MANIPAL ACADEMY OF HIGHER EDUCATION

THIRD SEMESTER B.TECH END SEMESTER EXAMINATIONS, DEC 2022

NETWORK ANALYSIS [BME 2154]

Marks: 50

Duration: 180 mins.


A

Answer all the questions.

Instructions to Candidates: Answer ALL questions Missing data may be suitably assumed


- 1) For the network shown apply source transformation and reduce the network with a single voltage source in series with a single resistance between the terminals AB. Clearly indicate each step in the process of transformation. (3)


A)

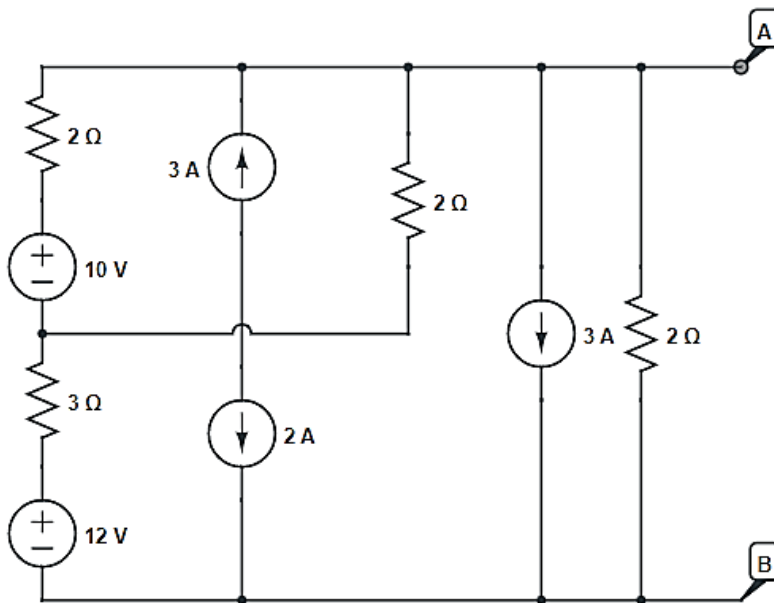


B)

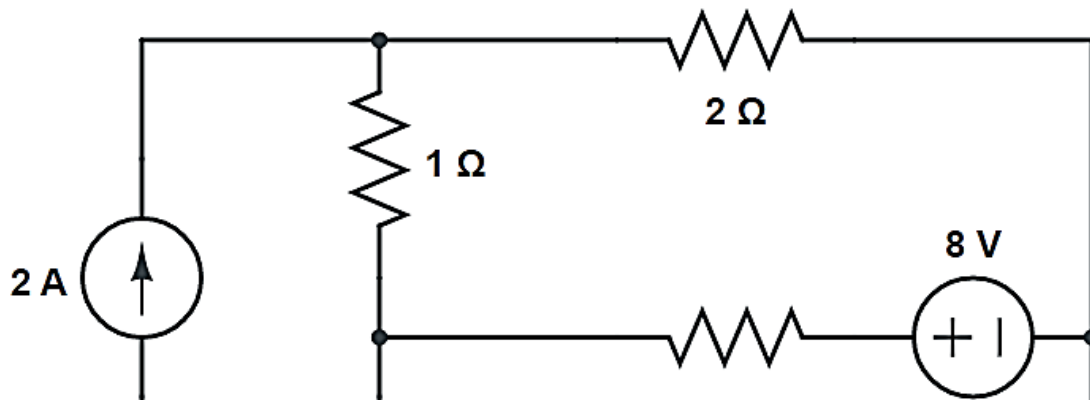- In the circuit shown calculate the power dissipated in each resistor, apply loop analysis to solve the network. (3)



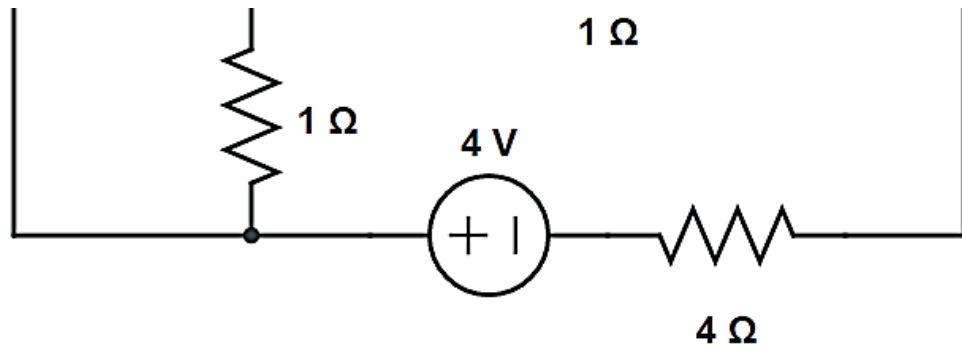


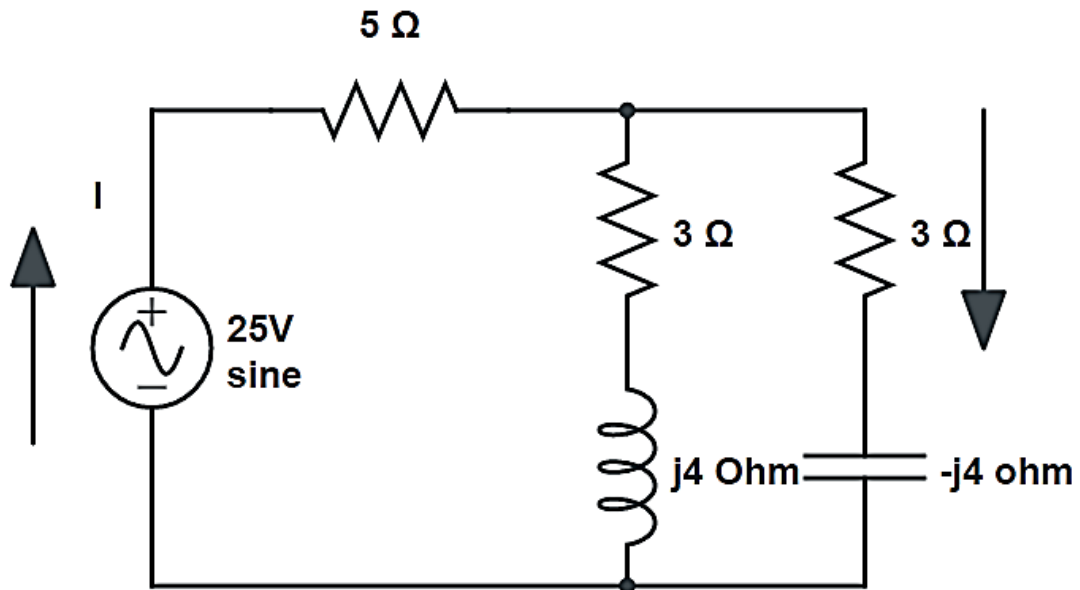C) Apply and verify the reciprocity theorem to calculate the current I in $(3-j4)$ ohm impedance. (4)





2) Apply and verify Millmans theorem, calculate the current I and power dissipated in 8 ohm resistor. (3)

A)

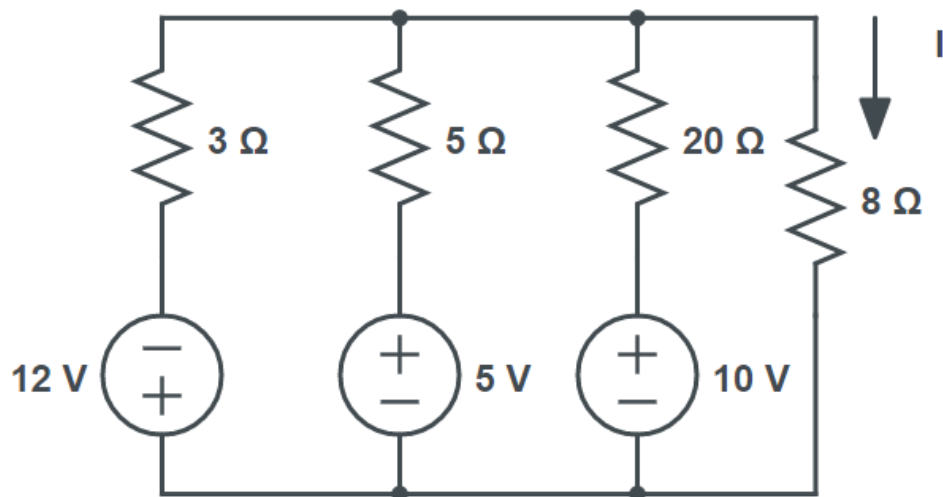


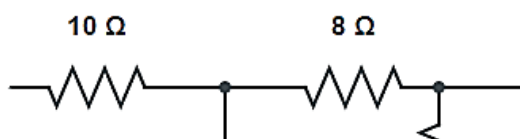B) Obtain the delta equivalent circuit by doing the transformation. (3)



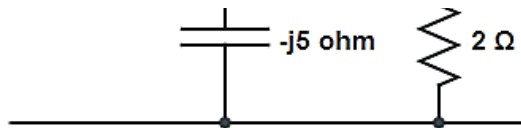


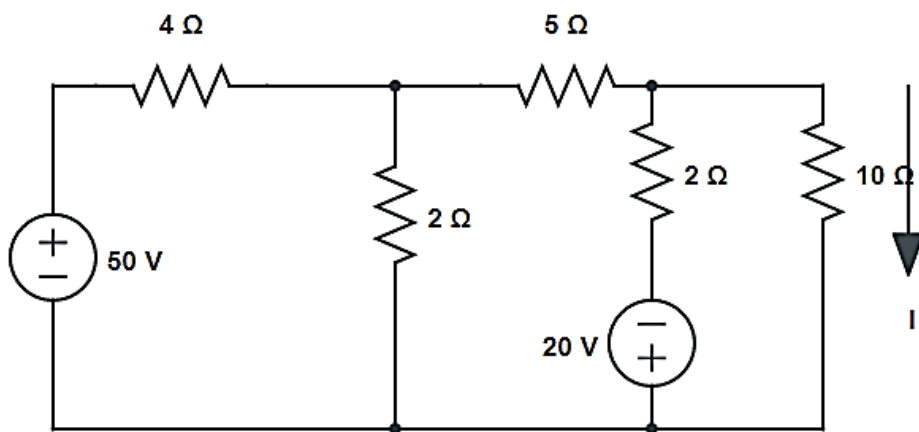- C) Apply Thevenins Theorem to calculate current I in 10 ohm resistor. (4)




- 3) For the network shown the switch is closed assuming all initial conditions as zero, calculate I , di/dt and d^2i/dt^2 at $t=0^+$. (3)

A)

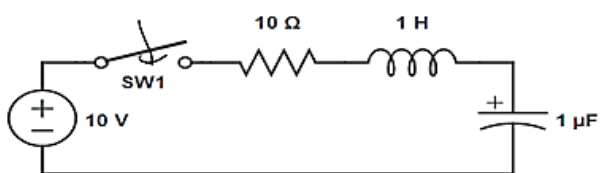

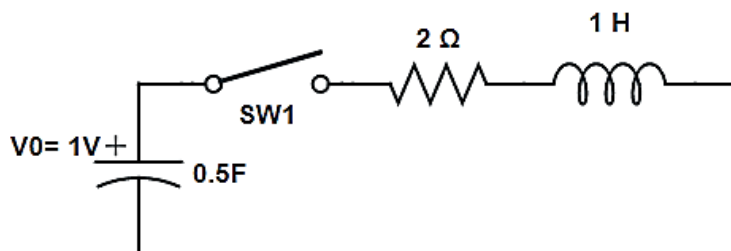- B) For the circuit shown the capacitor is initially charged to a voltage $V_0 = 1\text{ V}$ for $t < 0$. At $t=0$ switch is closed. Obtain the current $i(t)$ using Laplace transform and sketch the waveform. (4)




- C) State and prove Initial value and Final value theorem. (3)

Derive the inverse Laplace transform of

$$F(s) = \frac{3s}{s^2 + 3s + 2}$$

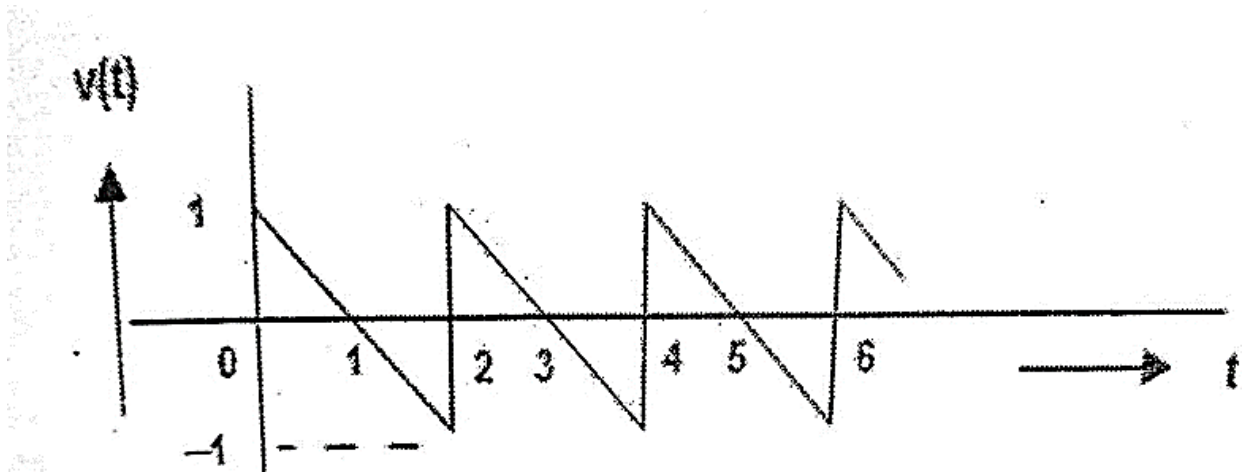
- A) (4)
- B) Determine the Laplace transform for the periodic waveform. (4)



- C) Determine Laplace transform of $f(t) = \sin wt$. (3)

- 5) For the circuit shown obtain the Z parameters. (3)

A)

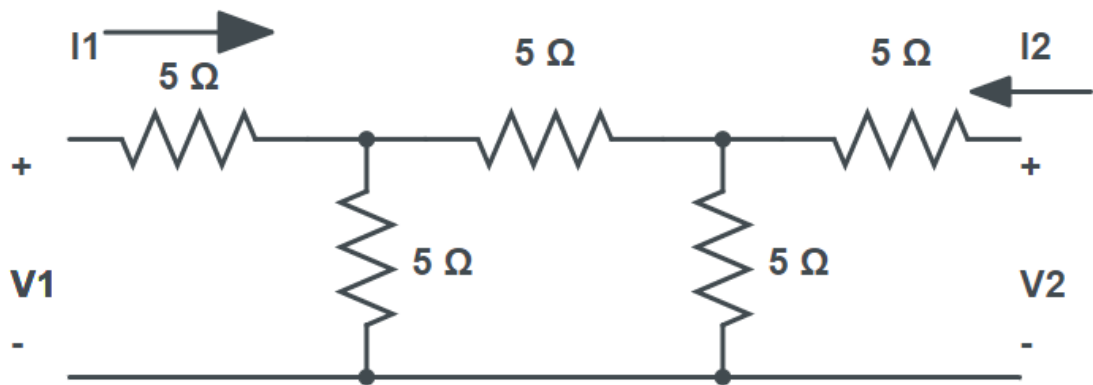

- B) Derive and represent the equivalent circuit of Y parameters. (4)

- C) Derive the expression of $G_{12}(s) = V_2(s)/V_1(s)$. (3)

