

Question Paper

Exam Date & Time: 13-Dec-2022 (02:30 PM - 05:30 PM)



MANIPAL ACADEMY OF HIGHER EDUCATION

THIRD SEMESTER B.TECH. (ELECTRONICS AND COMMUNICATION ENGINEERING) EXAMINATIONS - DECEMBER 2022
SUBJECT : ECE 2154 - NETWORK ANALYSIS

Marks: 50

Duration: 180 mins.

Answer all the questions.

- 1A) Consider the circuit of Figure. 1A. (4)
- Determine the current in the load resistor, R_L using the Superposition theorem.
 - Verify that the superposition theorem does not apply to power.

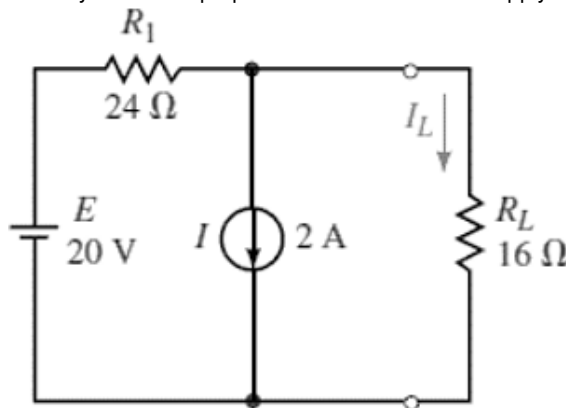


Figure. 1A

- 1B) Convert the voltage source of Figure 1B. into a current source and verify that the current, I_L , through the load is the (3)
same for each source.


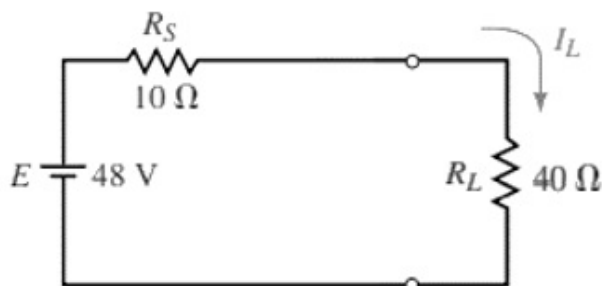


Figure 1B

- 1C) (3)

For the network shown in Figure 1C., Find V_1 , V_2 , V_3 and V_4 .

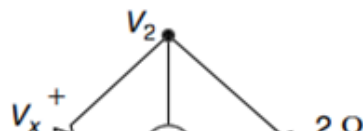

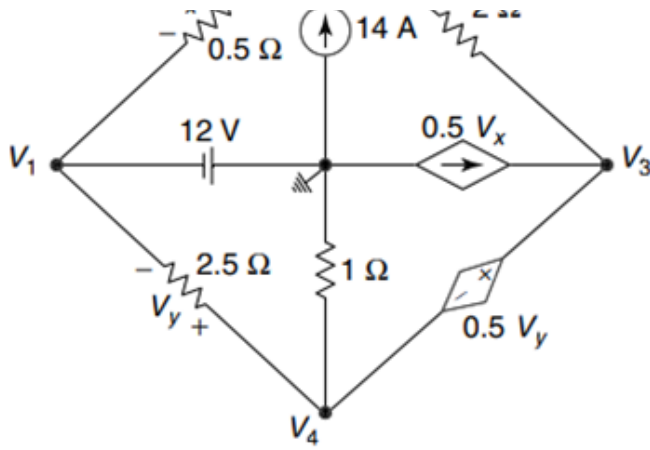


Figure 1C

- 2A) In the network shown in Figure 2A, the switch is closed at $t = 0$, with zero capacitor voltage and zero inductor current. (4)
Solve for v_L , v_2 and dv_2/dt at $t = 0^+$.


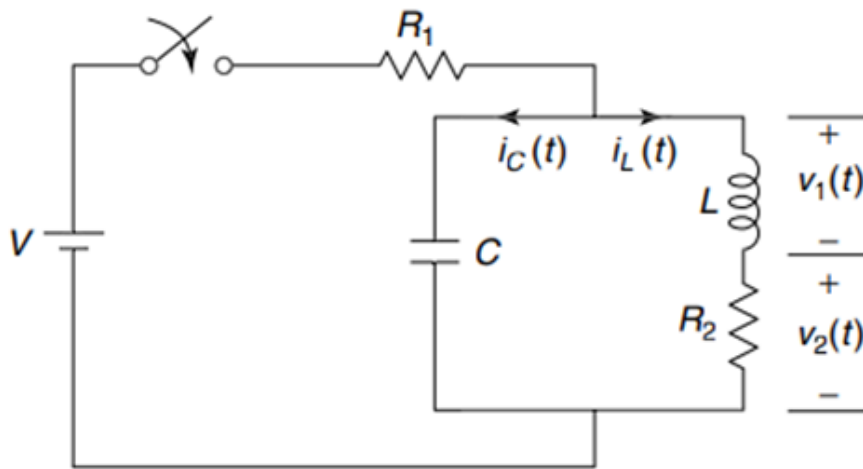


Figure 2A

- 2B) In the network shown in Figure 2B, a steady state is reached with the switch open. At $t = 0$, the switch is closed. (3)
For the element values given, determine the values of

$V_a(0^-)$, $V_a(0^+)$, $V_b(0^-)$ and $V_b(0^+)$.

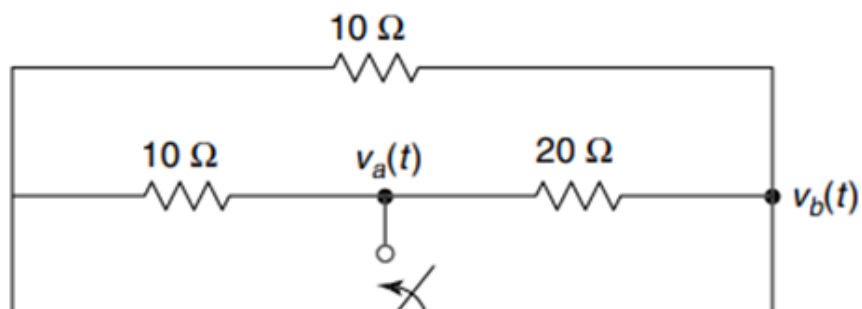

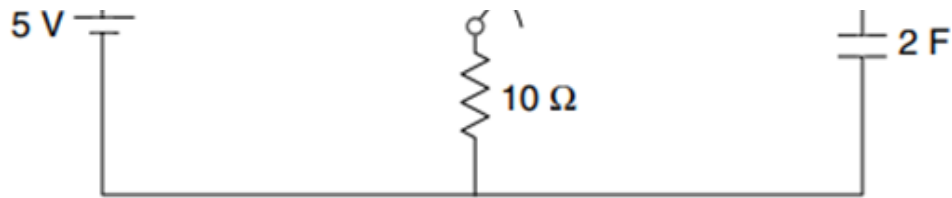


Figure 2B

- 2C) In the network shown in Figure 2C, find $v_o(t)$ if $i(0) = 5\text{ A}$ and $v(t) = 0$. (3)

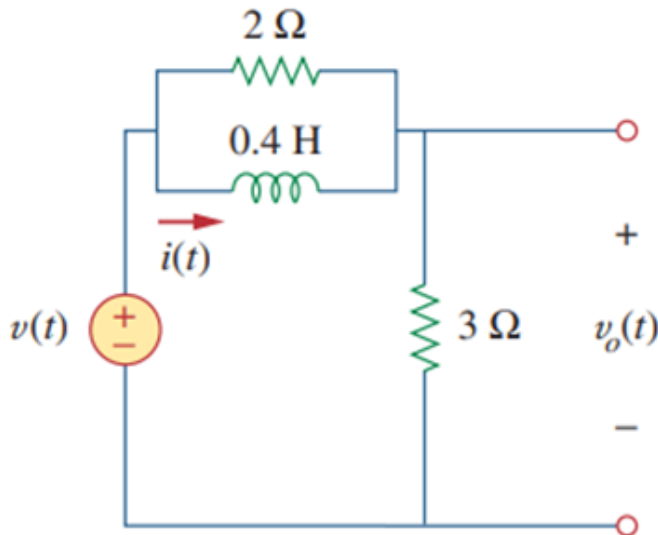


Figure 2C

- 3A) A symmetrical square wave of amplitude $\pm 5\text{V}$ and frequency 3kHz is impressed on an RC low pass circuit. If $R = 6\text{k}\Omega$ and $C = 0.2\mu\text{F}$, calculate and plot the steady state output with respect to time. (4)
- 3B) A pulse of 10V amplitude and duration 1ms is applied to a high pass RC circuit with $R = 20\text{k}\Omega$ and $C = 0.7\mu\text{F}$. Plot the output waveform to scale and calculate the percent tilt in the output. (3)
- 3C) A symmetrical square wave whose average value is zero has a peak-to-peak amplitude of 25V and a period of $4\mu\text{s}$. This waveform is applied to a circuit whose upper 3dB frequency is $1/2\pi\text{ MHz}$. Calculate and sketch the steady state output waveform. In particular what is the peak to peak output amplitude. (3)
- 4A) For the network shown in the Fig. 4A, the switch is closed at $t = 0$. Determine the current $i(t)$ assuming zero initial conditions using Laplace Transform. (4)

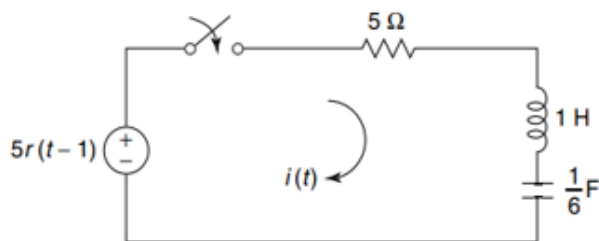


Fig. 4A

- 4B) For the network shown in the Fig. 4B, find the response $v_o(t)$ using Laplace Transform. (3)

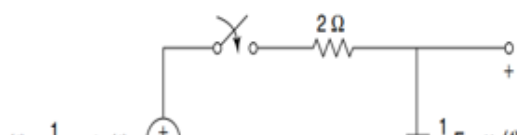




Fig. 4B

- 4C) For the network shown in the Fig. 4C, determine the current $i(t)$ when the switch is closed at $t=0$ with zero initial conditions using Laplace Transform. (3)

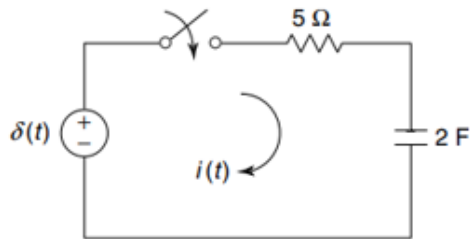


Fig. 4C

- 5A) Find the y parameters for the circuit shown in Figure 5A. (4)

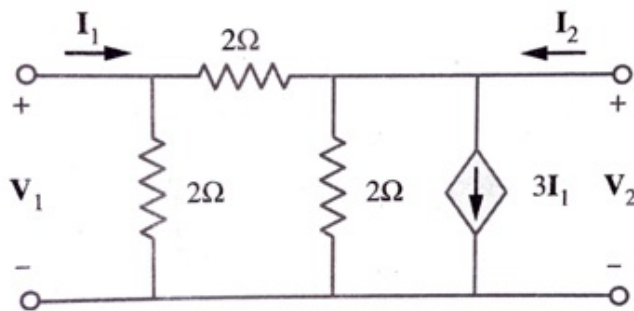


Figure 5A

- 5B) Find the network function $\frac{V_2}{V_1}$ for the network shown in Figure 5B. (3)

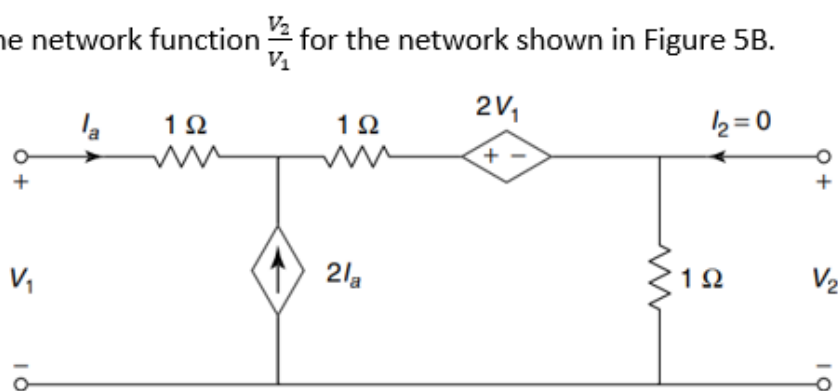


Figure 5B

- 5C) Derive the expression for z parameters in terms of y parameters. (3)

-----End-----