



Time: 3 Hrs.


Date: January 2023

Max. Marks: 50

Instructions to Candidates:


- ❖ Answer **ALL** the questions.
- ❖ Missing data may be suitably assumed.

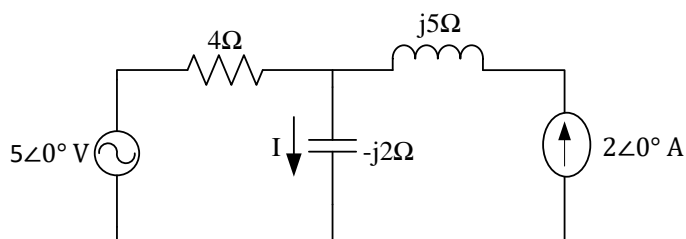1A. Determine the current 'I' using superposition theorem



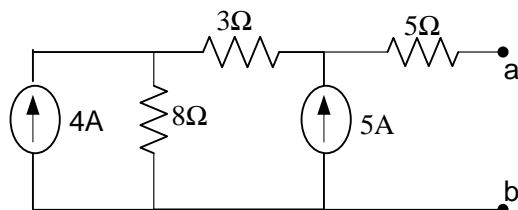
(03)

1B. Find the Norton's equivalent circuit for the circuit below



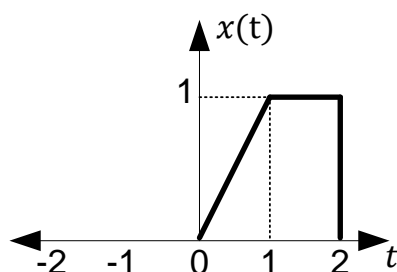
(03)

1C. For the signal $x(t)$ shown, sketch the signal $2x\left(\frac{t}{2} - 1\right)$



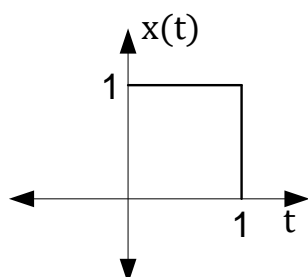(04)

2A. Find the even and odd component of signal $X(t)$.




(03)

- 2B.** Find the fundamental period of the signal given below.


$$x(t) = \sin \frac{6\pi}{7} t + 3\sin 4\pi t + 2\sin \frac{6\pi}{5} t \quad (02)$$

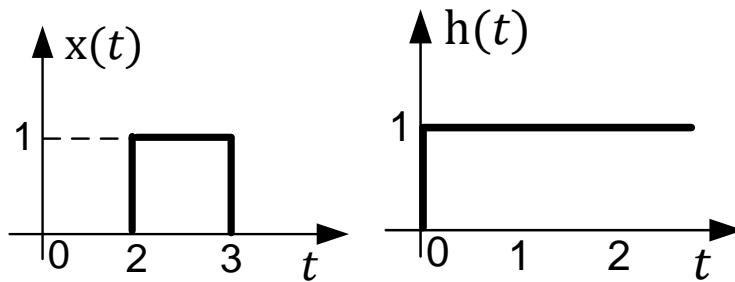- 2C.** Determine the output response $y(t)$, when the impulse response $h(t)$ for an input $x(t)$ is as shown in Fig.



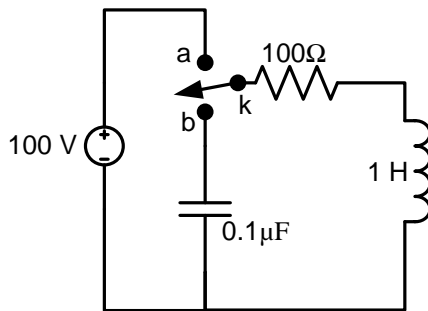
(05)

- 3A.** In the network shown, the switch 'K' is changed from position a to b at $t=0$. Solve for i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t=0^+$ if $R=100\ \Omega$, $L=1\text{ H}$, $C=0.1\ \mu\text{F}$ and $V=100\text{ V}$.



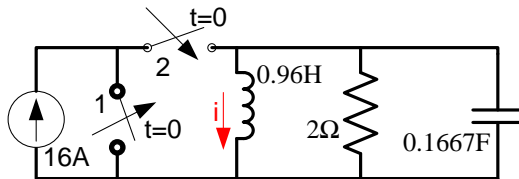(03)

- 3B.** Switch 1 and switch 2 operates synchronously and is complementary (s1 on \rightarrow s2 off and s2 on \rightarrow s1 off). Switch1 has been closed for a long time and at $t=0$ s, switch 1 is open, Find $i(t)$ for $t>0$



(04)

- 3C.** In the network shown, switch is changed from A to B at $t=0$. Find the current through the capacitor using Laplace Transform method


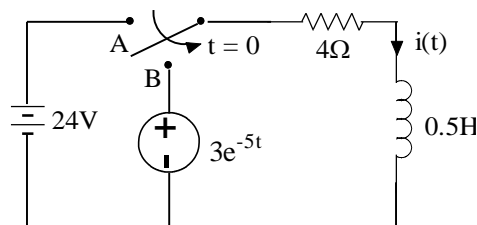


Fig. 3A


(03)

- 4A.** Write the Trigonometric Fourier Series of the waveform shown. Also, plot the magnitude and phase spectra.


(05)

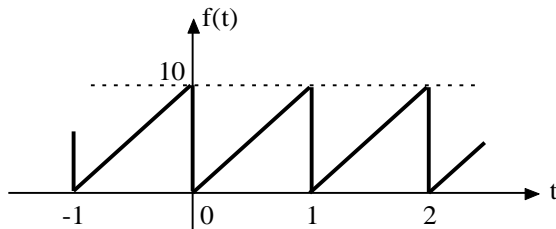

- 4B.** Consider a periodic signal $x(t)$ with $\omega_o = 2\pi$ and $a_o = 1$; $a_1 = a_{-1} = \frac{1}{4}$; $a_2 = a_{-2} = \frac{1}{2}$; $a_3 = a_{-3} = \frac{1}{3}$; Give the Fourier series representation in exponential and also in trigonometric form. **(03)**
- 4C.** Obtain the Fourier transform of signal $x(t) = e^{-at}u(t)$; $a > 0$ **(02)**
- 5A.** Derive the h-parameters of the network given below.

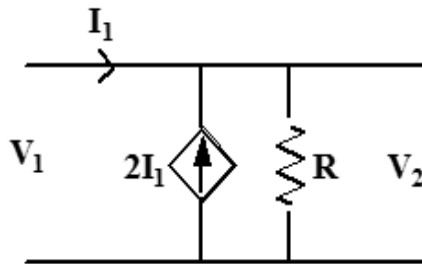

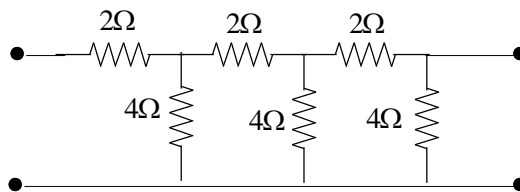- 5B.** A two port network is defined by the parameters: $Y_{21} = 6$, $Y_{22} = 8$, $h_{11} = 5$, $h_{12} = 2$. Find the T parameters. **(03)**
- 5C.** Decompose the network shown into two, 2 port networks connected in cascade and hence find the overall Z parameters.



(05)