

Question Paper

Exam Date & Time: 22-May-2023 (02:30 PM - 05:30 PM)



MANIPAL ACADEMY OF HIGHER EDUCATION

FOURTH SEMESTER B.TECH. (ELECTRONICS AND COMMUNICATION ENGINEERING) EXAMINATIONS - MAY/JUNE
2023

SUBJECT: ECE 2253/ ECE_2253 - LINEAR INTEGRATED CIRCUITS

Marks: 50


Duration: 180 mins.

Answer all the questions.


Missing data may be suitably assumed.

Assume Opamp saturation voltage to be $\pm 12V$.

 
- 1A) Obtain expression for output voltage of the circuit shown below. Also if V_1 is varied from 0 to 10 V, (5)
keeping V_2, V_3, V_4 at 1V, sketch output voltage with respect to input voltage.



 
- 1B) In the Circuit shown in figure, an ideal Zener diode with breakdown voltage of 4.7V is used. Plot the (3)
output voltage versus the input voltage. Input voltage varies from 0 to 15 V.



 
- 1C) Circuit shown below is voltage to current converter. Given $V_1 = 2V$, $R_1 = 1k\Omega$ maximum output (2)
current through the op-amp is $\pm 10mA$. Determine (i) I_L (ii) Maximum value of R_L that can be used.
(iii) Maximum value of V_1 that can be used, given $R_1 = 1k\Omega$ and $R_L = 0$.



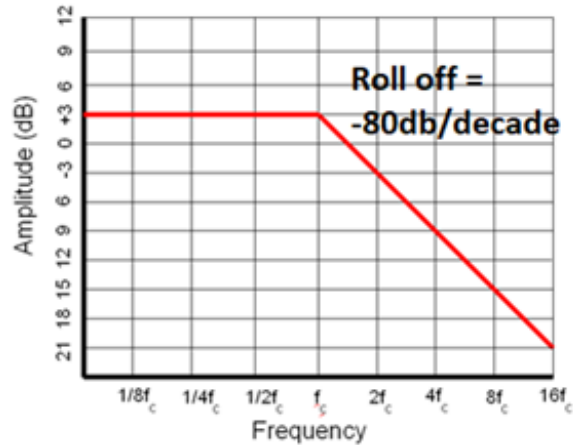
- 2A) Design a Butterworth LPF with cut-off frequency, $f_c = 1\text{kHz}$ for the frequency response shown in Fig. Q2A. (5)



 - 2B) Analyse the temperature compensated logarithmic amplifier with a neat diagram and obtain the output expression. (3)
- 2C) For the circuit shown in Fig. Q2C. given a silicon diode, and $V_{\text{Sat}} = \pm 13\text{V}$. Draw the transfer characteristics. (2)




 - 3A) i) By marking all the voltage levels and time intervals, plot V_O as a function of time for the circuit shown in figure. (5)
- ii) What would be the effect on waveform, if $2\text{k}\Omega$ resistor is replaced by a $1\text{k}\Omega$ fixed resistor in series with a $1\text{k}\Omega$ potentiometer and the latter is varied from minimum to maximum value.



3B) Design a 555 timer based circuit to give a square waveform of 1kHz frequency and duty cycle adjustable between 25% to 75%. (3)

 3C) For the circuit of shown, if V_I is a triangular waveform defined as in figure, by marking all the time intervals and voltage levels, plot V_O as a function of time. (2)



4A) Design a astable multivibrator shown in Fig. Q4A having with frequency 1KHz. Assume $C = 0.1\mu F$, also find the duty cycle D. (5)

 


Fig. Q4A

4B) Draw the internal diagram of VCO and explain its working. (3)

4C) With a neat block diagram explain the working of frequency multiplier using PLL. (2)

5A) Design a 4-bit R - 2R DAC to result in an output voltage of 0.5V when the input is 0001. Use V_{REF} of -5V and resistor connected to output terminal of 1kΩ value. What would be the output voltage when the input is 1111. Plot V_O if the input is coming from a 4-bit Johnson counter driven with a 1kHz clock signal. (5)

5B) Explain the working principle of a SAR ADC with an example. (3)

5C) In a 4 bit ADC, if the clock frequency is 1kHz, determine the minimum and maximum conversion (2)

time, if the ADC is (i) counter type (ii) successive approximation type.

-----End-----