

# Question Paper

Exam Date & Time: 24-May-2023 (02:30 PM - 05:30 PM)



## MANIPAL ACADEMY OF HIGHER EDUCATION

FOURTH SEMESTER B.TECH END SEMESTER EXAMINATIONS, MAY 2023

### DIGITAL SYSTEM DESIGN [ICE 2251]

Marks: 50

Duration: 180 mins.

A

Answer all the questions.

Instructions to Candidates: Answer ALL questions Missing data may be suitably assumed

- 1) Distinguish between top-down and bottom-up design methodology with an example of a 4-Bit ripple carry counter. [CO2, PO1,2,3,12, BL2] (3)
- A)
- B) Use structural modelling technique to implement a full adder using two half adders. [CO3, PO1,2,3, BL3] (4)
- C) Based on the choice of the system user, one of the following four options is implemented, model the system using dataflow method and write a brief note explaining your logic. [CO3, PO2,3, BL3] (3)

Option	Action
1	Rotate half step Clockwise (CW)
2	Rotate half step Counter Clockwise (CCW)
3	Rotate full step Clockwise (CW)
4	Rotate full step Counter Clockwise (CCW)

- 2) Differentiate among any four different programming technologies that are used to make the FPGAs field programmable. [CO4, PO2,3, BL2] (4)
- A)
- B) Given inputs are:  $a = 4'b1010$ ,  $b = 4'b1111$ . What would be the output in the following cases? (4)
- i.  $a \& b$  ii)  $a \&\& b$  iii)  $a \& a$  iv)  $a \gg 1$
- v.  $a \ggg 1$  vi)  $y = \{2\{a\}\}$  vii)  $a \wedge b$  viii)  $z = \{a, b\}$
- [CO3, PO1,3,12, BL3]
- C) What is the difference between the following two lines of Verilog code? (2)
- $\#5 a = b;$
- $a = \#5 b;$  [CO3, PO1,2,3, BL3]
- 3) Implement a synchronous machine in Verilog that detects two successive bursts of logic 1 followed by two successive bursts of logic 0. Draw a timing diagram for the same, showing inputs, state transitions, and sequence detection. [CO3, PO1,2,3,12, BL4] (5)
- A)

- B) Write a Verilog code that implements the following operation depending on the input select S1 and S0. Given A and B are 4 bit inputs. (3)

S1	S0	Operation
0	0	1's complement of A
0	1	2's complement of B
1	0	reversing the bit position of A
1	1	reversing the bit position of B


[CO3, PO1,2,12, BL3]

- C) Differentiate between tasks and functions in Verilog. [CO4, PO1,2,3,12, BL2] (2)

- 4) Draw a neat block diagram of a Mealy machine. [CO3, PO1,2,3,12, BL2] (2)

A)

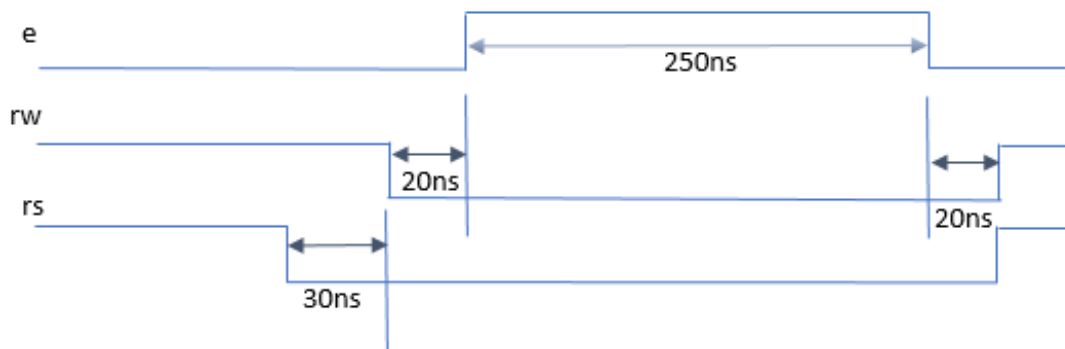- B) Design a digital system to generate the following waveform. Assume a system clock with period 10ns. [CO3, PO1,2,3,12, BL4] (5)



- C) Implement a UDP for a level-sensitive latch with clear. [CO3, PO1,2, BL3] (3)

- 5) Compare sequential and parallel blocks with appropriate examples. [CO4, PO1,3, BL3] (3)

A)


- B) A full subtractor has three 1-bit inputs, x, y, and z (previous borrow), and two 1-bit outputs D(Difference) and B(Borrow). The logic equations are: (4)

$$D = \bar{x}\bar{y}z + \bar{x}y\bar{z} + x\bar{y}\bar{z} + xyz$$

$$B = \bar{x}y + \bar{x}z + yz$$

Write Verilog description using dataflow modeling. Instantiate the subtractor module inside a stimulus block and test all possible combinations of inputs x, y, and z. [CO4, PO1,2, BL3]

 - C) Develop the test vectors to test the logic circuit below for all stuck at faults. [CO5, PO1,2,12 BL4] (3)



-----End-----