

Question Paper

Exam Date & Time: 07-Dec-2023 (09:30 AM - 12:30 PM)



MANIPAL ACADEMY OF HIGHER EDUCATION

THIRD SEMESTER B.TECH. DEGREE EXAMINATIONS - NOVEMBER / DECEMBER 2023
SUBJECT: CSE 2123- DIGITAL SYSTEM DESIGN


Marks: 50

Duration: 180 mins.

Answer all the questions.

Missing data may be suitably assumed.

 
- 1A) For the following state diagram, derive the expressions required for the synchronous sequential circuit design using JK flip-flops. (5)




- 1B) Make use of functional decomposition to find the minimum-cost circuit for the function $f(x_1, x_2, x_3, x_4) = \sum m(4, 7, 9, 10, 12, 13, 14, 15)$. Assume that the input variables are available in uncomplemented form only. (3)
- 1C) Demonstrate SR latch (basic Flip Flop circuit) using NAND gates with its function table. (2)
- 2A) It is required to develop a system to swap the contents of two n-bit registers. Assume that a temporary register is available to assist swapping. Adopt state table approach to design control circuit. Control circuit has two inputs clock and w. The swapping process is initiated when w=1, and on completion the control circuit asserts a signal Done to 1. (5)
- i) Derive the expression for the outputs of control circuit.
ii) Develop bus architecture of the system based on tri-state buffer.
- 2B) A combinational circuit receives two single-bit inputs A and B and produces a single-bit output $Y = F1 \oplus F2$. The Boolean functions F1 and F2 are as given below and are implemented using a decoder and OR gates. Design a minimal circuit for Y using only one decoder, one 2:1 multiplexer, and OR gates. (3)
- $F1(A, B) = \sum m(2, 3)$

$$F2(A, B) = \sum m(0,1,3)$$

 - 2C) Construct JK Flip Flop from D Flip Flop (2)
- 3A) Design the synchronous counter with the following repeated binary sequence: 0, 1, 2, 4, 6. Use D flip-flops. Check if it is self-correcting or not. (5)
- 3B) Analyze the following state diagram and perform the state reduction. (3)



- 3C) Distinguish between Moore and Mealy models of sequential circuit design. (2)
- 4A) Since a computer has many registers, paths must be provided to transfer information from one register to another. An efficient scheme for transferring the information between registers in a multiple-register configuration is a common bus system. Design a 4-bit common bus system for 4-registers of 4-bits each using multiplexers. (5)
- 4B) Design 3-bit Johnson counter by implementing the following steps. (3)
 a) Draw the state-transition diagram.
 b) Construct state table using T flip-flops.
 c) Design the Counter.
- 4C) Design NAND gate using CMOS technology. (2)
- 5A) Draw the state table and design the synchronous sequential circuit for the following state diagram using JK FF: (4)

 

- 5B) Design a combinational unit that can act as adder and subtractor for two 4-bit numbers. Provide suitable explanation. (4)
- 5C) Design a 4-bit ring counter using D flip-flops. (2)

-----End-----