Reg. No.



III SEMESTER B.TECH. (ELECTRICAL & ELECTRONICS ENGINEERING) END SEMESTER EXAMINATIONS, DECEMBER 2023

ND SEMESTER EXAMINATIONS, DESEMBER 20

ELECTRICAL MACHINERY-I [ELE 2123]

REVISED CREDIT SYSTEM

Time	: 3 Hours	05 December 2023	Max. Marks: 50
Instructions to Candidates:			
	✤ Answer ALL the question	ns.	
	 Missing data may be suit 	tably assumed.	
1A.	A 500 kVA, 11,000 / 415 on the secondary winding	V, 50 Hz, single-phase transforme g.	er has 100 turns 3
	Determine the following:		
	a) On full-load, primary	and secondary currents.	

- b) Primary turns.
- c) Based on answers to (a) and (b), comment on the physical dimensions of the conductors used in primary and secondary windings.
- d) If a tap-changer has to be installed, where will it be connected? With suitable reasoning, justify your answer.
- 1B. The following data were obtained on a 7.5 kVA, 500 / 250 V, 50 Hz single- $_{\mbox{4}}$ phase transformer:

Open-circuit test: 250 V, 1.25 A, 150 W (on low voltage side) Short-circuit test: 22.5 V, 15 A, 180 W (on high voltage side) Determine the following:

- a) kVA load for maximum efficiency.
- b) Value of maximum efficiency for unity power factor load.
- c) Analyze why the value of maximum efficiency will be lower for load power factor values other than unity.
- 1C. A 100 kVA, 11,500 / 2,300 V, 50 Hz, single-phase, two-winding transformer 3 should be connected as autotransformer. Draw the various connections possible for the autotransformer. Also, determine the corresponding voltage ratios and the kVA ratings.
- 2A. Three identical single-phase transformers each of rating 10 kVA, 200 V/100 V, 3 50 Hz are available. It is proposed to form a 3-phase transformer bank using these. Input line voltage of the transformer bank is $200\sqrt{3}$ V and the expected output line voltage is 100 V.
 - a) Choose a suitable combination for the connections of primary and secondary windings of the transformer bank.
 - b) Draw the connection diagram of the bank and analyse your choice.

- c) Determine the line currents on primary and secondary sides when this bank supplies full load.
- 2B. A 3-phase, 400 V, 50 Hz, 4 pole induction motor is rated for an output of 15 4 HP at 1,440 rpm. When supplying rated load, its stator losses are 800 W and 5 N-m of torque meets friction and windage losses. Determine the following for this loading:
 - a) Slip
 - b) Rotor copper loss
 - c) Input to the motor
 - d) Efficiency
- 2C. A three-phase squirrel cage induction motor is required to be used as a threephase generator. Explain how this can be achieved. Draw and explain the torque-slip characteristics for the entire operation indicating salient points.
- 3A. How is torque produced in a capacitor start single phase induction motor. Is 3 there any need for this capacitor after starting? Explain.
- 3B. A 415V, 3 phase, 50 Hz squirrel cage motor draws 5 times its full load current 3 during starting. Which of the following starters you would recommend?
 - a) Direct Online starter
 - b) Star- Delta starter

Give sufficient reasons. Also, draw the connection diagram of the motor and starter to the supply.

3C. A 4kW, 400V, 50Hz, 3 phase, 4 pole delta connected induction motor has stator resistance of 0.36 Ω per phase and rotor resistance of 0.06 Ω per phase. The no load and blocked rotor test data are as follows:
No load test: 400 V, 3.3 A, p.f =0.174
Blocked rotor test: 210V, 16A, p.f =0.45
Estimate the single-phase equivalent circuit of the induction motor.

- 4A. Explain and describe the effect of armature m.m.f. on the main field flux with 3 the help of magnetization curve of a DC generator.
- 4B. A 200V DC shunt motor takes 27A at rated load and runs at 800 rpm. Its field 3 resistance is 100 Ω and armature resistance is 0.5 Ω . Compute the power and torque developed by the motor at rated speed.
- 4C. With neat diagrams explain the process of commutation in DC machines.
- 5A. A 230V DC shunt motor is taking 5A during Swinburne's Test. The armature 3 resistance is 0.2 Ω and the filed circuit resistance is 115 Ω . If this motor is loaded such that it draws 72A on full load, Determine the efficiency of the motor.
- 5B. The speed of a 240V DC shunt motor must be increased above its base speed 3 for a particular application. Explain how this can be achieved?

4

5C. Design the resistance section of a three-point starter to be used with a DC 4 shunt motor of 220V, 1500 rpm. The maximum allowable starting current is 60A and the rated current is 30A. Consider the starter has 5 studs and the armature resistance is 0.5 Ω .