

Question Paper

Exam Date & Time: 05-Dec-2023 (09:30 AM - 12:30 PM)



MANIPAL ACADEMY OF HIGHER EDUCATION

THIRD SEMESTER B.TECH. DEGREE EXAMINATIONS - NOVEMBER / DECEMBER 2023
SUBJECT: ECE 2121- ANALOG ELECTRONIC CIRCUITS

Marks: 50

Duration: 180 mins.

Answer all the questions.

Missing data may be suitably assumed.

- 1A) The circuit shown in FIG.Q(1A) must be designed for a voltage drop of 200 mV across R_S . Assume $\mu_n C_{ox} = 200 \mu A/V^2$ and $V_{TH} = 0.4V$. (4)
- i) Calculate the minimum allowable value of (W/L) if 'M1' must remain in saturation.
ii) What are the required values of ' R_1 ' and ' R_2 ' for an input impedance of at least 30 K Ω ?

 


FIG.Q(1A)

- 1B) Draw the small signal model and determine the input impedance of the circuit shown in FIG.Q(1B). (3)
- Assume $\lambda = 0$.

 


FIG.Q(1B)

- 1C) An integrated circuit employs the source follower and the common-source stage as shown in FIG.Q(1C). Design a current mirror that produces I_1 and I_2 from a 0.3 mA reference. (3)

 


FIG.Q(1C)

- 2A) Design an amplifier to drive a 50Ω load with a voltage gain of 0.5 and a power budget of 10 mW. Assume $\mu_n C_{ox} = 100 \mu\text{A/V}^2$, $V_{TH} = 0.5\text{ V}$, $\lambda = 0$ and $V_{DD} = 1.8\text{ V}$. (4)
- 2B) Assuming $\lambda \neq 0$, compute the single-ended differential and common mode voltage gains for the circuit shown in FIG.Q(2B) using half circuit analysis. (3)

 


FIG.Q(2B)

- 2C) Design the circuit shown in FIG.Q(2C) for a voltage gain of 20 and a power budget of 1 mW with $V_{DD} = 1.8\text{ V}$. Assume ' M_1 ' operates at the edge of saturation for an input common-mode level of 1 V. Assume $\mu_n C_{ox} = 2\mu_p C_{ox} = 100 \mu\text{A/V}^2$, $V_{TH,n} = 0.5\text{ V}$, $V_{TH,p} = -0.4\text{ V}$, $\lambda_n = 0.5$ and $\lambda_p = 0.1\text{ V}^{-1}$ (3)

 


FIG.Q(2C)

- 3A) For the circuit shown in FIG.Q(3A), find the input and output poles at high frequencies for $\lambda \neq 0$. Sketch the frequency response. (4)

 


FIG.Q3(A)

- 3B) For the circuit shown in FIG.Q3(B), find the poles at low frequencies. Also, sketch its low frequency response. Assume $\lambda = 0$. (3)

 


FIG.Q3(B)

- 3C) For the circuit shown in FIG.Q(3C), find the pole frequencies and sketch the frequency response. (3)

 


FIG.Q(3C)

- 4A) Determine the closed-loop gain, I/O impedance of the circuit shown in FIG. Q(4A), assuming $R1 + R2$ is very large & $\lambda = 0$. (4)

 


FIG. Q(4B)

FIG. Q(4C)

5B) Explain the working principle of ring oscillator with a neat circuit diagram. Obtain the expressions for (3)
minimum gain and frequency of oscillation. Also, find the frequency of oscillation for drain resistance
and capacitance of $1\text{K}\Omega$ and $1\mu\text{F}$.

5C)

Explain the working principle of class AB amplifier with circuit diagram.

(3)

-----End-----