



VII SEMESTER B. TECH (ELECTRICAL & ELECTRONICS ENGINEERING) END SEMESTER EXAMINATIONS, DECEMBER 2023

MODERN POWER CONVERTER [ELE 4085]

REVISED CREDIT SYSTEM

Time: 3 Hours

Date: 05 DECEMBER 2023

Max. Marks: 50

Instructions to Candidates:

- ❖ Answer **ALL** the questions.
- ❖ Missing data may be suitably assumed.

- 1A.** Make a technical comparison between AT and ATX Power supply. (02)
- 1B.** State and prove ampere-second balance and volt-second balance. Also, establish the relationship between input voltage and output voltage for Boost-type DC-DC converters by applying ampere-second balance to the capacitor. (04)
- 1C.** Design a suitable converter to charge a battery voltage of 400V. The input to the converter varies from 380V to 420V. The operating frequency is 20kHz and the converter is supplying a load of 1.6kW. Assume all are ideal components. (04)
- 2A.** You are assigned to design a power electronic LED driver suitable for a Honda City car LED Bumper Light of 100W with a voltage rating of 12V power from the car battery supply of 48V. (i) Select Forward converter type dc-dc converter suited for this driver. Find maximum and minimum values of inductor currents(ii) Design the number of turns and capacitors for this converter. Assume the output voltage ripple is 0.5%, inductor $L_x = 0.5\text{mH}$, the duty ratio is 0.4, and the switching frequency is 35 kHz. (04)
- 2B.** Classify the different soft switching techniques that can be developed to enhance the efficiency of the converters. (03)
- 2C.** Analyze the load current, diode current, and inductor voltage of a current-fed DC-DC converter. Derive an expression to estimate the output voltage. (03)
- 3A.** Design a fly-back converter and its component selection with the step-by-step procedure. Converter Operating with continuous conduction mode as shown in Fig.Q.no.3A.

V_{in}	40 to 90V
V_{out}	24V
I_0	1 AMP

(04)

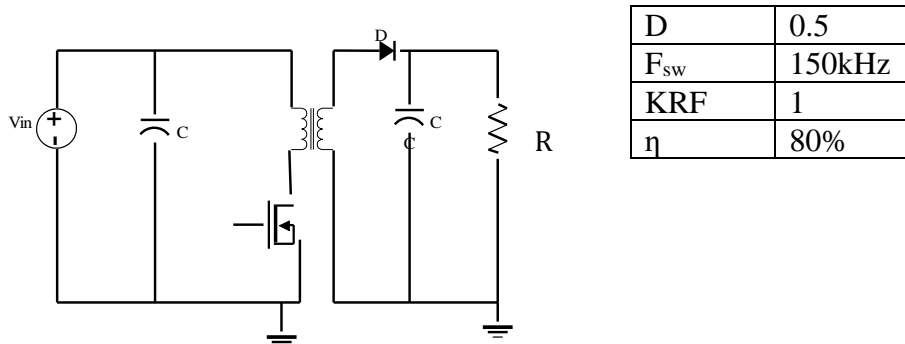


Fig.Q.no. 3A

- 3B. Describe the working of series load resonant converter with waveform of resonant inductor current and capacitor voltage operating under leading power factor. (04)

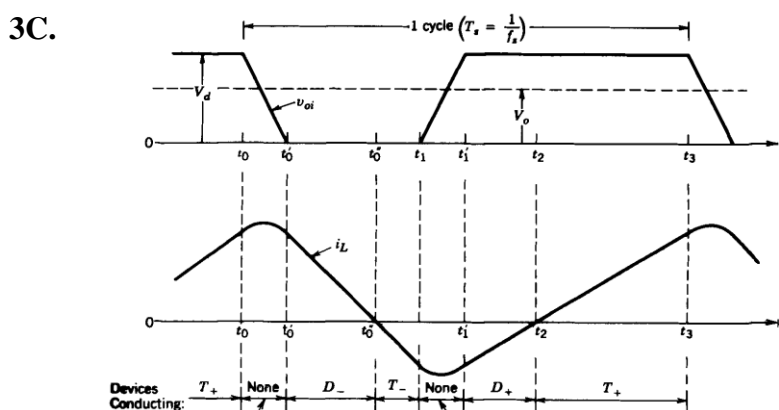


Fig.no.3C.

- With the reference of Fig.Q.no 3C. identify suitable converter Topology in switched mode power converter. (02)
- 4A. Analyze the waveform of resonant inductor current and capacitor voltage of a buck converter. The switch is required to conduct a peak Voltage that is higher than the source voltage V_s by an amount $I_o Z_o$ and explain its circuit properties. (04)
- 4B. A parallel loaded resonant converter is having the source voltage of 150V, resonant inductor and capacitor are $18\mu\text{H}$ $C_r = 0.82\mu\text{F}$, load resistance is $R_L = 10\Omega$, and switching frequency is $f_s = 120\text{kHz}$. Determine the output voltage of the converter. Assume the output filter components L_o and C_o produce a ripple-free output current and voltage. Justify the output voltage of the converter. Refer Fig.Q.no 4B. (04)

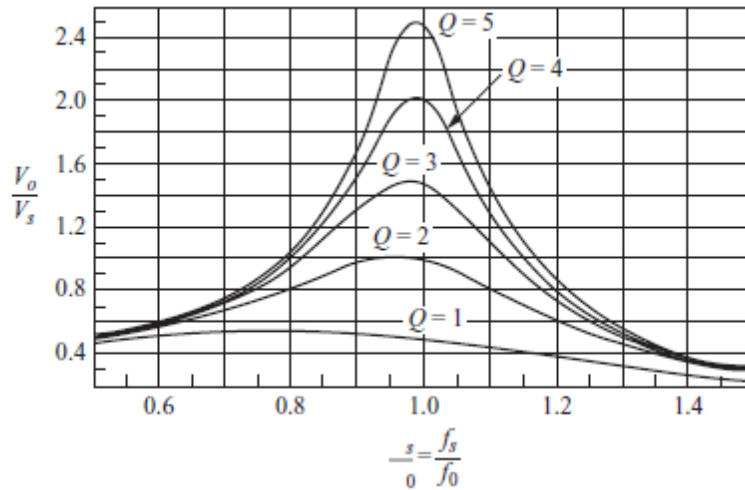


Fig.Q.no.4B.

- 4C.** Explain steady state characteristics and its important properties of a parallel-loaded resonant dc-dc converter (02)
- 5A.** Explain the parameters that need to be calculated for the inductor design in switched mode power supply. (03)
- 5B.** Develop a small signal AC model of the buck-boost converter with step-by-step procedure. Assuming ideal components and continuous conduction mode. (04)
- 5C.** Design a high-frequency transformer for the full bridge dc-dc converter. The source voltage is 48V the output voltage is 24V, the operating frequency of the converter is 20KHz, the load has 8Ω resistance. Assume the output voltage ripple is 1% and input voltage fluctuation is 10%, refer to the core selector chart in Table 1. (03)

Table 1: Physical Electrical and Magnetic characteristics of ferrite core

Core	Mean Length(mm ²)	Mean Magnetic length lm(mm ²)	Core cross-section (Ac*100mm ²)	Window area (Aw*100mm ²)	Area Product (Ap*10 ⁴ mm ²)	Effective relative permeability $\mu_r \pm 25\%$	A_L nh/TURNS ² $\pm 25\%$
P18/11	35.6	26	0.43	0.266	0.114	1480	3122
P 26/16	52	37.5	0.94	0.53	0.498	1670	5247
P30/19	60	45.2	1.36	0.747	1.016	1760	6703
P36/22	73	53.2	2.01	1.01	2.010	2030	9500
P42/29	86	68.6	2.64	1.81	4.778	2120	10250
P66/56	130	123	7.15	5.18	37.03		