

Question Paper

Exam Date & Time: 27-Nov-2023 (10:00 AM - 01:00 PM)



MANIPAL ACADEMY OF HIGHER EDUCATION

Manipal School of Information Sciences (MSIS), Manipal
First Semester Master of Engineering - ME (VLSI Design / Microelectronics and VLSI Technology) Degree Examination -
November / December 2023

High Level Digital Design [VLS 5001]

Marks: 100

Duration: 180 mins.

Monday, November 27, 2023

Answer all the questions.

- 1) Solve the following by converting them to single precision floating point numbers. (10)
 - $0.525 - 0.325$
 - $0.75 \times (-0.125)$. CO1, PO3, BL3
- 2) Apply the combinational logic design to detect a given number is between 5 to 13 when the input is 4-bit. Also draw the optimal circuit. CO1, PO3, BL3 (10)
- 3) Demonstrate funnel shifter design to shift 4-bits input with relevant explanation. CO2, PO3, BL3 (10)
- 4) Design and draw the circuit for a divided by 4 clock frequency circuit and explain its working principle. CO3, PO3, BL6 (10)
- 5) Design and draw a combined Moore FSM for detecting the sequences 001 and 100. Optimize the states using implication method and draw the circuit. CO3, PO3, BL6 (10)
- 6) Solve for total delay of the circuit (a) and hold slack for circuit (b) (10)

