Reg. No.



(A constituent unit of MAHE, Manipal)

IV SEMESTER B.TECH (ELECTRICAL & ELECTRONICS ENGINEERING)

END SEMESTER EXAMINATIONS, MAY 2024

POWER ELECTRONICS [ELE 2222]

REVISED CREDIT SYSTEM

Time:18	0 Minutes Date:	03 May 2024	Max. Marks: 50	
Instructions to Candidates:				
*	Answer ALL the questions.			
*	Missing data may be suitably assumed.			
1A.	 A half-wave uncontrolled rectifient 100Ω. The AC source is 230V rm (i). Determine the average load we (ii). Sketch the waveforms of load (iii). Subsequently, introduce a deredraw the above waveform dynamics following the incorport 	er is interfaced with a resistive is at 50Hz. With a neat circuit, voltage and average load current d current and load voltage. capacitor across the resistive lo s in (ii). Discuss the changes in poration of the capacitor.	load of :. ad and circuit (04)	
1B.	A single-phase full wave-contro operates from a 230 V, 50 Hz A	lled bridge rectifier feeding an C supply.	RL load	
	(i)With a neat circuit, discuss the conduction of the conduction o	the operation of the converter tion mode (CCM).	with RL	
	(ii)The converter provides an a a angle of 60° in CCM. Determine	verage load current of 10 A at the average load voltage.	a delay	
	(iii)For the firing angle of 60°, sl voltage, load current and SCR v	<etch state="" steady="" the="" waveform<br="">oltage (Sketch upto one cycle)</etch>	of load (04)	
1C.	For the converter in Q 1B, if connected across the output for angle, calculate the new average the steady state waveforms of upto one cycle)	a freewheeling diode (FWD) the same RL load and the sam ge load voltage with the FWD. load voltage and load current	is now le firing Redraw (Sketch (02)	
2A.	A single-phase full wave ac volt with an input voltage of 120V, 1.535 radians. Calculate (i) rms (iii) input power factor. (iv) rms	age controller feeds a load of R 60Hz. Firing angle for both the value of output voltage (ii) load SCR current.	= 15 Ω SCRs is d power (04)	
2B.	Analyse the operation of a built schematic and sketch the follow	ck dc dc converter with a neat ing waveforms.	: circuit	
	(i). Inductor current and inducto (ii). Capacitor current and capacit	r voltage :or voltage	(03)	

2C. An employee of a company was asked to design a power converter for the specifications shown in Table 1.

Input Voltage	8 V			
Output Voltage	4 V			
Output Current	1 A			
Switching frequency	200 kHz			
Inductor current	40%			
ripple				
Output Voltage ripple	2%			
Inductance (L)	12.5 µH			
Capacitance (C)	15.625 uF			

Tahle	1.	Specifications
Iable	т.	Specifications

The employee selects a boost topology as the power converter. Hence evaluate the design and answer the following questions:

(i). Is the boost topology ideal for the design specifications mentioned in Table 1? If not, suggest a better topology.

(ii). Are the designed values of L and C in Table 1 meeting the specifications and ripple considerations? Are they underrated or overrated? Justify with appropriate calculations.

- **3A.** A single-phase AC load requires a voltage of 100V rms at 50 Hz and is purely resistive. In the laboratory setting, there's a 100V DC supply. The designer's task is to select between a half bridge and a full bridge square wave inverter for connecting the DC supply to the AC load to meet the specified requirement. Justify your choice by providing a circuit diagram along with the following waveforms (Sketch upto 2 cycles):
 - (i) Load voltage and load current
 - (ii) Gating pulses
- **3B** A single-phase full bridge square wave inverter has a resistive load of R =10 Ω and a DC input voltage of Vs = 100 V. The desired output frequency is 50 Hz. Determine
 - (i). RMS of output voltage
 - (ii). RMS output voltage of fundamental component
 - (iii). The output power

(iv). THD

(v). The Harmonic factor of the third harmonic

(vi). The peak current and peak voltage of the switch.

- **3C** Discuss the advantages of PWM inverters and outline the difference between bipolar and unipolar PWM switching scheme.
- **4A** A three-phase bridge inverter delivers power to a resistive load from a 450V dc source. For a star connected load of 10 ohms per phase, the inverter is operated in 180° mode of conduction. The switch used in the circuit has a peak voltage rating of 600V and peak current rating of 20A. With a neat circuit diagram, evaluate the following.

(i). Compute rms value of load phase voltage and the rms value of the load current.

(ii). Compute the power consumed by the three-phase load.

(iii) Verify if the rating of the switch is meeting the design criteria of the circuit.

(iii) Sketch the waveforms of any one phase voltage upto one cycle.

(03)

(03)

(03)

(04)

- **4B** A single-phase full bridge inverter is used to produce a 50Hz voltage across a series R-L load using bipolar PWM, with R= 12Ω and X_L=16 Ω . The dc input to the bridge is 100V. The carrier signal has a frequency of 5kHz and a peak value of 1V. The control signal has a frequency of 50 Hz and a peak value of 0.8 V.
 - (i). Specify the amplitude modulation ratio and the frequency modulation ratio.
 - (ii). Calculate the peak amplitude of fundamental component of output voltage.
 - (iii). Calculate the peak amplitude of fundamental component of output current.
 - (iv). Sketch the harmonic spectrum of the load voltage
- **4C** Discuss the key considerations and design aspects related to gate drivers. Categorize the various types of gate drive circuits based on their functionalities and applications
- **5A** The Power MOSFET is used to switch a load of 5 Amps from 10 V supply at a duty cycle of 0.5 as shown in Figure 1. The switching frequency f_s is 100kHz and the duty cycle of operation D is 0.5. The On-state resistance $R_{DS(on)}$ of the MOSFET is 50m Ω . The turn on time and the turn off time of the MOSFET is same and is given as $t_{ON}=t_{OFF}=2ns$.
 - (i) Estimate the conduction loss and switching loss in the Power MOSFET.
 - (ii) Sketch the turn on and turn off switching characteristics of the Power MOSFET.

[Given: The RMS of the drain current through the MOSFET is $I_{Drms} = I_{D(ON)}\sqrt{D}$]



(i)Determine the corresponding value of the duty cycle applied to the boost converter required to extract the maximum power from the solar modules.

(ii)Draw the block diagram of the entire system

5C Draw the block diagram of an electric drive and explain the role of power electronic converters in the electric drive system

(03)

(05)

(03)

(03)

(02)



Figure 1