Reg. No.



(A constituent unit of MAHE, Manipal)

REDRY

DEPARTMENT OF ELECTRICAL & ELECTRONICS ENGINEERING II SEMESTER M.TECH. (ELECTRIC VEHICLE TECHNOLOGY) MAKE UP EXAMINATIONS, JUNE 2024

POWER CONVERTERS FOR ELECTRIC VEHICLES [ELE 5415]

Time: 3	Hours Date: 21 June 2024	Max.	Marks: 50
1A.	With the help of circuit topology, switching sequence, and overlage waveforms, explain the working of an H bridge in selecting a simple square wave switching scheme.	output verter	(05)
1B.	A single phase fully controlled rectifier is supplied with 230V 50 supply. Considering a DC motor armature as the load, and enough inductance is added for continuous conduction,a) Calculate the average output voltage of the rectifier at a firing of 45 degrees.	Hz AC ı filter angle	
	b) Draw the waveforms of output voltage and current.c) Suggest few methods to ensure continuous conduction		(05)
2A	Consider the listed single phase converters. Differenciate them on the devices used and the possible quadrants of operation. Also the output voltage waveform in each case at a suitable firing angl RLE load.	based draw e with	 ,
	a) Uncontrolled rectifier c) Fully controlled rectifier.		(05)
2B.	Does interleaved DC-DC converter is able to achieve bidired feature? Justify your answer. Also explain the circuit topolog working.	tional y and	(05)
3A.	What is the concept behind inductive charging? Explain each state the converter configuration with an inductive charging system suitable schematic diagram.	age of 1 with	(05)
3B.	Consider a single-phase fully controlled bridge rectifier feeding th armature of a separately excited DC motor. The power supply to rectifier is 240 V, 50Hz. The motor needs to be operated at the ra speed. At what firing angle, the rated speed can be achieved?	ie the ated	
	Motor ratings: 220V, 16A, 1000rpm, Armature winding resistance $1.1 \ \Omega$. Assume continuous conduction.	e is	(05)
4 A .	 Consider a three-phase H bridge inverter configuration. a) Explain the working of the converter with sinusoidal switching scheme. b) Also draw and explain the harmonic exects of the converter with sinusoidal successful and explain the harmonic exects. 	PWM	
	voltage.	ντρυτ	(05)

4B.	What is the input-output voltage relationship of a boost DC-DC converter. Derive the expression for the same.	
	A DC link voltage needs to be maintained at 220 V for an application where the battery bank can provide 80V. What should be the duty cycle of operation of a boost converter which is used for this conversion.	(05)
5A.	Demonstrate the need of powerfactor correction, in electric vehicle charging system, with the help of suitable block schematic diagrams. Also differentiate the terms, distortion power factor & displacement	(05)
5B.	Write a technical note on Matrix converter and its application in electric	()
	vehicles	(05)