



II SEMESTER M. TECH (EMBEDDED CONTROL AND AUTOMATION)
END SEMESTER EXAMINATIONS MAY 2024
VLSI SYSTEM DESIGN (ICE 5412)

Time:3 Hours

09-05 -2024

MAX. MARKS: 50

Instructions to Candidates:

- ❖ Answer **ALL** the questions.

Q.No.	Description	M	CO	PO'S	BL
1A	Differentiate between enhancement mode and depletion mode transistors.	3	1	5	4
1B	An nFET with $L=0.5 \mu\text{m}$ is built in a process where the process transconductance is $100 \mu\text{A} / \text{V}^2$ and $V_{Tn} = 0.7 \text{V}$. The gate source voltage is set to a value of $V_{Gsn} = V_{DD} = 3.3 \text{V}$. Calculate the required channel width 'W' to obtain a resistance $R_n = 950 \Omega$.	3	1	4	3
1C	Calculate the total capacitance C_{out} of the NOT gate shown in figure 1C with a load capacitance $C_L = 120 \text{fF}$.	4	2	4	3

 


Figure 1C

2A	A CMOS logic gate that implements the function: $f = \overline{(a + b). (b + c). d}$ <p>is needed in a control network. Design the logic circuit with device sizes in the gate that equalize the nFET and pFET resistances. Identify the worst-case nFET and pFET paths that will slow down the response.</p>	4	2	4	5
2B	With equations, illustrate how device parameters (any six) of a MOSFET are scaled using the constant voltage scaling model.	3	2	5	3
2C	Compare and contrast the working of pass transistors and transmission gates.	3	2	4	4
3A	Sketch the transistor-level schematic and stick diagram for implementing the following function: $f = \overline{a.b.c + a.d}$	3	3	4	3

- 3B** Consider the two designs of a 2-input AND gate shown in Figure 3B (a) and (b). Justify which of the two circuits will be faster with a calculation of the path effort, delay, and input capacitances x and y to achieve this delay. 4 3 4 5

 


Figure 3B

- 3C** Sketch a transistor level schematic of a pseudo-nMOS gate that implements the function: 3 3 4 3

$$F = \overline{A(B + C + D) + E.F.G}$$

- 4A** Sketch the transistor level schematic of a clocked JK latch. 3 3 4 3

- 4B** Implement the following state table using a ROM and two D flip-flops where 'X' is the input and 'Z' is the output and S_0, S_1, S_2 and S_3 are the states: 3 4 4 3

Present State	Next State		Output (Z)	
	X=0	X=1	X=0	X=1
S_0	S_0	S_1	0	1
S_1	S_2	S_3	1	0
S_2	S_1	S_3	1	0
S_3	S_3	S_2	0	1

Draw the block diagram and the ROM truth table.

- 4C** Illustrate different programming technologies of an FPGA with figures. 4 4 5 3
- 5A** With a flowchart, illustrate the design flow starting from the specification of a chip to its implementation. 4 4 5 3
- 5B** Compare the three main approaches followed in design for testability in VLSI systems. 3 5 5 4
- 5C** Interpret the different types of IC packaging techniques that are available in VLSI systems. 3 5 5 3