Question Paper

Exam Date & Time: 30-Apr-2024 (10:00 AM - 01:00 PM)



MANIPAL ACADEMY OF HIGHER EDUCATION

Manipal School of Information Sciences (MSIS), Manipal Second Semester Master of Engineering - ME (VLSI Design / Microelectronics and VLSI Technology) Degree Examination - April / May 2024

Physical Design Elective -2 [VLS 5234]

Marks: 100

Tuesday, April 30, 2024

Answer all the questions.

¹⁾ Differentiate two input NOR and NAND gate circuit using CMOS logic. Explain ⁽¹⁰⁾ their transistor sizing considering a reference inverter of size 3/1.

CO - 1, BT-4, Marks-10

Duration: 180 mins.

- ²⁾ Distinguish dynamic logic from static CMOS logic including suitable examples ⁽¹⁰⁾ CO - 1, BT-4, Marks-10
- ³⁾ Implement reduced order binary decision diagram for the circuit given below ⁽¹⁰⁾ CO - 2, BT-3, Marks-10



⁴⁾ Examine whether the following circuit meets a timing cycle = 11? Show the different steps to calculate Arrival Time, Required Arrival Time, and Slack.

CO - 3, BT-4, Marks-10





- ⁵⁾ Sketch height and width of ASIC and Core logic. Describe clock planning. ⁽¹⁰⁾ CO - 3, BT-4, Marks-10
- ⁶⁾ List the objectives of routing? Explain Source to sink, Minimum spanning tree ⁽¹⁰⁾ and Half-perimeter methods in routing with suitable examples CO 4, BT-2, Marks-10
- ⁷⁾ Explain the different types of capacitances considered in the extraction (10) procedure after the layout? CO - 4, BT-2, Marks-10
- ⁸⁾ Differentiate between verification and testing. Compute the probability of fault ⁽¹⁰⁾ in a system with 10 million transistor and the probability of fault of individual transistor is 0.1 micron CO - 5, BT-4, Marks-10
- ⁹⁾ Solve for the input vectors for detecting the stuck at faults using faulty expressions for

 (a) x1 stuck at 0 (b) x2 stuck at 1

CO - 5, BT-3, Marks-10





¹⁰⁾ Solve for the test vector for the s-a-0 shown using D algorithm



(10)



-----End-----